



**Hochschule
Augsburg** University of
Applied Sciences

Test Signal Generator

VLSI-Design Module - Report

L Hillinger, D Cunnigham, R Dillon

SS2021

Contents

1	Introduction	5
2	Features	5
3	Functional Description	6
3.1	UART serial communication	6
3.2	Digital pattern generator	6
3.3	Pulse-width modulation	7
3.4	Pseudo-random number generator (LFSR)	7
4	General Description	8
4.1	Pwm component	13
4.2	Noise component	13
4.3	Pattern component	13
5	Design Description	14
5.1	UART serial receiver	14
5.1.1	Data received after reset	16
5.2	Pattern generator	16
5.3	Pulse-width modulation	18
5.4	Pseudo-random number generator (LFSR)	19
5.5	External time base and external triggering design	19
6	Test Results	21
6.1	Noise Generator	21
6.2	PWM Generator	23
7	Application Note	25
8	Further Improvements	26
8.1	System control register	26
8.2	Pwm switch off	26
8.3	Testbench tsg and de1_tsg	26
8.4	More test scenarios	27
9	References	27
10	Appendix	27
10.1	Device Utilization and Performance	27
10.2	Project Hierarchy	27
10.3	Module Hierarchy	29
10.4	Code	30

List of Tables

1	Test Signal Generator - Description of I/O Signals	8
2	I/O Table for the Serial Reciever	14
4	I/O Table for the Pattern Generator	17
5	I/O Table for the PWM Generator	19
6	Results from testing the Noise Generator	22
7	Results from testing the PWM Generator	24

List of Figures

1	UART Example- Schematic	6
2	Expected output of the pattern generator	6
3	PWM Example - Schematic	7
4	LFSR Exampled - Schematic	8
5	Test Signal Generator Schematic Symbol	8
6	Pwm implementation	13
7	Implemented Serial Receiver File - Schematic	14
8	UART Serial Reciever State Machine File - Schematic	15
9	Data out valid after reset	16
10	Pattern Generator State Machine File - Schematic	17
11	Implemented PWM File - Schematic	18
12	Noise/PWM enable and external trigger design	19
13	Pattern enable and external trigger design	20
14	Oscilloscope readings of the Noise Generator with a period and width of one. . .	21
15	Oscilloscope readings of the Noise Generator with a period and width of one. Example of bitwidth	22
16	Oscilloscope readings of the PWM Generator with a period and width of one. Example of bitwidth	23
17	Oscilloscope readings of the PWM Generator with a period and width of 127. Example of bitwidth	24
18	Connected components on DE1 Altera Board	26
19	State Machine Fix	27

1 Introduction

Digital test signal generators (TSG) are a type of external measurement equipment that are available from several different vendors. These pieces of equipment produce a range of electrical stimuli signals that can be used to check the operation of other electrical devices. The goal of this module is to produce an on-chip version of this system with the following essential features included in the architecture and design: - Single pulse with variable duty cycle and frequency. - Digital noise based on pseudo random binary sequences of different length. - Arbitrary data bus sequences at selectable speed. - Internal/External Trigger. - External Time Base. Each of these features are necessary for the TSG to produce a data-set that can be used to give an engineer an informative viewpoint on their design so that they can modify it so that it lands within specification.

2 Features

These features are key to the TSG as they are utilised in many commercially available TSGs as such they are included in this TSG.

- Serial Transmission

Utilizing UART serial transmission allows for a large range of data to be transferred between the TSG and the subject system. It allows for the TSG to be given Parallel inputs and then communicate using serial transmission which can then be returned to a parallel data type for the target system to utilise.

- Single pulse with variable duty cycle and frequency

Utilising Pulse width modulation a series of digitally controlled electrical signals can be sent allowing for a spectrum of both peak voltage and high frequency testing within a single module.

- Digital noise based on pseudo random binary sequences of different length

Utilising LFSRs to generate a string of pseudo random binary that is then sent along the UART transmission lines to the subject board. It allows for the subject system's ability to handle junk data as well as other highly variable data types.

- Arbitrary data bus sequences at selectable speed

Utilising digital pattern generators to create arbitrary data busses that can then be sent using UART to a subject board. As the output of this system is arbitrary it allows for the clarity of transmissions that are sent to the subject board.

- Internal/External Trigger

Internal and external triggers allow for the TSG to be triggered by internally set rules or received data from the test subject system allowing for specific internal rules to be set up. External triggers allow for specific targeted stimulus to be produced by the TSG meaning that any of the above test types can be used with a high level of precision.

- External Time Base

An external time base allows for the entire TSG to be configured based on the system to be tested by the TSG system. As well as allowing for the TSG to be run at a different clock rate to the tested system.

3 Functional Description

3.1 UART serial communication

UART communication is a common form of data communication between electronic devices. It communicated the data serially in the form of digital signals.

 


Figure 1: UART Example- Schematic

UART communication has some characteristics that need to be considered for implementation. The signal begins with start bit (in the form of a high signal), the next in the sequence comes the data bits, the number of data bits is configurable and is dependant on the parameterisation of the serial modules. After the data sequence is complete, UART protocol then instructs you to send a stop bit, which is again a high signal.

3.2 Digital pattern generator

 


Figure 2: Expected output of the pattern generator

Digital Pattern Generators are a common way of creating signal for testing. Theoretically the Pattern Generator should allow the user to output a configurable pattern. The pattern can take various shapes, including standard pulses or outputting larger bit patterns depending on the system configuration.

3.3 Pulse-width modulation

Pulse Width Modulation (PWM) is a type of digital signal that has many uses for real world applications. It is a way in which you can digitally control some analog devices.

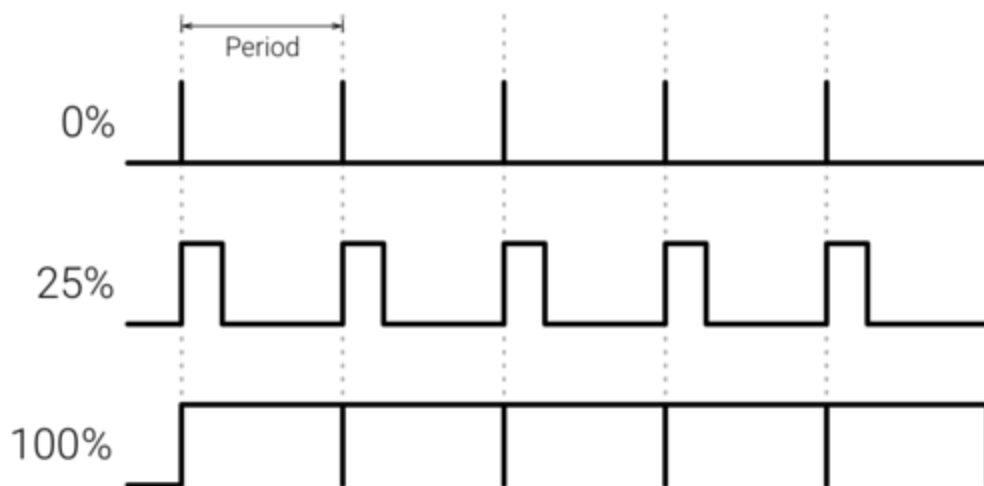


Figure 3: PWM Example - Schematic

PWM functions by switching between low and high signals to the requested amounts by the user. For each cycle, the signal will be high for the requested percentage. This is known as the Duty Cycle.


$$Period = \frac{1}{f}$$

$$Period = T_{on} + T_{off}$$

$$DutyCycle = \frac{T_{on}}{T_{on} + T_{off}} \times 100$$

 3.4 Pseudo-random number generator (LFSR)

Linear Feedback Shift Registers is a configuration of registers used in conjunction with an XOR gate to create a function dependant on it's previous state.



The number of cycles until the pseudo random number generator repeats himself is:
 $number\ of\ cycles = 2^n - 1$

With n as number of bits.

4 General Description




Table 1: Test Signal Generator - Description of I/O Signals

Name	Type	Direction	Polarity	Description
clk_i	std_ulogic	IN	HIGH	clock

Name	Type	Direction	Polarity	Description
rst_ni	std_ulogic	IN	LOW	asynchronous reset
en_tsg_pi	std_ulogic	IN	HIGH	external time base
en_serial_i	std_ulogic	IN	HIGH	oversample of 16, baudrate 9600
serial_data_i	std_ulogic	IN	HIGH	serial data, baudrate 9600
rxd_rdy_o	std_ulogic	OUT	HIGH	serial data ready to read
ext_trig_i	std_ulogic	IN	HIGH	external trigger
pwm_o	std_ulogic	OUT	HIGH	pwm signal
noise_o	std_ulogic	OUT	HIGH	1 bit pseudo random noise
prbs_o	std_ulogic_vector[23]	OUT	HIGH	pseudo random noise up to 23 bit
eoc_o	std_ulogic	OUT	HIGH	end of cycle of pseudo random noise
pattern_o	std_ulogic_vector[8]	OUT	HIGH	pattern output
pattern_valid_o	std_ulogic	OUT	HIGH	pattern valid
tc_pm_count_o	std_ulogic	OUT	HIGH	end of cycle pm upcounter
regfile_o	std_ulogic_vector[8]	OUT	HIGH	data input register file
addr_reg_o	std_ulogic_vector[8]	OUT	HIGH	address output serial register
data_reg_o	std_ulogic_vector[8]	OUT	HIGH	data output of serial registers

The test signal generator with its multiple I/Os can be broken down into 4 distinctive parts: - serial data handling - pulse width modulation generator - pattern generator - random noise generator

tsg

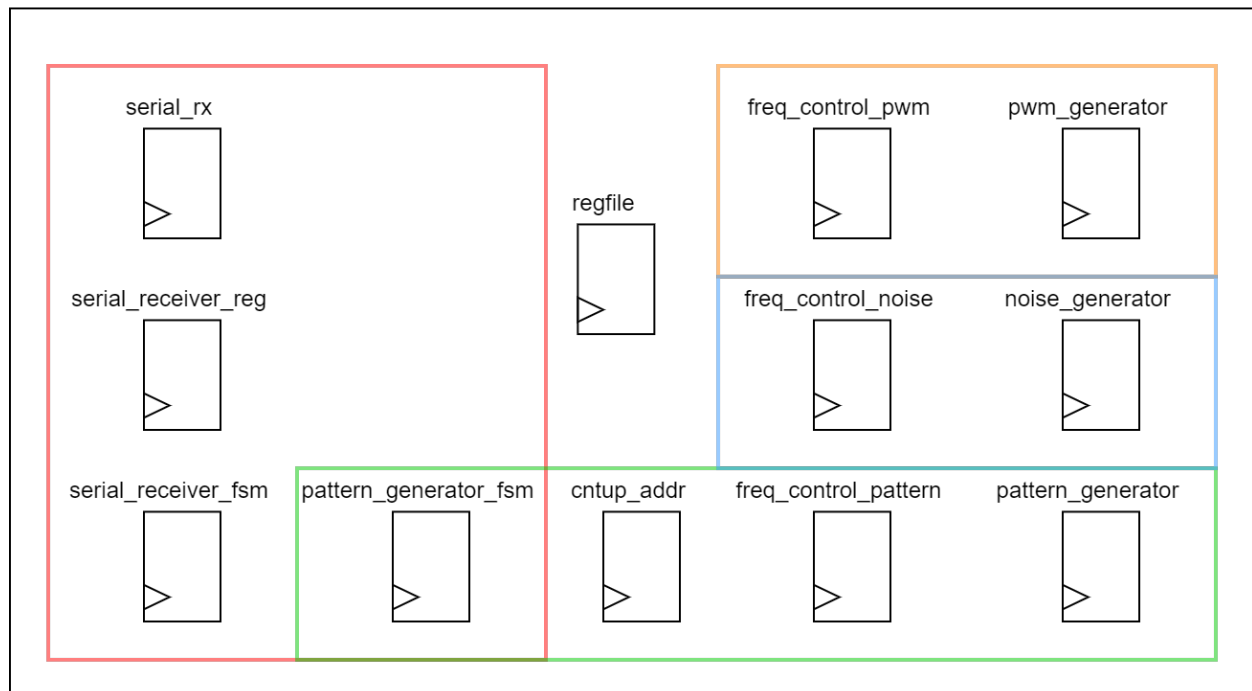

In the picture above you can recognize that the register file is the central part of the design. The register file receives data from the serial communication and writes them into its memory. Depending on the values in the memory the output components are controlled.

The register file has the following memory view.

		Bit7	..					0	

Address	Name	7	6	5	4	3	2	1	0

0x00									
0x01	system control							x	x
0x02									
0x03									
0x04	pwm pulse width	x	x	x	x	x	x	x	x
0x05	pwm period	x	x	x	x	x	x	x	x
0x06	pwm control							x	x
0x07									
0x08	noise prbsg length	x	x	x	x	x	x	x	x
0x09	noise period	x	x	x	x	x	x	x	x
0x0A									
0x0B	noise control							x	x
0x0C	pattern length	x	x	x	x	x	x	x	x
0x0D									
0x0E	pattern period	x	x	x	x	x	x	x	x
0x0F	pattern control							x	x

The meaning of the control parts of the registers is explained in the following.

system control

Bit 0 Meaning

0 system disable

1 system enable

Bit 1 Meaning

1 system clear [synchronous clear](not currently implemented see impr

pwm control

Bit 0 Meaning

0 pwm off

1 pwm on

Bit 1 Meaning

0 internal trigger

1 external trigger

noise prbsg length

Bit 7 6 5 4 3 2 1 0 Meaning

0 0 0 4-bit

0 0 1 7-bit 8B/10B-encoded pattern

0 1 0 15-bit ITU-T 0.150

0 1 1 17-bit OIF-CEI-P-02.0

1 0 0 20-bit ITU-T 0.150

1 0 1 23-bit ITU-T 0.150

noise control

Bit 0 Meaning

0 noise off
1 noise on

Bit 1 Meaning

0 internal trigger
1 external trigger

pattern control

Bit 1 0 Meaning

0 0 stop
0 1 single burst
1 0 continuous run
1 1 load data

Bit 2 Meaning

0 internal trigger
1 external trigger

Now the control part of the register will be explained in further detail. The system has an general enable “system control” which must be switched on to switch on all individual components (noise, pattern, pwm). All components allow for external triggering where you can change the state manually by pressing a button. When not specified the components run with the speed of the external time base which is further divided by the individual period settings. All three components have the same frequency divider component. The divided frequency can be calculated by the following formula:

$$\text{divided frequency} = \frac{\text{frequency of external time base}}{\text{period register value} + 1}$$

4.1 Pwm component

 


Figure 6: Pwm implementation

With the implemented pwm component a duty cycle of 0%-99,6% percent is possible. It can be computed by $duty\ cycle = \frac{pwm\ pulse\ width}{256}$. One counting cycle is performed with the frequency of the divided frequency. This results in a frequency of $\frac{divided\ frequency}{256}$.

4.2 Noise component

The noise component has an noise prbsg length and a period setting. The prbsg setting decides how many bits the lfsr has. That means it decides over the length of the pseudo random sequence until it repeats itself. They are designed after the given standards of pseudo random number generators and have different use cases. For more information about it see the standard documentations. One full cycle has the frequency of $\frac{divided\ frequency}{2^n - 1}$ with n as the number of bits of the lfsr.

4.3 Pattern component

The pattern generator has four possible control states: - stop - the pattern generator is switched off - load - the pattern generator is ready to receive the data sequence into its memory - before sending the number sequence the number of values must be specified in the pattern length register! - e.g. pattern length 4 -> pattern load -> pattern sequence 4 5 7 2 -> single burst/continuous run - single burst - a single burst puts out the sequence only once - continuous run - puts out the sequence forever - stops when the pattern control bits change One value of a sequence is available for the time of $\frac{1}{divided\ frequency}$. A full cycle that includes all values has the frequency of $\frac{divided\ frequency}{pattern\ length}$.

5 Design Description

5.1 UART serial receiver

The serial receiver module is based on a design made using a Moore state machine and it was provided to the design team by the design manager. The purpose of the module is to allow for the correct sequencing and addressing of the data. The module functions by using a synchronous high active reset. This state machine directly communicates with the other state machine present on the project directly via the data valid signal, signalling that the data has arrived.

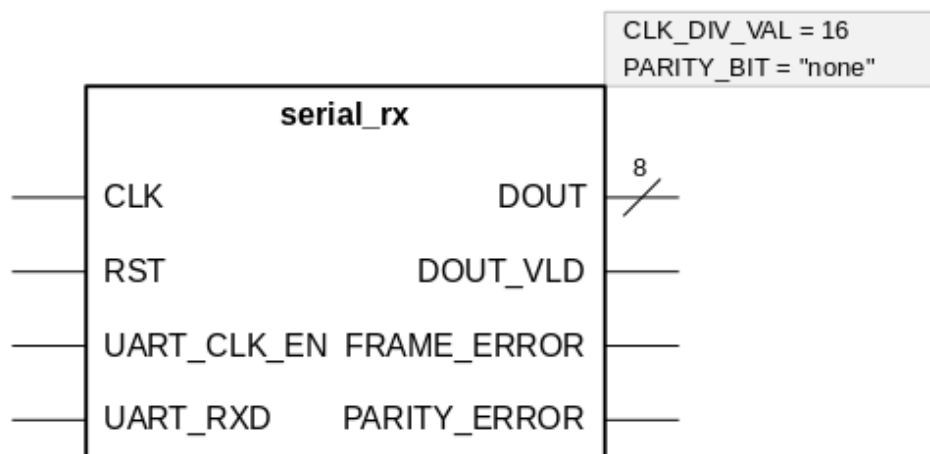


Figure 7: Implemented Serial Receiver File - Schematic

Table 2: I/O Table for the Serial Receiver

Name	Type	Direction	Polarity	Description
CLK	std_ulogic	IN	HIGH	
RST	std_ulogic	IN	HIGH	
UART_CLK_EN	std_ulogic	IN	HIGH	
UART_RXD	std_ulogic	IN	HIGH	
DOUT	std_ulogic_vector[8]	OUT	HIGH	
DOUT_VLD	std_ulogic	OUT	HIGH	
FRAME_ERROR	std_ulogic	OUT	HIGH	
PARITY_ERROR		OUT	HIGH	

Name	Type	Default value
CLK_DIV_VAL	integer	16
PARITY_BIT	string	"none"

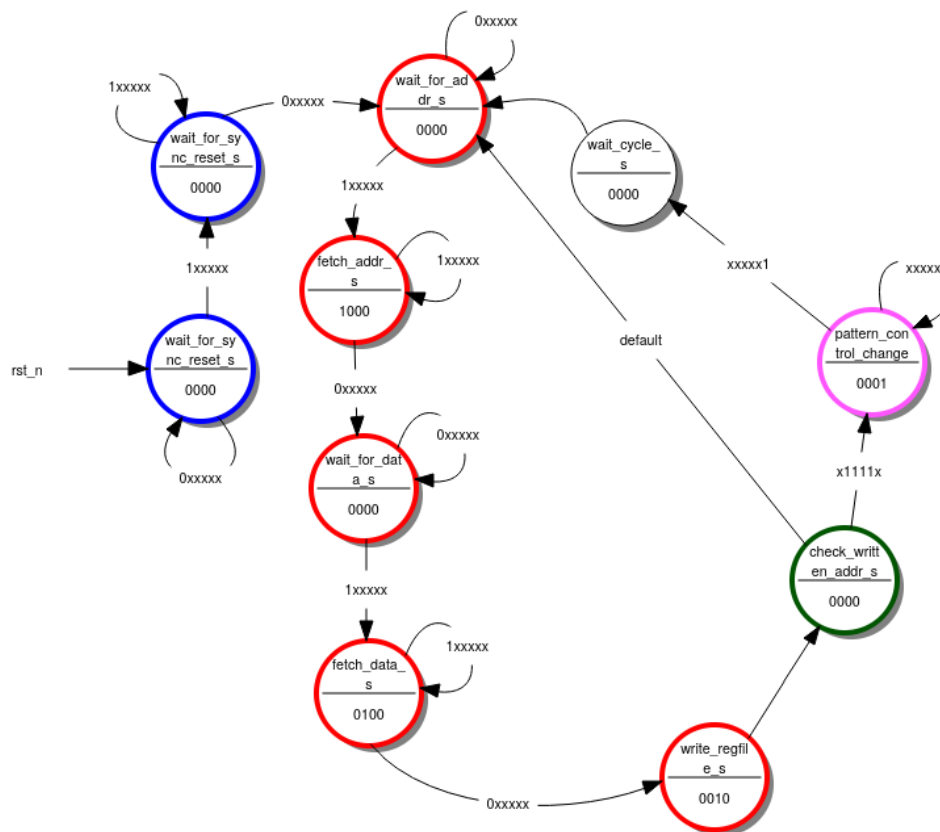


Figure 8: UART Serial Receiver State Machine File - Schematic

Colours on the state machine represent:

- Blue: This is a workaround to handle the rxd_rdy signal causing errors in the operation. More information below.
- Red: This aspect of the state machine manages the receipt of the address and data information.
- Green: These states are to check if there is a change in the signal from pattern control. If there is a change, it then goes to the pink state.
- Pink: This single state is responsible for the communication with the Pattern State Machine.

Inputs:	rx_d_rec	addr[3..0]	pm_checked		
State/Output		en_addr_reg	en_data_reg	en_regfile_wr	pm_control_changed
wait_for_addr_s		0	0	0	0
fetch_addr_s		1	0	0	0

wait_for_data_s	0	0	0	0
fetch_data_s	0	1	0	0
write_regfile_s	0	0	1	0
check_written_addr_s	0	0	0	0
pattern_control_changed_s	0	0	0	1
wait_cycle_s	0	0	0	0
wait_for_sync_reset_serialrx_s	0	0	0	0
wait_for_sync_reset_serialrx2_s	0	0	0	0

This is then directly wired to the `serial_receiver_reg.vhd` module. The purpose is this is for the project to work, the register file (`regfile.vhd`) needs to know both the address and the data values simultaneously - meaning that the information must be stored somewhere. This file takes the values in and stores them to registers temporarily and resets every cycle.

5.1.1 Data received after reset

 



Figure 9: Data out valid after reset

The two states at the beginning of the serial receiver state machine are required to work around a problem that the serial rx component creates. After a reset the serial rx component puts out a data valid signal for one cycle. This seems to be a design problem (see `tsg testbench` at the beginning: `DIN_VLD`). Without these states we have the issue that after an reset we would immediately transition to the state were we are waiting for the data. We are skipping the address states. For that reason the first two states are added.

5.2 Pattern generator

Table 4: I/O Table for the Pattern Generator

Name	Type	Direction	Polarity	Description
en_write_pm	std_ulogic	IN	HIGH	
clk_i	std_ulogic	IN	HIGH	
pm_control_i	std_ulogic_vector[2]	IN	HIGH	
addr_cnt_i	std_ulogic_vector[8]	IN	HIGH	
rx_data_i	std_ulogic_vector[8]	IN	HIGH	
pattern_o	std_ulogic_vector[8]	OUT	HIGH	

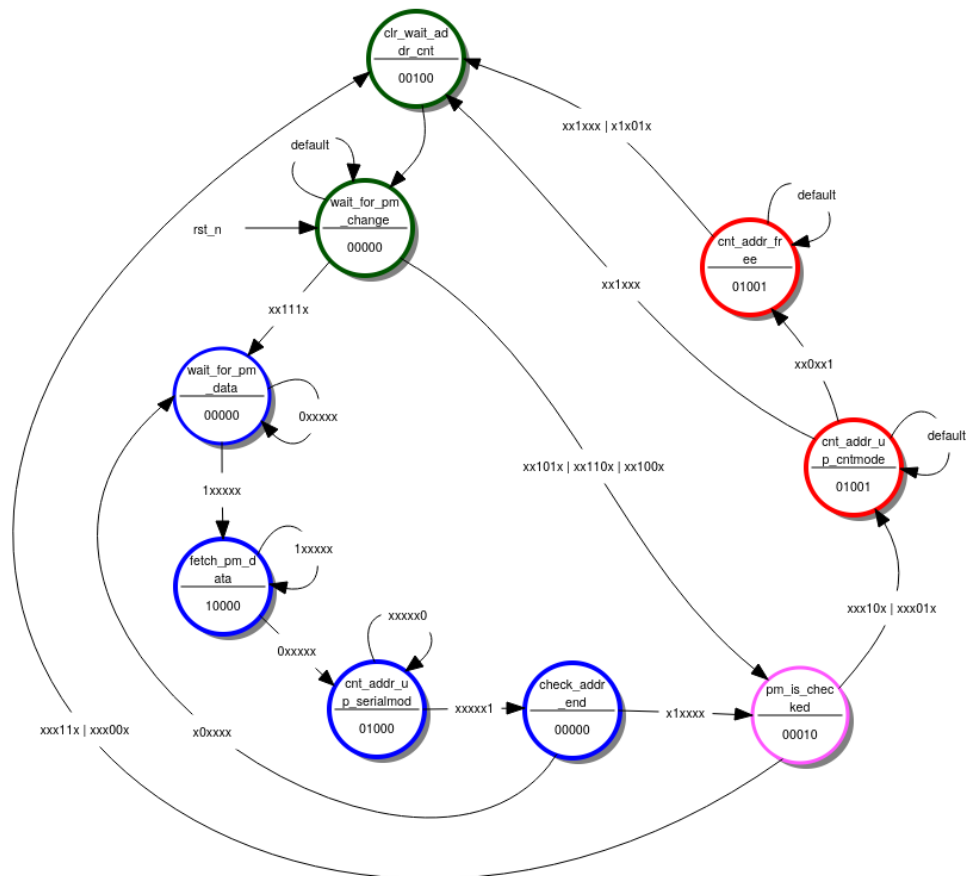**Figure 10:** Pattern Generator State Machine File - Schematic

Colours on the state machine represent:

- Blue: These states deal with the loading of the data and address information.
- Red: This aspect of the state machine manages a workaround related to the tc_pm.
- Green: These states are to manage the initialisation and the reset of the state machine.

- Pink: This single state is responsible for the communication with the Serial Communication State Machine.

```
-- Inputs:   rxd_rec   tc_pm   pm_control_changed   pm_control[1..0]   addr_cnt_enabled

-- State/Output      en_pm en_pm_cnt clr_pm_cnt pm_checked pattern_valid
-- wait_for_pm_change  0     0         0         0         0
-- clr_wait_addr_cnt   0     0         1         0         0
-- wait_for_pm_data    0     0         0         0         0
-- fetch_pm_data       1     0         0         0         0
-- cnt_addr_up_serialmode 0     1         0         0         0
-- check_addr_end       0     0         0         0         0
-- pm_is_checked        0     0         0         1         0
-- cnt_addr_up_cntmode   0     1         0         0         1
-- cnt_addr_free        0     1         0         0         1
```

5.3 Pulse-width modulation

The PWM generator module is connected to one of the instantiations of the freq_control module. The output from the Frequency Control module is input to the generator to assign the total width (and thus the frequency) of the PWM.

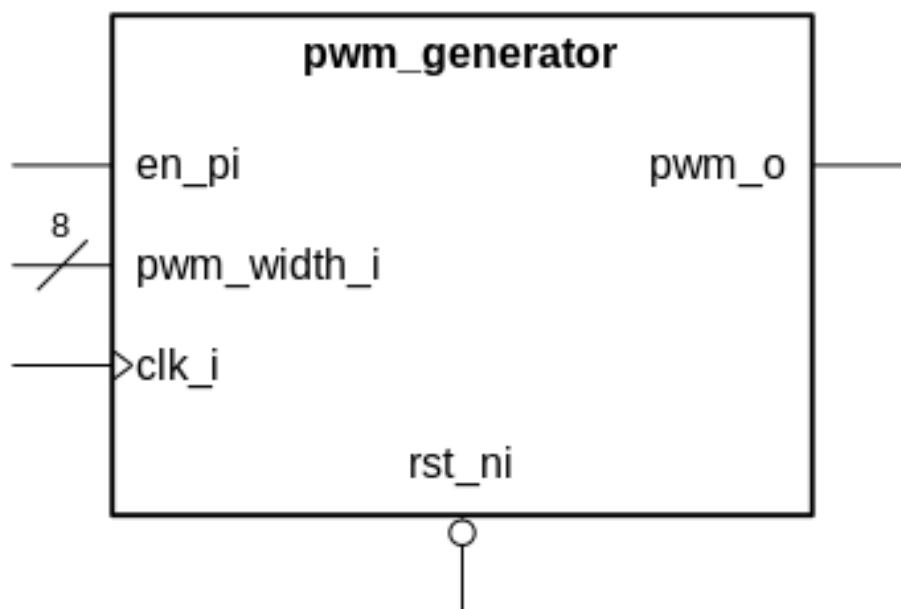


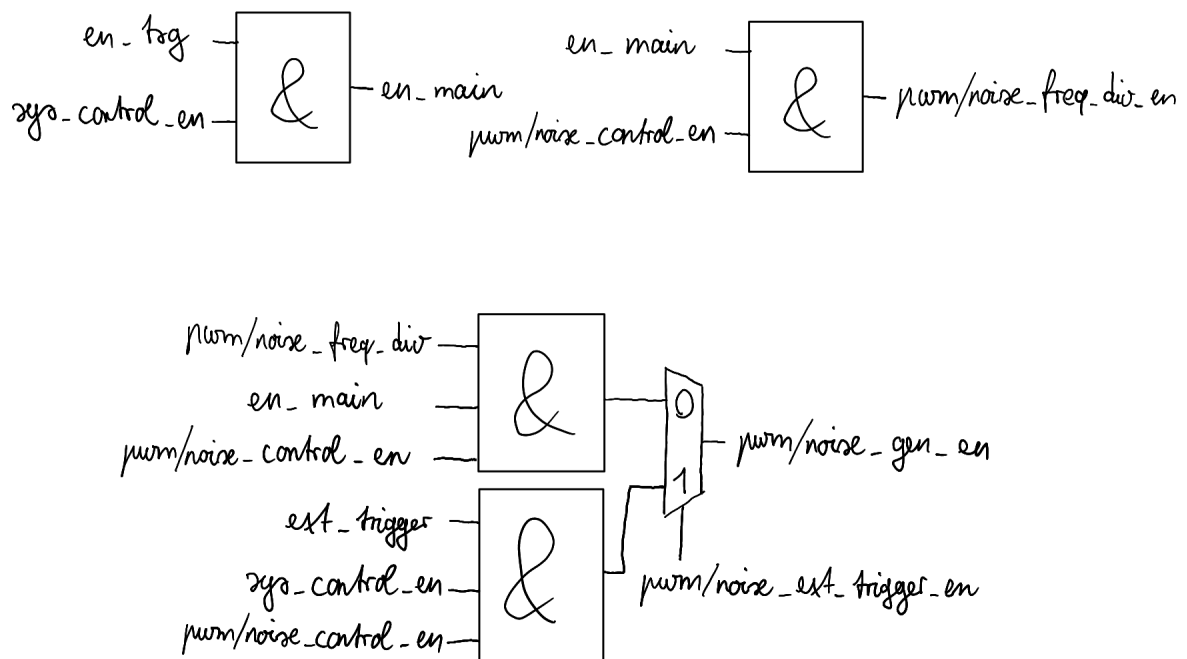
Figure 11: Implemented PWM File - Schematic

Table 5: I/O Table for the PWM Generator

Name	Type	Direction	Polarity	Description
en_pi	std_ulogic	IN	HIGH	
rst_ni	std_ulogic	IN	LOW	
pwm_width_i	std_ulogic_vector[8]	IN	HIGH	
clk_i	std_ulogic	IN	HIGH	
pwm_o	std_ulogic	OUT	HIGH	

5.4 Pseudo-random number generator (LFSR)

5.5 External time base and external triggering design

**Figure 12:** Noise/PWM enable and external trigger design

To get the external time base and external triggering to work correctly multiple AND gates and multiplexer are needed. For the pwm and the noise generator we have the same design. If the noise generator is enabled depends on the following conditions: - the whole system is enabled - pwm/noise generator is enabled - external time base on - frequency divider enabled When the external triggering of the noise/pwm generator is enabled it should only be controlled by external triggering if the system is on and the pwm/noise generator is enabled.

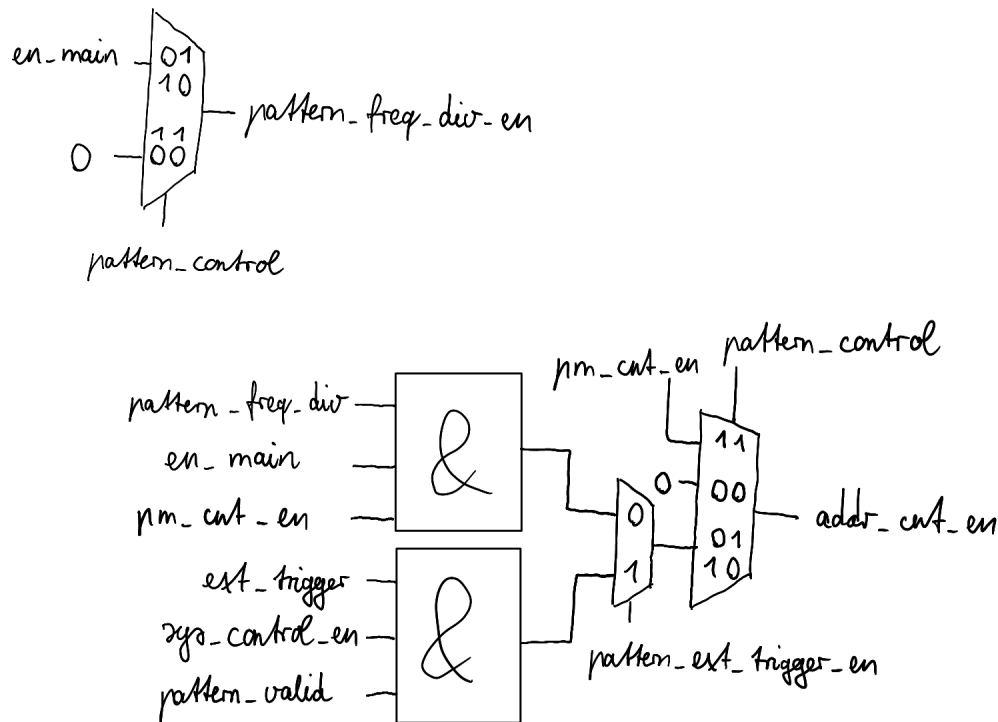


Figure 13: Pattern enable and external trigger design

For the pattern generator a more sophisticated system is needed. We need to differentiate between the four modes of our pattern generator: - 00 stop - 01 single burst - 10 continuous run - 11 load

In stop and load mode we do not care about the external triggering and the external time base. When loading the pattern generator the address upcounter only counts up when the pattern generator state machine gives an signal. Note that the address upcounter decides over the frequency of the pattern output, not the pattern generator (pattern memory) itself. The external trigger, external time base and frequency divider matters when we are in the two run modes. For the external triggering we need the additional signal pattern valid. This signal is provided by the pattern generator state machine and is true when the state machine is in a counting state. This is needed for the single burst mode to stop counting after one counting cycle.

6 Test Results

All of the results were calculated using the formulae mentioned above.

6.1 Noise Generator

Sending serial signals to select the address and the data bit respectively.

 


Figure 14: Oscilloscope readings of the Noise Generator with a period and width of one.

 


Figure 15: Oscilloscope readings of the Noise Generator with a period and width of one. Example of bitwidth

Expected results are found by implementing the formulae in the 4.

Table 6: Results from testing the Noise Generator

Number of Bits	Period Data	Expected Period(μ s)	Actual Period (μ s)
4	1	3	3
4	2	4.5	4.5
7	1	25.4	25.4
7	2	38.1	38.1

6.2 PWM Generator

 


Figure 16: Oscilloscope readings of the PWM Generator with a period and width of one. Example of bitwidth


 


Figure 17: Oscilloscope readings of the PWM Generator with a period and width of 127. Example of bitwidth

Table 7: Results from testing the PWM Generator

Width Data	Period	Expected Period(μ s)	Actual Period (μ s)
1	1	51.2	51.2
1	4	128	128
127	1	51.2	51.2
128	1	51.2	51.2
255	1	51.2	51.2

7 Application Note

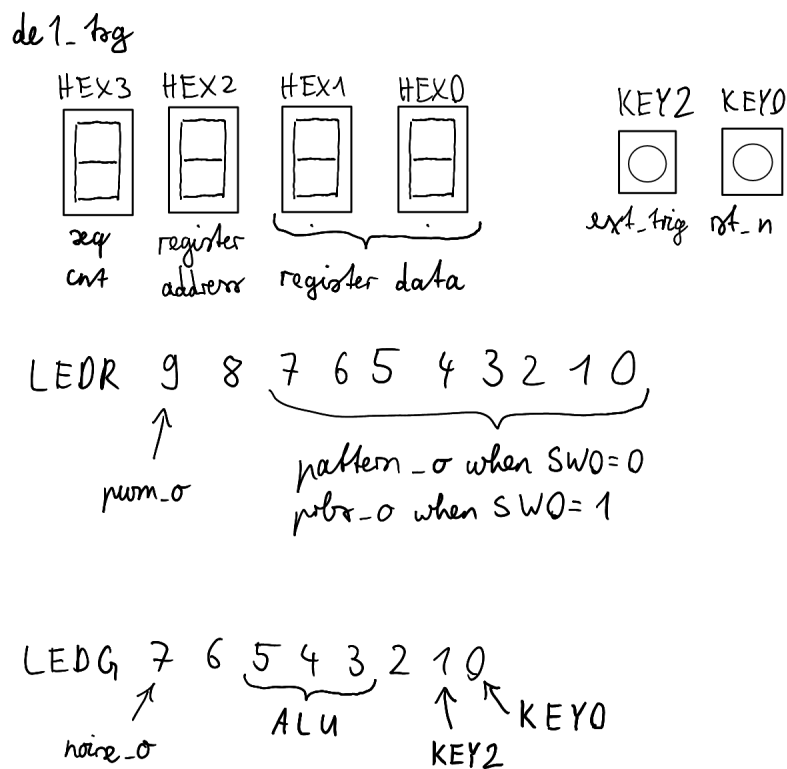

The wiring of the DE1 Board can be seen in the picture above. The test signal generator runs with an 50 MHz clock and a time base of 10 MHz on the enable. An synchroniser is added before the serial input to avoid metavalues because of asynchronous serial communication from the pc. The outputs of the test signal generator were connected to test components ALU and a 101 sequence detector. On the HEX3 display the number of 101 sequences detected is shown. Additionally some outputs are connected to the GPIOs for measurements. For the connections see `de1_tsg_structure.vhd`.

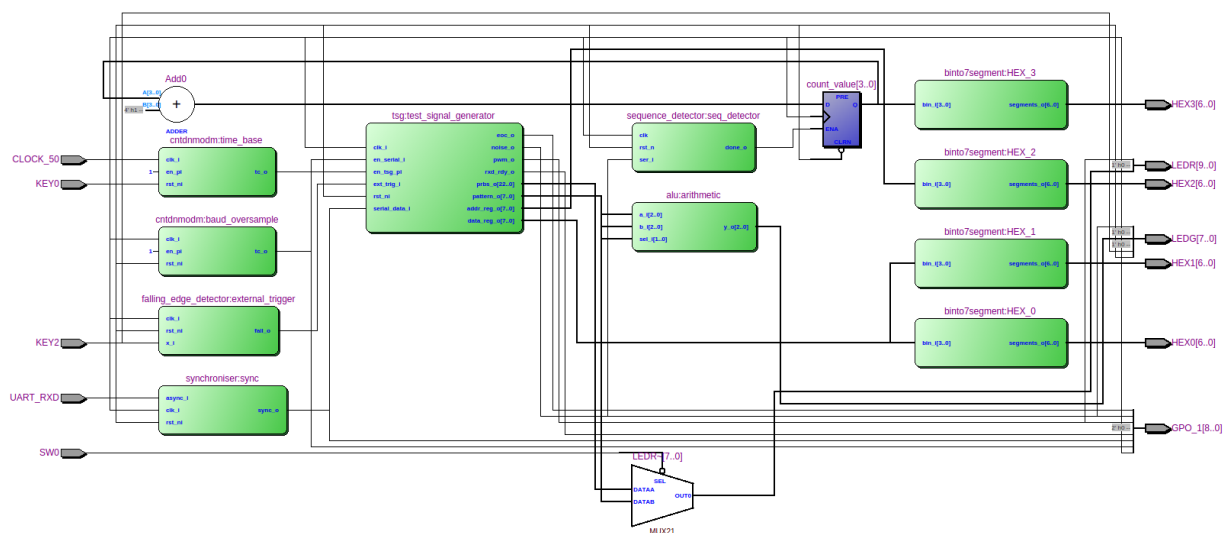


Figure 18: Connected components on DE1 Altera Board

8 Further Improvements

8.1 System control register

In the system control register is a bit included to do an synchronous clear over serial communication. It adds another possibility to reset the states of the synchronous components. At the moment only the asynchronous reset is available. To add this functionality an synchronous reset needs to be added to every component except the memory components (register file, pattern generator) and the address upcounter (has already one).

8.2 Pwm switch off

When the pwm module is switched off either by the system control or the pwm control the counters in the frequency control and pwm generator are kept in their current counting state. This could result in an constant output of a one. To solve this problem it is recommended to put in a switch in the pwm generator that puts out zero when the system control AND pwm control is zero. This approach is already implemented for the noise generator and can be implemented in the same way (see input en_noise_generator_i).

8.3 Testbench tsg and de1_tsg

With the fix in the serial receiver state machine (states at beginning) that solve the issue of data valid signal after reset a different problem occurred. In the real system the fix works but in the simulation this scenario does not happen. We have an immediate one after the reset and not a

zero and then the pulse of the data like in the real system. A possible fix is to add an additional state to the state machine.

 


Figure 19: State Machine Fix

8.4 More test scenarios

The pattern generator was not evaluated on the oscilloscope. It was only tested manually with the external trigger, where it worked correctly (burst mode and continuous run). That means it needs to be tested if the frequency in the automatic mode is correct.

9 References

10 Appendix

10.1 Device Utilization and Performance

10.2 Project Hierarchy

```

.
--- doc
|   +--- datasheet.yaml
|   +--- images
|   +--- makefile
|   +--- presentation.yaml
|   +--- report.yaml
|   +--- tables
|   +--- test_signal_generator_datasheet.md
|   +--- test_signal_generator_presentation.md
|   +--- test_signal_generator_report.md

```

```
|   +-- test_signal_generator_report.pdf
|   +-- uasa_meng_vlsi_template.tex
|   +-- vec.conf
+-- pnr
|   +-- de1_binto7segment
|   +-- de1_cntdnmodm
|   +-- de1_serial_rx
|   +-- de1_tsg
|   +-- makefile
+-- README.md
+-- scripts
|   +-- create_quartus_project_settings.tcl
|   +-- de1_pin_assignments_minimumio.tcl
|   +-- modelsim.ini
|   +-- quartus_project_flow.tcl
|   +-- test_variables.py
|   +-- write_to_ttyUSBx.py
+-- sim
|   +-- binto7segment
|   +-- cntdnmodm
|   +-- cntup_addr
|   +-- de1_tsg
|   +-- makefile
|   +-- noise_generator
|   +-- pattern_generator
|   +-- pwm_generator
|   +-- serial_rx
|   +-- tsg
+-- src
    +-- 101SequenceQfsm.fsm
    +-- a_falling_edge_detector_rtl.vhd
    +-- alu.vhd
    +-- alu.vhd.bak
    +-- a_tsg_structure.vhd
    +-- a_tsg_structure.vhd.bak
    +-- binto7segment_truthtable.vhd
    +-- cntdnmodm_rtl.vhd
    +-- cntup_addr.vhd
    +-- cntup_addr.vhd.bak
    +-- config_noise_generator.vhd
    +-- config_noise_generator.vhd.bak
    +-- de1_serial_rx_structure.vhd
    +-- de1_tsg_structure.vhd
    +-- de1_tsg_structure.vhd.bak
    +-- e_falling_edge_detector.vhd
    +-- e_tsg.vhd
    +-- freq_control.vhd
    +-- noise_generator.vhd
    +-- noise_generator.vhd.bak
    +-- pattern_generator_fsm.vhd
    +-- pattern_generator_qfsm.fsm
    +-- pattern_generator.vhd
    +-- pwm_generator.vhd
    +-- regfile_rtl.vhd
    +-- regfile_rtl.vhd.bak
    +-- sequence_detector.vhd
    +-- serial_receiver_fsm.vhd
    +-- serial_receiver_qfsm.fsm
    +-- serial_receiver_reg.vhd
    +-- serial_receiver_reg.vhd.bak
    +-- serial_rx.vhd
    +-- serial_tx.vhd
```

```
+++ sp_ssram_rtl.vhd
+++ synchroniser.vhd
+++ synchroniser.vhd.bak
+++ t_cntup_addr.vhd
+++ t_de1_tsg.vhd
+++ t_noise_generator.vhd
+++ t_pattern_generator.vhd
+++ t_pwm_generator.vhd
+++ t_serial_receiver_fsm.vhd
+++ t_serial_rx.vhd
+++ t_tsg.vhd
+++ uart_clk_div.vhd
+++ uart_parity.vhd
```

10.3 Module Hierarchy

tsg testbench:

```
t_tsg(tbench)
  e_tsg.vhd
  a_tsg_structure.vhd
  uart_clk_div.vhd
  uart_parity.vhd
  serial_rx.vhd
  serial_tx.vhd
  serial_receiver_reg.vhd
  serial_receiver_fsm.vhd
  regfile_rtl.vhd
  freq_control.vhd
  pwm_generator.vhd
  noise_generator.vhd
  config_noise_generator.vhd
  pattern_generator.vhd
  pattern_generator_fsm.vhd
  cntup_addr.vhd
  sp_ssram_rtl.vhd
  cntdnmodm_rtl.vhd
```

de1_tsg:

```
de1_tsg(structure)
  binto7segment_truthtable.vhd
  cntdnmodm_rtl.vhd
  synchroniser.vhd
  a_falling_edge_detector_rtl.vhd
  e_falling_edge_detector.vhd
  sequence_detector.vhd
  alu.vhd
  de1_tsg_structure.vhd
```

All files in tsg testbench also needed in de1_tsg.

10.4 Code

Register File:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY regfile IS
  GENERIC(
    ADDR_WIDTH : integer := 4;
    DATA_WIDTH : integer := 8
  );
  PORT(
    clk_i          : IN std_ulogic; -- system clock in
    wr_en_i        : IN std_ulogic; -- write enable in
    w_addr_i       : IN std_ulogic_vector (ADDR_WIDTH-1 DOWNT0 0);
    r_addr_i       : IN std_ulogic_vector (ADDR_WIDTH-1 DOWNT0 0);
    w_data_i       : IN std_ulogic_vector (DATA_WIDTH-1 DOWNT0 0);
    -- system_status_reg_i : IN std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    system_control_o : OUT std_ulogic_vector(1 DOWNT0 0);
    pwm_pulse_width_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    pwm_period_o    : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    pwm_control_o   : OUT std_ulogic_vector(1 DOWNT0 0);
    noise_length_o  : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    noise_period_o  : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    noise_control_o : OUT std_ulogic_vector(1 DOWNT0 0);
    pattern_mem_depth_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0); -- pattern_length
    -- pattern_data_o      : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    pattern_period_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    pattern_control_o : OUT std_ulogic_vector(2 DOWNT0 0);
    r_data_o        : OUT std_ulogic_vector (DATA_WIDTH-1 DOWNT0 0)
  );
END regfile;

ARCHITECTURE rtl OF regfile IS
  TYPE array_2d_t IS ARRAY (0 TO 2**ADDR_WIDTH-1) OF
    std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
  SIGNAL array_reg : array_2d_t;
BEGIN
  PROCESS(clk_i)
  BEGIN
    IF rising_edge(clk_i) THEN
      IF wr_en_i = '1' THEN
        array_reg(to_integer(unsigned(w_addr_i))) <= w_data_i;
      END IF;
    END IF;
  END PROCESS;

  system_control_o <= array_reg(1)(1 DOWNT0 0);
  pwm_pulse_width_o <= array_reg(4);
  pwm_period_o <= array_reg(5);
  pwm_control_o <= array_reg(6)(1 DOWNT0 0);
  noise_length_o <= array_reg(8);
  noise_period_o <= array_reg(9);
  noise_control_o <= array_reg(11)(1 DOWNT0 0);
  pattern_mem_depth_o <= array_reg(12);
  -- pattern_data_o <= array_reg(13);
  pattern_period_o <= array_reg(14);
  pattern_control_o <= array_reg(15)(2 DOWNT0 0);

```

```
-- read port
r_data_o <= array_reg(to_integer(unsigned(r_addr_i)));
END rtl;
```

ALU Test Device

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY alu IS
  PORT (a_i : IN std_ulogic_vector(2 DOWNTO 0); -- data input a
        b_i : IN std_ulogic_vector(2 DOWNTO 0); -- data input b
        sel_i : IN std_ulogic_vector(1 DOWNTO 0); -- select which input is connected to y

        y_o : OUT std_ulogic_vector(2 DOWNTO 0) -- data output y
        );
END ENTITY alu;

ARCHITECTURE rtl OF alu IS

  SIGNAL y_out : unsigned(2 DOWNTO 0); -- set as unsigned so it can be written
                                         -- to after the conversion

BEGIN

  WITH sel_i SELECT y_out <= -- uses select value to determine the operation below
    (unsigned(a_i) + unsigned(b_i)) WHEN "00", -- converted to unsigned to make logical arithmetic
    ↪ possible
    (unsigned(a_i) - unsigned(b_i)) WHEN "01", -- WHEN statement
    (unsigned(a_i and b_i)) WHEN "10", -- possible issues with data type
    (unsigned(a_i or b_i)) WHEN "11", -- possible issues with data type
    (OTHERS => '0') WHEN others;

  y_o <= std_ulogic_vector(y_out); -- converting the output to std_ulogic_vect
                                   -- to output

END rtl;
```

Noise Generator Configuration

- Description: Allows for switching between a number of different bits for the lfsr. Choose the
 ↪ bitwidth and where the feedbacks are for the xor.

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

-- https://www.itu.int/rec/T-REC-O.150-199605-I/en
ENTITY config_noise_generator IS
  GENERIC (
    num_of_bits : positive := 4; -- just a default value
    tap_high : positive := 4; -- xor connection 1
    tap_low : positive := 3; -- xor connection 2
  );
  PORT (
    en_pi : IN std_ulogic;
    clk_i : IN std_ulogic;
```

```

    rst_ni  : IN  std_ulogic;
    prbs_o   : OUT std_ulogic_vector(num_of_bits - 1 DOWNT0 0); --
    noise_o  : OUT std_ulogic;
    eoc_o    : OUT std_ulogic
  );
END ENTITY config_noise_generator;

ARCHITECTURE rtl OF config_noise_generator IS

    SIGNAL q      : std_ulogic_vector(num_of_bits - 1 DOWNT0 0); -- current state
    SIGNAL d      : std_ulogic_vector(num_of_bits - 1 DOWNT0 0); -- next state
    CONSTANT init : std_ulogic_vector(num_of_bits - 1 DOWNT0 0) := (0 => '1', OTHERS => '0');

BEGIN
    -- lfsr with xor feedback; 0 lines are on the right of the shift register, highest on the left
    -- next state logic
    d(num_of_bits - 2 DOWNT0 0) <= q(num_of_bits - 1 DOWNT0 1);
    d(num_of_bits - 1)          <= q(num_of_bits - tap_low) XOR q(num_of_bits - tap_high); --
    ↪ feedback

    -- outputs
    noise_o <= q(0);
    prbs_o  <= q;
    eoc_o   <= '1' WHEN q = init ELSE '0'; -- end/start of cycle

    state_register : q <= init WHEN rst_ni = '0' ELSE
                      d WHEN rising_edge(clk_i) AND en_pi = '1';

END ARCHITECTURE rtl;

```

Frequency Controller

```

-----
-- Module      : noise_freq_control
-----

-- Author      : Leo Hillinger, Ruairi Dillon & David Cunningham
-- Company     : University of Applied Sciences Augsburg
-----

-- Description: This module is to act like the frequency controller for the
-- three generators in the project.
-----

-- Revisions   : see end of file
-----

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY freq_control IS

    PORT (clk_i      : IN  std_ulogic;
          rst_ni     : IN  std_ulogic;
          en_pi      : IN  std_ulogic;
          count_o    : OUT std_ulogic_vector(7 DOWNT0 0);
          freq_o     : OUT std_ulogic;
          period_i   : IN  std_ulogic_vector(7 DOWNT0 0)
    );
END freq_control;

ARCHITECTURE rtl OF freq_control IS

```



```

    SIGNAL next_state, current_state : unsigned(7 DOWNT0 0);

    CONSTANT zero : unsigned(current_state'length-1 DOWNT0 0) := (OTHERS => '0'); -- means vector
    ↪ with only zeros

-- "The constant is like a variable object type, the value of which cannot
-- be changed. A signal object can be of different types; we saw before, for
-- example, that a signal object can be of type std logic or of other types
-- like integer, custom types, etc. The same applies for variable objects."

BEGIN

    -- includes decremter and modulo logic
    next_state_logic : next_state <= unsigned(period_i) WHEN current_state = 0 ELSE
                        current_state - 1;

    state_register : current_state <= zero WHEN rst_ni = '0' ELSE
                    next_state WHEN rising_edge(clk_i) AND (en_pi = '1');

    counter_output : count_o <= std_ulogic_vector(current_state);

    terminal_count : freq_o <= '1' WHEN current_state = 0 ELSE '0';

END rtl;

-----
-- Revisions:
-- -----
-- $Id:$
-----

```

Pattern Generator

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
-- use IEEE.numeric_std.all;

ENTITY pattern_generator IS
    PORT (
        en_write_pm : IN std_ulogic;
        clk_i       : IN std_ulogic;
        pm_control_i : IN std_ulogic_vector(1 downto 0); -- only the control bits are needed (not bit
    ↪ 2)
        addr_cnt_i   : IN std_ulogic_vector(7 downto 0);
        rxd_data_i   : IN std_ulogic_vector(7 DOWNT0 0); -- uart data
        pattern_o    : OUT std_ulogic_vector(7 DOWNT0 0)
    );
END ENTITY pattern_generator;

ARCHITECTURE structure OF pattern_generator IS

    COMPONENT sp_ssram IS
        GENERIC (
            addr_width : positive; -- a number > 0
            data_width  : positive);
        PORT (

```

```

    clk_i  : IN  std_ulogic;
    we_i   : IN  std_ulogic;
    addr_i : IN  std_ulogic_vector;
    d_i    : IN  std_ulogic_vector;
    q_o    : OUT std_ulogic_vector);
END COMPONENT sp_ssram;

CONSTANT addr_width : natural := 8;
CONSTANT data_width : natural := 8;

SIGNAL pm_out      : std_ulogic_vector(data_width - 1 DOWNT0 0);
SIGNAL pattern_temp : std_ulogic_vector(data_width - 1 DOWNT0 0);

BEGIN

    pattern_memory : sp_ssram
        GENERIC MAP (
            addr_width => addr_width,
            data_width => data_width)
        PORT MAP (
            clk_i  => clk_i,
            we_i   => en_write_pm,
            addr_i => addr_cnt_i,
            d_i    => rxd_data_i,
            q_o    => pm_out);

    WITH pm_control_i SELECT
        pattern_temp <= (OTHERS => '0') WHEN "00", -- stop
        pm_out       WHEN "01", -- single burst
        pm_out       WHEN "10", -- continous burst
        (OTHERS      => '0') WHEN "11", -- load
        (OTHERS      => '0') WHEN OTHERS;

    output_register : pattern_o <= pattern_temp WHEN rising_edge(clk_i);

END ARCHITECTURE structure;

```

PWM Generator

```

-- Leo Hillinger and Ruairi Dillon 28/05/2021

-- Description: Intakes an enable, system clock, reset and a value to set the
-- width (i.e. frequency). The width is the size of the whole signal (high and
-- low). It then outputs a signal which forms the pwm of the set size.

LIBRARY ieee;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY pwm_generator IS

    PORT(
        en_pi      : IN  std_ulogic;           -- enable pin
        rst_ni     : IN  std_ulogic;           -- reset
        pwm_width_i : IN  std_ulogic_vector(7 DOWNT0 0); -- size of the pwm total signal
        clk_i      : IN  std_ulogic;           -- clock in
        pwm_o      : OUT std_ulogic;           -- output signal from module
    );

```

```

END pwm_generator;

ARCHITECTURE rtl OF pwm_generator IS

    SIGNAL next_state, current_state : unsigned(7 DOWNTO 0); -- states

    SIGNAL pwm_temp : std_ulogic; -- temporary place holder for state logic below

BEGIN
    -- "just a down counter"
    -- next state is "11111111" current state is equal zero. this is then used to
    -- be compared to the requested width from freq_control
    -- the width is the size of the whole signal (high and
    -- low). It then outputs a signal which forms the pwm of the set size.
    --current state will be equal to "00000000" when the reset is pressed, or
    --else it will be equal to the next_state value when enabled.

    state_register : current_state <= (others => '0') WHEN rst_ni = '0' ELSE
                                next_state WHEN rising_edge(clk_i) AND (en_pi = '1');

    -- sets the output value to pwm temp when current state is lesser than the
    -- width, thus making the desired pulse width proportional to the 8 bits (255).
    counter_output : pwm_temp <= '1' WHEN current_state < unsigned(pwm_width_i) ELSE
                                '0';

    -- setting the output to a registered for integration with other modules
    output_register : pwm_o <= '0' WHEN rst_ni = '0' ELSE
                                pwm_temp WHEN rising_edge(clk_i);

END rtl;

```

Register File

```

-----
-- Module      : regfile
-----
-- Author       : <johann.ferber@hs-augsburg.de>
-- Company      : University of Applied Sciences Augsburg
-- Copyright (c) 2021 <johann.ferber@hs-augsburg.de>
-----
-- Description: Register File - parameterisable by data width and address width
-----
-- Revisions    : see end of file
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY regfile IS
    GENERIC(
        ADDR_WIDTH : integer := 4;
        DATA_WIDTH : integer := 8
    );
    PORT(
        clk_i          : IN std_ulogic;
        wr_en_i        : IN std_ulogic;
        w_addr_i       : IN std_ulogic_vector (ADDR_WIDTH-1 DOWNTO 0);

```

```

r_addr_i      : IN  std_ulogic_vector (ADDR_WIDTH-1 DOWNT0 0);
w_data_i      : IN  std_ulogic_vector (DATA_WIDTH-1 DOWNT0 0);
-- system_status_reg_i : IN  std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
system_control_o : OUT std_ulogic_vector(1 DOWNT0 0);
pwm_pulse_width_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pwm_period_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pwm_control_o : OUT std_ulogic_vector(1 DOWNT0 0);
noise_length_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
noise_period_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
noise_control_o : OUT std_ulogic_vector(1 DOWNT0 0);
pattern_mem_depth_o

: OUT std_ulogic_vector(2 DOWNT0 0);
r_data_o      : OUT std_ulogic_vector (DATA_WIDTH-1 DOWNT0 0)
);
END regfile;

ARCHITECTURE rtl OF regfile IS
    TYPE array_2d_t IS ARRAY (0 TO 2**ADDR_WIDTH-1) OF -- array = (2^address width)-1
        std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    SIGNAL array_reg : array_2d_t;
BEGIN
    PROCESS(clk_i)
    BEGIN
        IF rising_edge(clk_i) THEN
            IF wr_en_i = '1' THEN -- if the write is enabled
                array_reg(to_integer(unsigned(w_addr_i))) <= w_data_i; -- then it takes address, turns
-- to integer for use as index of array,
                END IF; -- then it writes data to the
-- array at the index of address
            END IF;
        END PROCESS;

        system_control_o <= array_reg(1)(1 DOWNT0 0); -- because system control is two bits
        pwm_pulse_width_o <= array_reg(4);
        pwm_period_o <= array_reg(5);
        pwm_control_o <= array_reg(6)(1 DOWNT0 0);
        noise_length_o <= array_reg(8);
        noise_period_o <= array_reg(9);
        noise_control_o <= array_reg(11)(1 DOWNT0 0);
        pattern_mem_depth_o <= array_reg(12);
        pattern_period_o <= array_reg(14);
        pattern_control_o <= array_reg(15)(2 DOWNT0 0); -- because pattern control has three bits to
-- write to

-- read port
        r_data_o <= array_reg(to_integer(unsigned(r_addr_i)));
    END rtl;

```

Serial Receiver Register File

```

-- Description: takes information on the address and the data externally (serial reciever),
-- to then store to registers.
-- In the scope of the project, this then gets sent to the register file to be
-- processed from there.

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

```

```

entity serial_receiver_reg is
    port (
        rst_ni : in std_ulogic;
        clk_i   : in std_ulogic;
        en_addr_reg_i : in std_ulogic;
        en_data_reg_i : in std_ulogic;
        rxd_data_i : in std_ulogic_vector(7 downto 0); -- uart data
        regfile_addr_o : out std_ulogic_vector(3 downto 0);
        regfile_data_o : out std_ulogic_vector(7 downto 0)
    );
end entity serial_receiver_reg;

architecture rtl of serial_receiver_reg is

begin

    addr_register : regfile_addr_o <= (others => '0') WHEN rst_ni = '0' ELSE
        std_ulogic_vector(resize(unsigned(rxd_data_i), 4)) WHEN rising_edge(clk_i) AND (en_addr_reg_i
        ↪ = '1'); -- slices the four most significant bits off of the address

    data_register : regfile_data_o <= (others => '0') WHEN rst_ni = '0' ELSE
        rxd_data_i WHEN rising_edge(clk_i) AND (en_data_reg_i = '1');

end architecture rtl;

```

```

-- Description: Synchroniser functions by taking in asynchronous data, then it
-- goes through two flip flops, the Q of the first flip flop is connected to
-- the D of the other flipflop. The output of this is a signal synchronous with
-- the clock input.
-- Clocks and resets are common for both flipflops.

```

```

-- ASK LEO HOW THE FLIP FLOPS ARE ACTUALLY INSTANTIATED

```

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

```

```

entity synchroniser is
    port (
        clk_i : in std_ulogic; -- common clock
        rst_ni : in std_ulogic; -- common reset
        async_i : in std_ulogic; -- the input, asynchronous data
        sync_o : out std_ulogic -- the data output
    );
end entity synchroniser;

```

```

architecture rtl of synchroniser is

```

```

    signal ff1_i, ff2_i : std_ulogic; -- flip flop one and flip flop two's input
    signal ff1_o, ff2_o : std_ulogic; -- flip flop one and flip flop two's output

```

```

BEGIN

```

```

--Sensitivity lists are parameters to a process which lists all the signals that the process is
↪ sensitive to. If any
--of the signals change, the process will wake up, and the code within it is executed. We've
↪ already learned to
--use the wait on and wait until statements for waking up a process when a signal changes.

```

```
sync: process(clk_i, rst_ni) -- sensitivity list
begin
    if rst_ni = '0' then
        ff1_o <= '0';
        ff2_o <= '0';
    elsif rising_edge(clk_i) then
        ff1_o <= ff1_i; -- connects the input of the first flip flop to the
                        -- output of the first
        ff2_o <= ff2_i;
    end if;
end process sync;

ff1_i <= async_i; -- setting the input as the input of flip flop 1
ff2_i <= ff1_o; -- flip flop two's input being wired to

sync_o <= ff2_o; -- then the overall system's output

end architecture rtl;
```