



**Hochschule
Augsburg** University of
Applied Sciences

Test Signal Generator

VLSI-Design Module - Report

L Hillinger, D Cunnigham, R Dillon

SS2021

Contents

1	Introduction	6
2	Functional Description	6
2.1	UART serial communication	6
2.2	Digital pattern generator	7
2.3	Pulse-width modulation	7
2.4	Pseudo-random number generator (LFSR)	8
3	General Description	8
3.1	Mnemonics python script	12
3.2	PWM Component	12
3.3	Noise Component	12
3.4	Pattern Component	13
4	Design Description	13
4.1	UART serial receiver	13
4.1.1	Data received after reset	16
4.2	Pattern generator	16
4.3	Pulse-width modulation	18
4.4	Pseudo-random number generator (LFSR)	19
4.5	External time base and external triggering design	20
5	Test Results	22
5.1	Noise Generator	22
5.2	PWM Generator	24
5.3	Pattern Generator	25
6	Application Note	26
7	Further Improvements	27
7.1	System Control Register	27
7.2	PWM Switch Off	27
7.3	Testbench tsg and de1_tsg	27
7.4	More Test Scenarios	28
8	References	28
9	Appendix	28
9.1	Device Utilization and Performance	28
9.2	Project Hierarchy	29
9.3	Module Hierarchy	31

9.4	Code	32
-----	----------------	----

List of Tables

1	Test Signal Generator - Description of I/O Signals	9
2	I/O Table for the Serial Receiver	14
4	I/O Table for the Pattern Generator	17
5	I/O Table for the PWM Generator	18
6	Results from testing the Noise Generator	23
7	Results from testing the PWM Generator	25

List of Figures

1	UART Example- Schematic [1]	6
2	Expected output of the pattern generator	7
3	PWM Example - Schematic [3]	7
4	LFSR Exampled - Schematic [2]	8
5	Test Signal Generator Schematic Symbol	8
6	Test Signal Generator Breakup Drawing	10
7	Pwm implementation	12
8	Implemented Serial Receiver File - Schematic	14
9	UART Serial Receiver State Machine File - Schematic	15
10	Data out valid after reset	16
11	Pattern Generator State Machine File - Schematic	17
12	Implemented PWM File - Schematic	18
13	Implemented LFSR	19
14	Noise/PWM enable and external trigger design	20
15	Pattern enable and external trigger design	21
16	Oscilloscope readings of the Noise Generator with a period and width of one.	22
17	Oscilloscope readings of the Noise Generator with a period and width of one. Example of bitwidth	23
18	Oscilloscope readings of the PWM Generator with a period and width of one. Example of bitwidth	24
19	Oscilloscope readings of the PWM Generator with a period and width of 127. Example of bitwidth	25
20	Connected components on DE1 Altera Board	27
21	State Machine Fix	28

1 Introduction

Digital test signal generators (TSG) are a type of external measurement equipment that are available from several different vendors. These pieces of equipment produce a range of electrical stimuli signals that can be used to check the operation of other electrical devices. The goal of this module is to produce an on-chip version of this system with the following essential features included in the architecture and design: - Serially configurable - Single pulse with variable duty cycle and frequency (PWM) - Digital noise based on pseudo random binary sequences of different length - Configurable data sequences at selectable speed (pattern generator) - Internal/External triggering of generators - External Time Base for selectable base frequency

2 Functional Description

2.1 UART serial communication

UART communication is a common form of data communication between electronic devices. It communicated the data serially in the form of digital signals.

 


Figure 1: UART Example- Schematic [1]

UART communication has some characteristics that need to be considered for implementation. The signal begins with a start bit (in the form of a low signal), the next in the sequence comes the data bits, the number of data bits is configurable and is dependant on the parameterisation of the serial modules. After the data sequence is complete, UART protocol then instructs you to send a stop bit, which is a high signal.

Due to the asynchronous nature of this communication method it requires a baud rate for the transfer to be configured. It is asynchronous because the sending and receiving devices work with different clock cycles. The baud rate (speed of communication) has to be the same on both devices. Typical baud rates are 9600, 14400 and 19200.

2.2 Digital pattern generator

 


Figure 2: Expected output of the pattern generator

Digital Pattern Generators are a common way of creating signal for testing. The Pattern Generator allows the user to output a configurable pattern. The pattern can take various shapes, including standard pulses or outputting larger bit patterns depending on the system configuration.

2.3 Pulse-width modulation

Pulse Width Modulation (PWM) is a type of digital signal that has many uses for real world applications. It is a way in which you can digitally control some analog devices.

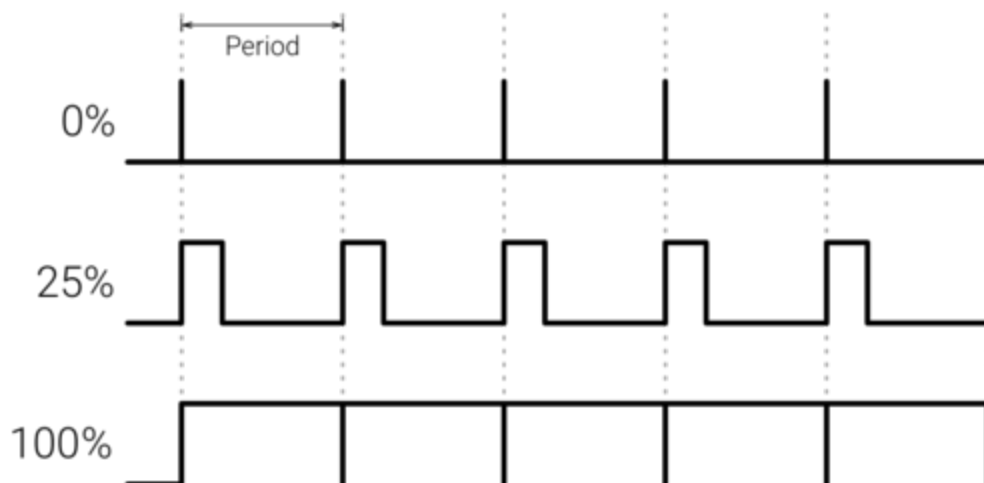


Figure 3: PWM Example - Schematic [3]

PWM functions by switching between low and high signals to the requested amounts by the user. For each cycle, the signal will be high for the requested percentage. This is known as the Duty Cycle.

$$Period = T_{on} + T_{off}$$

$$DutyCycle = \frac{T_{on}}{T_{on} + T_{off}} \times 100$$

A typical use case for PWM is dimming of a led with change of the duty cycle.

2.4 Pseudo-random number generator (LFSR)

Linear Feedback Shift Registers is a configuration of registers used in conjunction with an XOR gate to create a function dependant on it's previous state.

 


Figure 4: LFSR Exampled - Schematic [2]

By continually shifting to the right and going through the XOR gate, it generates a series of pseudo random numbers.

The number of cycles until the pseudo random number generator repeats himself is:

$$\text{number of cycles} = 2^n - 1$$

With n as number of bits. The polynomial on which the LFSR is based on decides on the number of bits and the feedback connection of the XOR gate.

3 General Description

 


Figure 5: Test Signal Generator Schematic Symbol

Table 1: Test Signal Generator - Description of I/O Signals

Name	Type	Direction	Polarity	Description
clk_i	std_ulogic	IN	HIGH	clock
rst_ni	std_ulogic	IN	LOW	asynchronous reset
en_tsg_pi	std_ulogic	IN	HIGH	external time base
en_serial_i	std_ulogic	IN	HIGH	oversample of 16, baudrate 9600
serial_data_i	std_ulogic	IN	HIGH	serial data, baudrate 9600
rxd_rdy_o	std_ulogic	OUT	HIGH	serial data ready to read
ext_trig_i	std_ulogic	IN	HIGH	external trigger
pwm_o	std_ulogic	OUT	HIGH	pwm signal
noise_o	std_ulogic	OUT	HIGH	1 bit pseudo random noise
prbs_o	std_ulogic_vector[23]	OUT	HIGH	pseudo random noise up to 23 bit
eoc_o	std_ulogic	OUT	HIGH	end of cycle of pseudo random noise
pattern_o	std_ulogic_vector[8]	OUT	HIGH	pattern output
pattern_valid_o	std_ulogic	OUT	HIGH	pattern valid
tc_pm_count_o	std_ulogic	OUT	HIGH	end of cycle pm upcounter
regfile_o	std_ulogic_vector[8]	OUT	HIGH	data input register file
addr_reg_o	std_ulogic_vector[8]	OUT	HIGH	address output serial register
data_reg_o	std_ulogic_vector[8]	OUT	HIGH	data output of serial registers

The test signal generator with its multiple I/Os can be broken down into 4 distinctive parts:

- serial data handling
- pulse width modulation generator
- pattern generator
- random noise generator

tsg

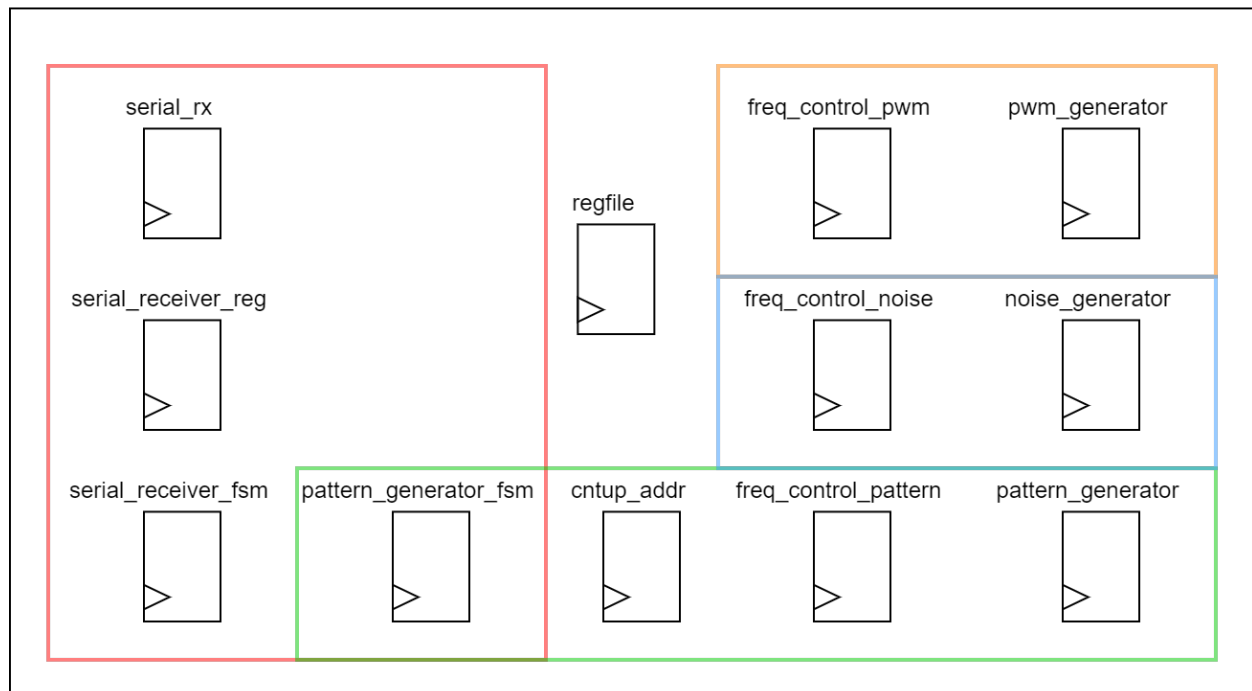


Figure 6: Test Signal Generator Breakup Drawing

In the picture above you can recognize that the register file is the central part of the design. The register file receives data from the serial communication and writes them into its memory. Depending on the values in the memory the output components are controlled.

The register file has the following memory view.

		Bit7	..					0	
Address	Name	7	6	5	4	3	2	1	0
0x00									
0x01	system control							x	x
0x02									
0x03									
0x04	pwm pulse width	x	x	x	x	x	x	x	x
0x05	pwm period	x	x	x	x	x	x	x	x
0x06	pwm control							x	x
0x07									
0x08	noise prbsg length	x	x	x	x	x	x	x	x
0x09	noise period	x	x	x	x	x	x	x	x
0x0A									
0x0B	noise control							x	x
0x0C	pattern length	x	x	x	x	x	x	x	x
0x0D									
0x0E	pattern period	x	x	x	x	x	x	x	x
0x0F	pattern control							x	x

The meaning of the control parts of the registers is explained in the following.

system control

Bit 0 Meaning

- 0 system disable
- 1 system enable

Bit 1 Meaning

- 1 system clear [synchronous clear](not currently implemented see improvements!)

pwm control

Bit 0 Meaning

- 0 pwm off
- 1 pwm on

Bit 1 Meaning

- 0 internal trigger
- 1 external trigger

noise prbsg length

Bit 7 6 5 4 3 2 1 0 Meaning

- 0 0 0 4-bit
- 0 0 1 7-bit 8B/10B-encoded pattern
- 0 1 0 15-bit ITU-T 0.150
- 0 1 1 17-bit OIF-CEI-P-02.0
- 1 0 0 20-bit ITU-T 0.150
- 1 0 1 23-bit ITU-T 0.150

noise control

Bit 0 Meaning

- 0 noise off
- 1 noise on

Bit 1 Meaning

- 0 internal trigger
- 1 external trigger

pattern control

Bit 1 0 Meaning

- 0 0 stop
- 0 1 single burst
- 1 0 continuous run
- 1 1 load data

Bit 2 Meaning

- 0 internal trigger
- 1 external trigger

Now the control part of the register will be explained in further detail. The system has an general enable “system control” which must be switched on to switch on all individual components (noise, pattern, pwm). All components allow for external triggering where you can change the state manually by pressing a button. When not specified the components run with the speed of the external time base which is further divided by the individual period settings. All three components have the same frequency divider component. The divided frequency can be calculated by the following formula:

$$\text{divided frequency} = \frac{\text{frequency of external time base}}{\text{period register value}+1}$$

3.1 Mnemonics python script

In the script folder of this project two python scripts are provided. The `write_to_ttyUSBx.py` writes the serial commands that are written out as text to the device. All serial commands are defined in `test_variables.py` as a python dictionary that contains address byte and data byte.

3.2 PWM Component

 


Figure 7: Pwm implementation

With the implemented pwm component a duty cycle of 0%-99,6% percent is possible. It can be computed by $\text{duty cycle} = \frac{\text{pwm pulse width}}{256}$. One counting cycle is performed with the frequency of the divided frequency. This results in a frequency of $\frac{\text{divided frequency}}{256}$.

3.3 Noise Component

The noise component has an noise prbgs length and a period setting. The prbgs setting decides how many bits the lfsr has. That means it decides over the length of the pseudo random sequence until it repeats itself. They are designed after the given standards of pseudo random number generators and have different use cases. For more information about it see the standard

documentations. One full cycle has the frequency of $\frac{\text{divided frequency}}{2^n - 1}$ with n as the number of bits of the lfsr.

3.4 Pattern Component

The pattern generator has four possible control states:


- stop
 - the pattern generator is switched off
- load
 - the pattern generator is ready to receive the data sequence into its memory
 - before sending the number sequence the number of values must be specified in the pattern length register!
 - * e.g. pattern length 4 -> pattern load -> pattern sequence 4 5 7 2 -> single burst/continuous run
 - supports up to 256 single eight bit values
- single burst
 - a single burst puts out the sequence only once
- continuous run
 - puts out the sequence forever
 - stops when the pattern control bits change

One value of a sequence is available for the time of $\frac{1}{\text{divided frequency}}$. A full cycle that includes all values has the frequency of $\frac{\text{divided frequency}}{\text{pattern length}}$.

4 Design Description

4.1 UART serial receiver

The serial communication contains three main components. The serial_rx module is based on a design made using a Moore state machine and it was provided to the design team by the design manager. The purpose of the module is to allow for the correct sequencing and addressing of the data that arrives through serial communication. The module functions has a synchronous high active reset. This module directly communicates with the other state machine present on the project directly via the data valid signal, signaling that the address/data has arrived.

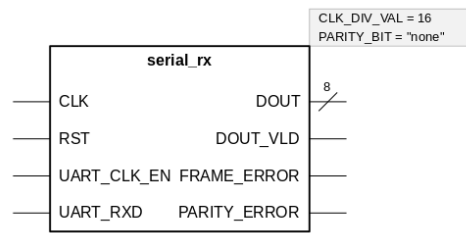**Figure 8:** Implemented Serial Receiver File - Schematic**Table 2:** I/O Table for the Serial Receiver

Name	Type	Direction	Polarity	Description
CLK	std_ulogic	IN	HIGH	
RST	std_ulogic	IN	HIGH	synchronous, high active
UART_CLK_EN	std_ulogic	IN	HIGH	frequency=baudrate*CLK_DIV_VAL
UART_RXD	std_ulogic	IN	HIGH	serial data in
DOUT	std_ulogic_vector[8]	OUT	HIGH	serial data
DOUT_VLD	std_ulogic	OUT	HIGH	serial data valid
FRAME_ERROR	std_ulogic	OUT	HIGH	
PARITY_ERROR		OUT	HIGH	

Name	Type	Value
CLK_DIV_VAL	integer	16
PARITY_BIT	string	"none"

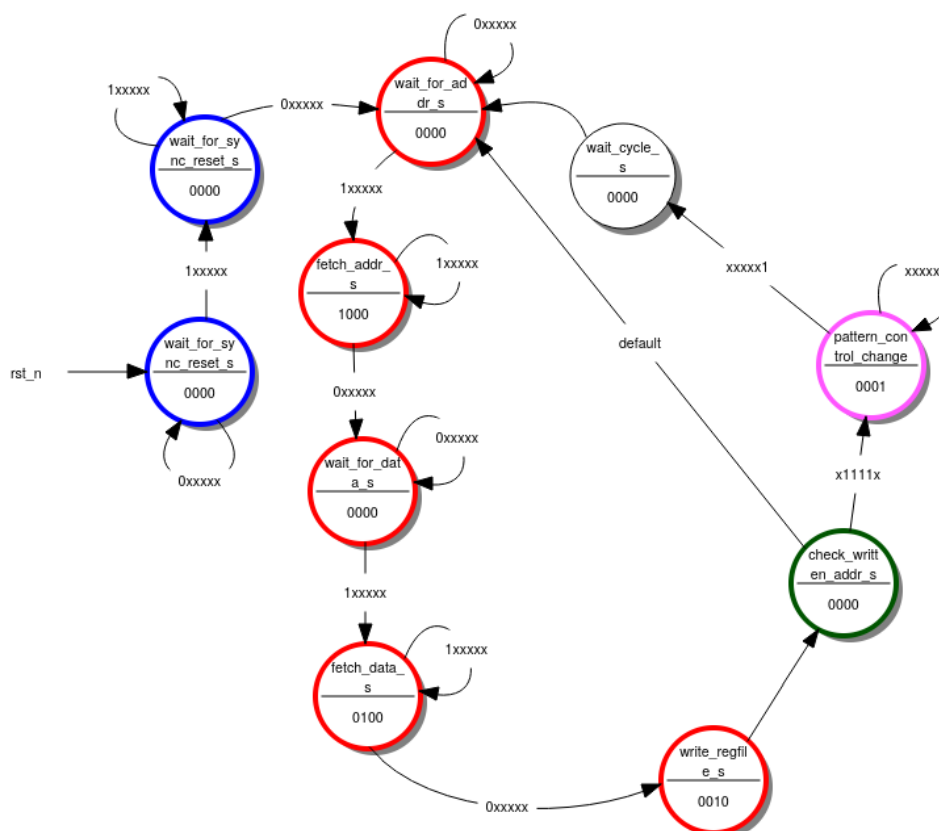


Figure 9: UART Serial Receiver State Machine File - Schematic

Colours on the state machine represent:

- Blue: This is a workaround to handle the `rx_d_rdy` signal causing errors in the operation. More information below.
- Red: This aspect of the state machine manages the receipt of the address and data information.
- Green: These states are to check if there is a change in the signal from pattern control. If there is a change, it then goes to the pink state.
- Pink: This single state is responsible for the communication with the Pattern State Machine. It sends out the `pm_control_changed` signal. The other state machine reacts on this signal and when it is finished it sends `pm_checked` for one cycle. Now this state machine can go back to the wait for address state.

Inputs:	rx_d_rec	addr[3..0]	pm_checked		
State/Output		en_addr_reg	en_data_reg	en_regfile_wr	pm_control_changed
wait_for_addr_s		0	0	0	0
fetch_addr_s		1	0	0	0
wait_for_data_s		0	0	0	0
fetch_data_s		0	1	0	0
write_regfile_s		0	0	1	0
check_written_addr_s		0	0	0	0
pattern_control_changed_s		0	0	0	1

```
wait_cycle_s           0           0           0           0
wait_for_sync_reset_serialrx_s 0           0           0           0
wait_for_sync_reset_serialrx2_s 0           0           0           0
```

This is then directly wired to the `serial_receiver_reg.vhd` module. It contains two registers. The purpose for this is that the register file (`regfile.vhd`) needs to know both the address and the data values simultaneously - meaning that the information must be stored somewhere temporarily before it can be written to the register file.

4.1.1 Data received after reset

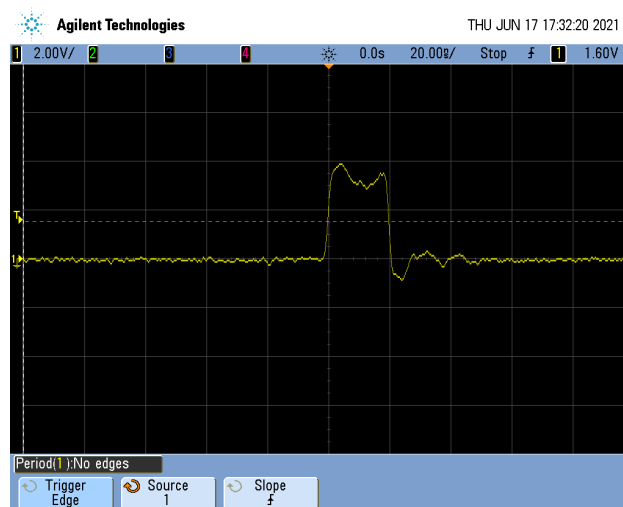


Figure 10: Data out valid after reset


The two states at the beginning of the serial receiver state machine are required to work around a problem that the serial rx component creates. After a reset the serial rx component puts out a data valid signal for one cycle. This seems to be a design problem (see `tsg testbench` at the beginning: `DIN_VLD`). Without these states we have the issue that after an reset we would immediately transition to the state were we are waiting for the data. We are skipping the address states. For that reason the first two states are added.

4.2 Pattern generator

The pattern generator contains a frequency control unit, state machine and an address upcounter for the additional memory that is contained in the `pattern_generator.vhd`. The output of the pattern generator is controlled by the state machine that controls the address upcounter which is responsible for the output of the memory.

Table 4: I/O Table for the Pattern Generator

Name	Type	Direction	Polarity	Description
en_write_pm	std_ulogic	IN	HIGH	write memory
clk_i	std_ulogic	IN	HIGH	
pm_control_i	std_ulogic_vector[2]	IN	HIGH	register file control
addr_cnt_i	std_ulogic_vector[8]	IN	HIGH	upcounted address
rx_data_i	std_ulogic_vector[8]	IN	HIGH	data from serial_rx
pattern_o	std_ulogic_vector[8]	OUT	HIGH	pattern output

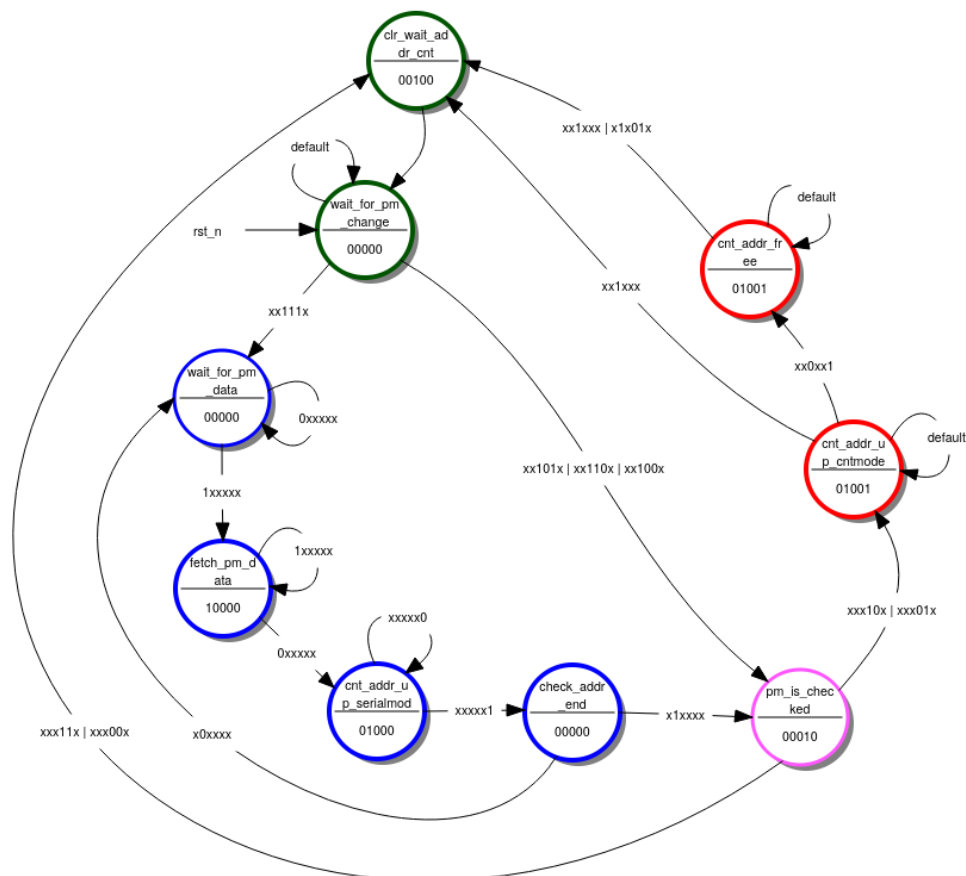**Figure 11:** Pattern Generator State Machine File - Schematic

Colours on the state machine represent:

- Blue: These states deal with the loading of the data and address information.
- Red: This aspect of the state machine is responsible for enabling the address upcounter. The first red state is a workaround for the tc_pm signal put out by the address upcounter.

It is one when the counter is at zero. Without the first red state we would immediately transition through the second red state.

- Green: These states are to manage the initialisation and the reset of the state machine.
- Pink: This single state is responsible for the communication with the Serial Communication State Machine.

Inputs:	rx_d_rec	tc_pm	pm_control_changed	pm_control[1..0]	addr_cnt_enable
State/Output	en_pm	en_pm_cnt	clr_pm_cnt	pm_checked	pattern_valid
wait_for_pm_change	0	0	0	0	0
clr_wait_addr_cnt	0	0	1	0	0
wait_for_pm_data	0	0	0	0	0
fetch_pm_data	1	0	0	0	0
cnt_addr_up_serialmode	0	1	0	0	0
check_addr_end	0	0	0	0	0
pm_is_checked	0	0	0	1	0
cnt_addr_up_cntmode	0	1	0	0	1
cnt_addr_free	0	1	0	0	1

4.3 Pulse-width modulation

The PWM generator module is connected to one of the instantiations of the freq_control module. The output from the Frequency Control module is input to the enable of the PWM generator to assign the total width (and thus the frequency) of the PWM.

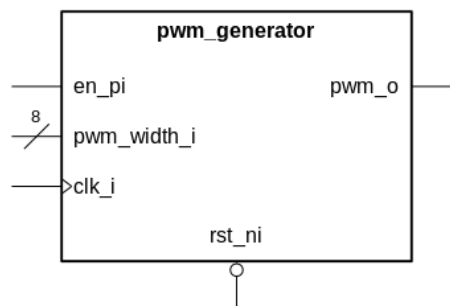


Figure 12: Implemented PWM File - Schematic

Table 5: I/O Table for the PWM Generator

Name	Type	Direction	Polarity	Description
en_pi	std_ulogic	IN	HIGH	
rst_ni	std_ulogic	IN	LOW	
pwm_width_i	std_ulogic_vector[8]	IN	HIGH	on pulse width of pwm

Name	Type	Direction	Polarity	Description
clk_i	std_ulogic	IN	HIGH	
pwm_o	std_ulogic	OUT	HIGH	pwm output

4.4 Pseudo-random number generator (LFSR)

The design of the LFSR was made to be as configurable as possible. The `config_noise_generator.vhd` contains a configurable noise generator. You can decide the size (number of registers), and the position of the two connections of the feedback XOR. This component is instantiated multiple times in the `noise_generator.vhd`. The module outputs three different signals, `prbs_o`, `noise_o` and `eoc_o`.

- `prbs_o` - The full noise signal. Bit size is constant but active bits depend on chosen LFSR.
- `noise_o` - This is the noise signal output, the signal that can be used by a user for testing their device.
- `eoc_o` - Sends a pulse once all random numbers have been generated, thus completing a cycle.

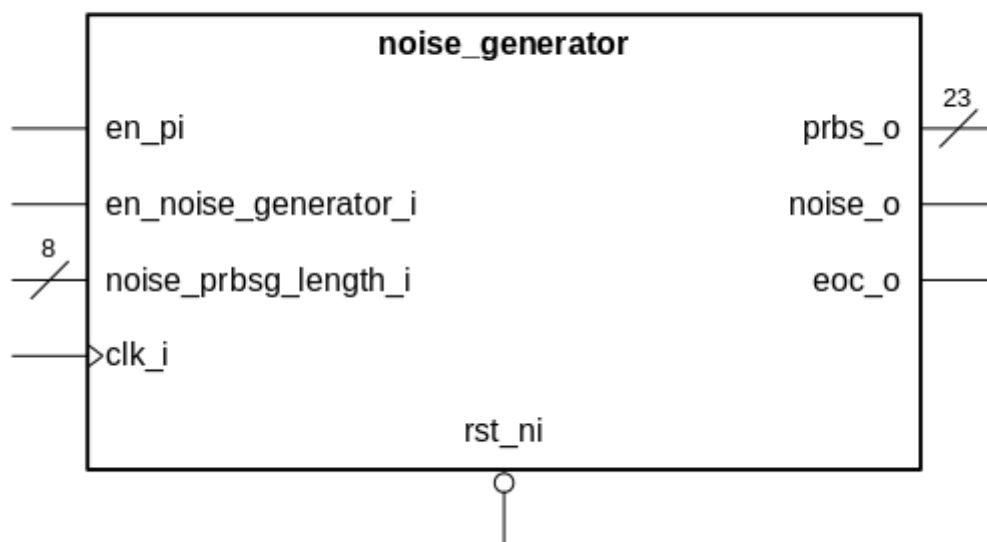


Figure 13: Implemented LFSR

4.5 External time base and external triggering design

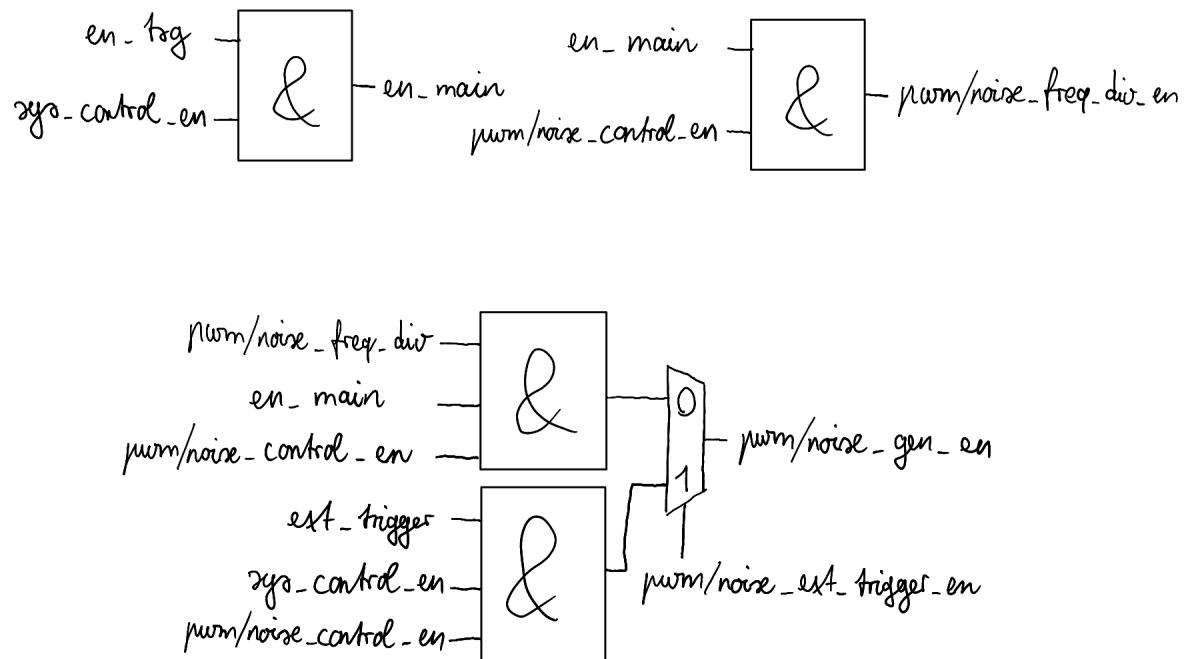


Figure 14: Noise/PWM enable and external trigger design

To get the external time base and external triggering to work correctly multiple AND gates and multiplexer are needed. For the pwm and the noise generator we have the same design. If the noise generator is enabled depends on the following conditions:

- the whole system is enabled
- pwm/noise generator is enabled
- external time base on
- frequency divider enabled

When the external triggering of the noise/pwm generator is enabled it should only be controlled by external triggering if the system is on and the pwm/noise generator is enabled.

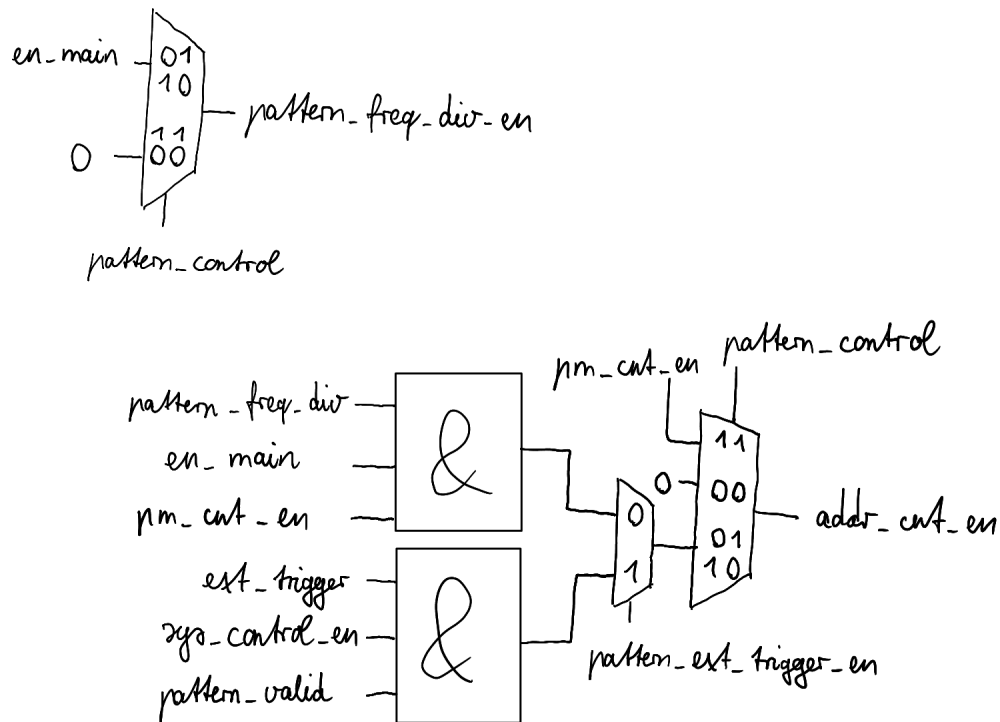


Figure 15: Pattern enable and external trigger design

For the pattern generator a more sophisticated system is needed. We need to differentiate between the four modes of our pattern generator:

- 00 stop
- 01 single burst
- 10 continuous run
- 11 load

In stop and load mode we do not care about the external triggering and the external time base. When loading the pattern generator the address upcounter only counts up when the pattern generator state machine gives an signal. Note that the address upcounter decides over the frequency of the pattern output, not the pattern generator (pattern memory) itself. The external trigger, external time base and frequency divider matters when we are in the two run modes. For the external triggering we need the additional signal pattern valid. This signal is provided by the pattern generator state machine and is true when the state machine is in a counting state. This is needed for the single burst mode to stop counting after one counting cycle.

5 Test Results

5.1 Noise Generator

 


Figure 16: Oscilloscope readings of the Noise Generator with a period and width of one.

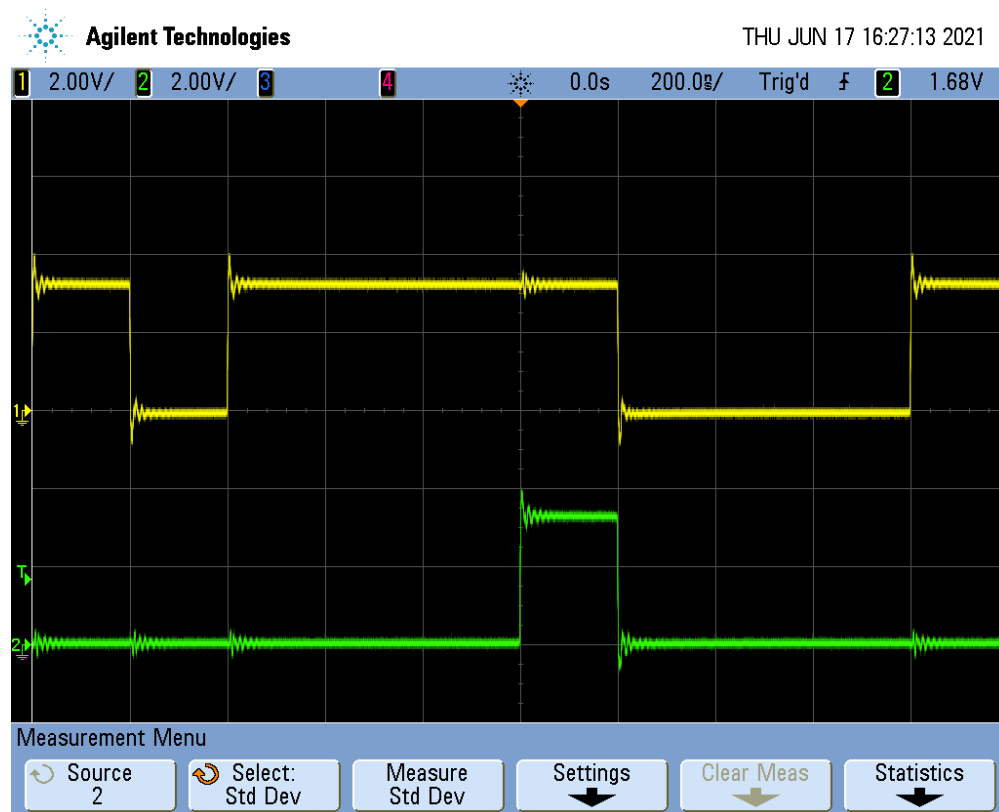


Figure 17: Oscilloscope readings of the Noise Generator with a period and width of one. Example of bitwidth

Expected results are found by implementing the formulae in section 3.

Table 6: Results from testing the Noise Generator

Number of Bits	Period Data	Expected Period(μ s)	Actual Period (μ s)
4	1	3	3
4	2	4.5	4.5
7	1	25.4	25.4
7	2	38.1	38.1

The external triggering was tested manually for the 4 and 7 bit noise generator.

5.2 PWM Generator

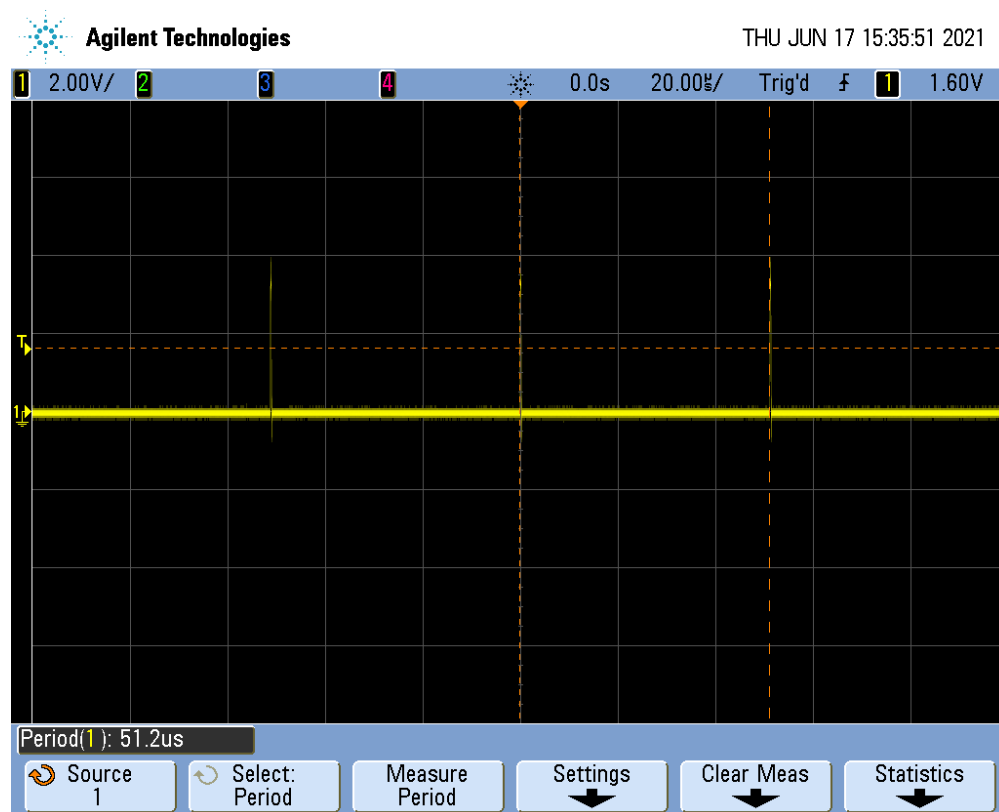


Figure 18: Oscilloscope readings of the PWM Generator with a period and width of one. Example of bitwidth

 


Figure 19: Oscilloscope readings of the PWM Generator with a period and width of 127. Example of bitwidth

Table 7: Results from testing the PWM Generator


Width Data	Period	Expected Period(μ s)	Actual Period (μ s)
1	1	51.2	51.2
1	4	128	128
127	1	51.2	51.2
128	1	51.2	51.2
255	1	51.2	51.2

The external triggering from the PWM generator was tested inside the simulator `t_tsg.vhd` because the counting value can be seen.

5.3 Pattern Generator

The pattern generator was tested manually with the external trigger on the board. A test with the oscilloscope is necessary to confirm that the variable frequency works as intended.

6 Application Note

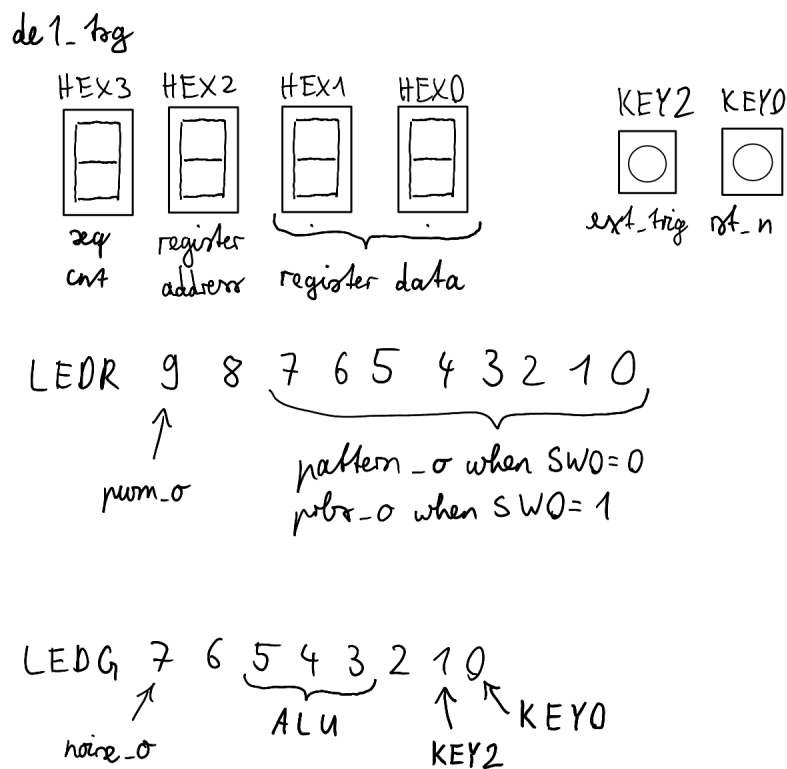

The wiring of the DE1 Board can be seen in the picture above. The test signal generator runs with an 50 MHz clock and a time base of 10 MHz on the enable. An synchroniser is added before the serial input to avoid metavalues because of asynchronous serial communication from the pc. The outputs of the test signal generator were connected to test components ALU and a 101 sequence detector. On the HEX3 display the number of 101 sequences detected is shown. Additionally some outputs are connected to the GPIOs for measurements. For the connections see `de1_tsg_structure.vhd`.

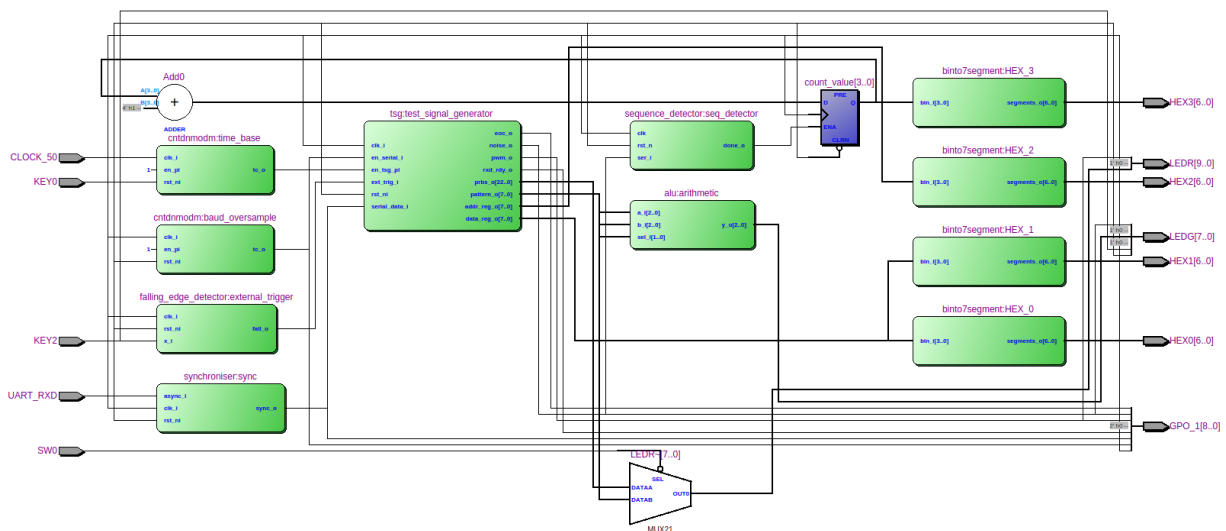


Figure 20: Connected components on DE1 Altera Board

7 Further Improvements

7.1 System Control Register

In the system control register is a bit included to do an synchronous clear over serial communication. It adds another possibility to reset the states of the synchronous components. At the moment only the asynchronous reset is available. To add this functionality an synchronous reset needs to be added to every component except the memory components (register file, pattern generator) and the address upcounter (has already one).

7.2 PWM Switch Off

When the PWM module is switched off either by the system control or the pwm control the counters in the frequency control and pwm generator are kept in their current counting state. This could result in an constant output of a one. To solve this problem it is recommended to put in a switch in the pwm generator that puts out zero when the system control AND pwm control is zero. This approach is already implemented for the noise generator and can be implemented in the same way (see input `en_noise_generator_i`).

7.3 Testbench `tsg` and `de1_tsg`

With the fix in the serial receiver state machine (states at beginning) that solve the issue of data valid signal after reset a different problem occurred. In the real system the fix works but in the simulation this scenario does not happen. We have an immediate one after the reset and not a

zero and then the pulse of the data like in the real system. A possible fix is to add an additional state to the state machine.

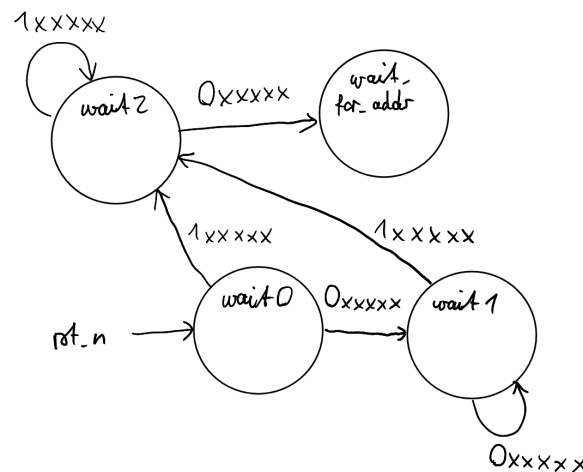


Figure 21: State Machine Fix

7.4 More Test Scenarios

The pattern generator was not evaluated on the oscilloscope. It was only tested manually with the external trigger, where it worked correctly (burst mode and continuous run). That means it needs to be tested if the frequency in the automatic mode is correct.

8 References

- 1: www.digi.com - UART Example
- 2: www.researchgate.net - Four Bit Linear Shift Register
- 3: www.wiki.analog.com - PWM Example

9 Appendix

9.1 Device Utilization and Performance

The following tables show the device utilization and the timing analysis results.

```

+-----+
; Fitter Summary                                     ;
+-----+-----+
; Fitter Status                                     ; Successful - Tue Jun 22 17:39:17 2021 ;
; Quartus II 32-bit Version                         ; 13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition ;

```

```

; Revision Name                ; del_tsg                ;
; Top-level Entity Name       ; del_tsg                ;
; Family                      ; Cyclone II             ;
; Device                      ; EP2C20F484C7           ;
; Timing Models               ; Final                  ;
; Total logic elements        ; 403 / 18,752 ( 2 % )   ;
;   Total combinational functions ; 328 / 18,752 ( 2 % )   ;
;   Dedicated logic registers  ; 276 / 18,752 ( 1 % )   ;
; Total registers             ; 276                    ;
; Total pins                  ; 60 / 315 ( 19 % )      ;
; Total virtual pins          ; 0                      ;
; Total memory bits           ; 2,048 / 239,616 ( < 1 % ) ;
; Embedded Multiplier 9-bit elements ; 0 / 52 ( 0 % )      ;
; Total PLLs                  ; 0 / 4 ( 0 % )         ;
+-----+-----+-----+

```

```

+-----+
; TimeQuest Timing Analyzer Summary
+-----+
; Quartus II Version ; Version 13.0.1 Build 232 06/12/2013 Service Pack 1 SJ Web Edition ;
; Revision Name      ; del_tsg
; Device Family      ; Cyclone II
; Device Name        ; EP2C20F484C7
; Timing Models      ; Final
; Delay Model        ; Combined
; Rise/Fall Delays   ; Unavailable
+-----+

```

```

+-----+
; Clocks
+-----+-----+-----+-----+
; Clock Name ; Type ; Period ; Frequency ;
+-----+-----+-----+-----+
; CLOCK_50   ; Base ; 20.000 ; 50.0 MHz ;
+-----+-----+-----+-----+

```

```

+-----+
; Multicorner Timing Analysis Summary
+-----+-----+-----+-----+-----+
; Clock          ; Setup ; Hold  ; Recovery ; Removal ; Minimum Pulse Width ;
+-----+-----+-----+-----+-----+
; Worst-case Slack ; 2.201 ; 0.215 ; 12.201  ; 4.354  ; 7.436
; CLOCK_50         ; 2.201 ; 0.215 ; 12.201  ; 4.354  ; 7.436
; Design-wide TNS  ; 0.0   ; 0.0   ; 0.0     ; 0.0    ; 0.0
; CLOCK_50         ; 0.000 ; 0.000 ; 0.000   ; 0.000  ; 0.000
+-----+-----+-----+-----+-----+

```

9.2 Project Hierarchy

```

.
+-- doc
|   +-- datasheet.yaml
|   +-- images
|   +-- makefile
|   +-- presentation.yaml
|   +-- report.yaml

```

```
| +-- tables
| +-- test_signal_generator_datasheet.md
| +-- test_signal_generator_presentation.md
| +-- test_signal_generator_report.md
| +-- test_signal_generator_report.pdf
| +-- uasa_meng_vlsi_template.tex
| +-- vec.conf
+-- pnr
| +-- de1_binto7segment
| +-- de1_cntdnmodm
| +-- de1_serial_rx
| +-- de1_tsg
| +-- makefile
+-- README.md
+-- scripts
| +-- create_quartus_project_settings.tcl
| +-- de1_pin_assignments_minimumio.tcl
| +-- modelsim.ini
| +-- quartus_project_flow.tcl
| +-- test_variables.py
| +-- write_to_ttyUSBx.py
+-- sim
| +-- binto7segment
| +-- cntdnmodm
| +-- cntup_addr
| +-- de1_tsg
| +-- makefile
| +-- noise_generator
| +-- pattern_generator
| +-- pwm_generator
| +-- serial_rx
| +-- tsg
+-- src
+-- 101SequenceQfsm.fsm
+-- a_falling_edge_detector_rtl.vhd
+-- alu.vhd
+-- alu.vhd.bak
+-- a_tsg_structure.vhd
+-- a_tsg_structure.vhd.bak
+-- binto7segment_truthtable.vhd
+-- cntdnmodm_rtl.vhd
+-- cntup_addr.vhd
+-- cntup_addr.vhd.bak
+-- config_noise_generator.vhd
+-- config_noise_generator.vhd.bak
+-- de1_serial_rx_structure.vhd
+-- de1_tsg_structure.vhd
+-- de1_tsg_structure.vhd.bak
+-- e_falling_edge_detector.vhd
+-- e_tsg.vhd
+-- freq_control.vhd
+-- noise_generator.vhd
+-- noise_generator.vhd.bak
+-- pattern_generator_fsm.vhd
+-- pattern_generator_qfsm.fsm
+-- pattern_generator.vhd
+-- pwm_generator.vhd
+-- regfile_rtl.vhd
+-- regfile_rtl.vhd.bak
+-- sequence_detector.vhd
+-- serial_receiver_fsm.vhd
+-- serial_receiver_qfsm.fsm
```

```
+++ serial_receiver_reg.vhd
+++ serial_receiver_reg.vhd.bak
+++ serial_rx.vhd
+++ serial_tx.vhd
+++ sp_ssram_rtl.vhd
+++ synchroniser.vhd
+++ synchroniser.vhd.bak
+++ t_cntup_addr.vhd
+++ t_de1_tsg.vhd
+++ t_noise_generator.vhd
+++ t_pattern_generator.vhd
+++ t_pwm_generator.vhd
+++ t_serial_receiver_fsm.vhd
+++ t_serial_rx.vhd
+++ t_tsg.vhd
+++ uart_clk_div.vhd
+++ uart_parity.vhd
```

9.3 Module Hierarchy

tsg testbench:

```
t_tsg(tbench)
  e_tsg.vhd
  a_tsg_structure.vhd
  uart_clk_div.vhd
  uart_parity.vhd
  serial_rx.vhd
  serial_tx.vhd
  serial_receiver_reg.vhd
  serial_receiver_fsm.vhd
  regfile_rtl.vhd
  freq_control.vhd
  pwm_generator.vhd
  noise_generator.vhd
  config_noise_generator.vhd
  pattern_generator.vhd
  pattern_generator_fsm.vhd
  cntup_addr.vhd
  sp_ssram_rtl.vhd
  cntdnmodm_rtl.vhd
```

de1_tsg:

```
de1_tsg(structure)
  binto7segment_truthtable.vhd
  cntdnmodm_rtl.vhd
  synchroniser.vhd
  a_falling_edge_detector_rtl.vhd
  e_falling_edge_detector.vhd
  sequence_detector.vhd
  alu.vhd
  de1_tsg_structure.vhd
```

All files in tsg testbench also needed in de1_tsg.

9.4 Code

tsg:

```

-----
-- Module      : tsg
-----

-- Author       : Johann Faerber
-- Company      : University of Applied Sciences Augsburg
-----

-- Description: Test Signal Generator
-----

-- Revisions    : see end of file
-----

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

ENTITY tsg IS
  PORT (
    clk_i          : IN  std_logic;
    rst_ni         : IN  std_logic;
    en_tsg_pi       : IN  std_logic; -- tsg enable, used with external time base
    en_serial_i     : IN  std_logic; -- enable for serial data: oversample of 16 with expected
    ↪ baudrate 9600
    serial_data_i   : IN  std_logic; -- serial data with baudrate 9600
    rxd_rdy_o       : OUT std_logic; -- debugging signal, output of serial_rx if serial data is
    ↪ ready to be read
    ext_trig_i      : IN  std_logic; -- external trigger for triggering test equipment
    pwm_o           : OUT std_logic; -- pulse width modulated signal
    noise_o         : OUT std_logic; -- 1 bit pseudo random noise
    prbs_o          : OUT std_logic_vector(22 DOWNTO 0); -- pseudo random noise up to 23 bit
    eoc_o           : OUT std_logic; -- end of cycle when pseudo random noise repeats
    pattern_o       : OUT std_logic_vector(7 DOWNTO 0); -- configurable changing pattern output
    pattern_valid_o : OUT std_logic; -- pattern valid, not currently implemented! (see
    ↪ improvements)
    tc_pm_count_o   : OUT std_logic; -- debugging signal, end of cycle for pattern memory
    ↪ upcounter
    regfile_o       : OUT std_logic_vector(7 DOWNTO 0); -- debugging signal, data input of
    ↪ register file
    addr_reg_o      : OUT std_logic_vector(7 DOWNTO 0); -- debugging signal, address output of
    ↪ serial_receiver registers
    data_reg_o      : OUT std_logic_vector(7 DOWNTO 0) -- debugging signal, data output of
    ↪ serial_receiver registers
  );
END tsg;

-----

-- Revisions:
-- -----
-- $Id:$
-----

```

tsg:

```

-----
-- Module      : structure of tsg
-----

-- Author       : Johann Faerber

```



```

-- Company      : University of Applied Sciences Augsburg
-----
-- Description: Test Signal Generator
-----
-- Revisions   : see end of file
-----

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ARCHITECTURE structure OF tsg IS

    -- components for serial communication
    COMPONENT serial_rx IS
        GENERIC (
            CLK_DIV_VAL : integer;
            PARITY_BIT   : string);
        PORT (
            CLK           : IN  std_ulogic;
            RST           : IN  std_ulogic;
            UART_CLK_EN   : IN  std_ulogic;
            UART_RXD      : IN  std_ulogic;
            DOUT          : OUT std_ulogic_vector(7 DOWNTO 0);
            DOUT_VLD      : OUT std_ulogic;
            FRAME_ERROR   : OUT std_ulogic;
            PARITY_ERROR  : OUT std_ulogic);
    END COMPONENT serial_rx;

    COMPONENT serial_receiver_reg IS
        PORT (
            rst_ni        : IN  std_ulogic;
            clk_i          : IN  std_ulogic;
            en_addr_reg_i  : IN  std_ulogic;
            en_data_reg_i  : IN  std_ulogic;
            rxd_data_i     : IN  std_ulogic_vector(7 DOWNTO 0);
            regfile_addr_o : OUT std_ulogic_vector(3 DOWNTO 0);
            regfile_data_o : OUT std_ulogic_vector(7 DOWNTO 0));
    END COMPONENT serial_receiver_reg;

    COMPONENT serial_receiver_fsm IS
        PORT (
            clk           : IN  std_ulogic;
            rst_n         : IN  std_ulogic;
            rxd_rec       : IN  std_ulogic;
            addr          : IN  std_ulogic_vector(3 DOWNTO 0);
            pm_checked    : IN  std_ulogic;
            en_addr_reg   : OUT std_ulogic;
            en_data_reg   : OUT std_ulogic;
            en_regfile_wr : OUT std_ulogic;
            pm_control_changed : OUT std_ulogic);
    END COMPONENT serial_receiver_fsm;

    COMPONENT regfile IS
        GENERIC (
            ADDR_WIDTH : integer;
            DATA_WIDTH : integer);
        PORT (
            clk_i        : IN  std_ulogic;
            wr_en_i       : IN  std_ulogic;
            w_addr_i      : IN  std_ulogic_vector (ADDR_WIDTH-1 DOWNTO 0);
            r_addr_i      : IN  std_ulogic_vector (ADDR_WIDTH-1 DOWNTO 0);

```

```

w_data_i      : IN  std_ulogic_vector (DATA_WIDTH-1 DOWNT0 0);
system_control_o : OUT std_ulogic_vector(1 DOWNT0 0);
pwm_pulse_width_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pwm_period_o    : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pwm_control_o   : OUT std_ulogic_vector(1 DOWNT0 0);
noise_length_o  : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
noise_period_o  : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
noise_control_o : OUT std_ulogic_vector(1 DOWNT0 0);
pattern_mem_depth_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pattern_period_o : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pattern_control_o : OUT std_ulogic_vector(2 DOWNT0 0);
r_data_o       : OUT std_ulogic_vector (DATA_WIDTH-1 DOWNT0 0));

END COMPONENT regfile;

-- for noise, pattern and pwm
COMPONENT freq_control IS
  PORT (
    clk_i      : IN  std_ulogic;
    rst_ni     : IN  std_ulogic;
    en_pi      : IN  std_ulogic;
    count_o    : OUT std_ulogic_vector(7 DOWNT0 0);
    freq_o     : OUT std_ulogic;
    period_i   : IN  std_ulogic_vector(7 DOWNT0 0));
END COMPONENT freq_control;

-- for pwm
COMPONENT pwm_generator IS
  PORT (
    en_pi      : IN  std_ulogic;
    rst_ni     : IN  std_ulogic;
    pwm_width_i : IN  std_ulogic_vector(7 DOWNT0 0);
    clk_i      : IN  std_ulogic;
    pwm_o      : OUT std_ulogic);
END COMPONENT pwm_generator;

-- for noise
COMPONENT noise_generator IS
  PORT (
    clk_i      : IN  std_ulogic;
    rst_ni     : IN  std_ulogic;
    en_pi      : IN  std_ulogic;
    en_noise_generator_i : IN  std_ulogic;
    noise_prbsg_length_i : IN  std_ulogic_vector(7 DOWNT0 0);
    prbs_o     : OUT std_ulogic_vector(22 DOWNT0 0);
    noise_o    : OUT std_ulogic;
    eoc_o      : OUT std_ulogic);
END COMPONENT noise_generator;

-- for pattern
COMPONENT pattern_generator IS
  PORT (
    en_write_pm : IN  std_ulogic;
    clk_i       : IN  std_ulogic;
    pm_control_i : IN  std_ulogic_vector(1 DOWNT0 0);
    addr_cnt_i  : IN  std_ulogic_vector(7 DOWNT0 0);
    rxd_data_i  : IN  std_ulogic_vector(7 DOWNT0 0);
    pattern_o   : OUT std_ulogic_vector(7 DOWNT0 0));
END COMPONENT pattern_generator;

COMPONENT pattern_generator_fsm IS
  PORT (
    clk      : IN  std_ulogic;

```

```

    rst_n          : IN std_ulogic;
    rxd_rec        : IN std_ulogic;
    tc_pm          : IN std_ulogic;
    pm_control_changed : IN std_ulogic;
    pm_control      : IN std_ulogic_vector(1 DOWNTO 0);
    addr_cnt_enabled : IN std_ulogic;
    en_pm           : OUT std_ulogic;
    en_pm_cnt       : OUT std_ulogic;
    clr_pm_cnt      : OUT std_ulogic;
    pm_checked      : OUT std_ulogic;
    pattern_valid    : OUT std_ulogic);
END COMPONENT pattern_generator_fsm;

COMPONENT cntup_addr IS
  PORT (
    clk_i  : IN std_ulogic;
    clr_i  : IN std_ulogic;
    rst_ni : IN std_ulogic;
    en_pi  : IN std_ulogic;
    len_i  : IN std_ulogic_vector(7 DOWNTO 0);
    q_o    : OUT std_ulogic_vector(7 DOWNTO 0);
    tc_o   : OUT std_ulogic);
END COMPONENT cntup_addr;

-- serial components instantiation
CONSTANT CLK_DIV_VAL      : integer := 16;
CONSTANT PARITY_BIT       : string  := "none";
CONSTANT regfile_addr_width : integer := 4;
CONSTANT regfile_data_width : integer := 8;

-- basic signals
SIGNAL clock      : std_ulogic;
SIGNAL reset      : std_ulogic;
SIGNAL en_main    : std_ulogic;      -- en_tsg and en_system
SIGNAL ext_trigger : std_ulogic;

-- serial signals
SIGNAL en_serial      : std_ulogic;
SIGNAL serial_data    : std_ulogic;
SIGNAL serial_data_o  : std_ulogic_vector(7 DOWNTO 0);
SIGNAL serial_data_valid_o : std_ulogic;

SIGNAL regfile_addr_o : std_ulogic_vector(regfile_addr_width - 1 DOWNTO 0);
SIGNAL regfile_data_o : std_ulogic_vector(regfile_data_width - 1 DOWNTO 0);

SIGNAL en_addr_reg  : std_ulogic;
SIGNAL en_data_reg  : std_ulogic;
SIGNAL en_regfile_wr : std_ulogic;

-- state machine communication
SIGNAL pm_checked      : std_ulogic;
SIGNAL pm_control_changed : std_ulogic;

-- regfile signals
SIGNAL system_control_o : std_ulogic_vector(1 DOWNTO 0);
SIGNAL pwm_pulse_width_o : std_ulogic_vector(regfile_data_width-1 DOWNTO 0);
SIGNAL pwm_period_o      : std_ulogic_vector(regfile_data_width-1 DOWNTO 0);
SIGNAL pwm_control_o     : std_ulogic_vector(1 DOWNTO 0);
SIGNAL noise_length_o    : std_ulogic_vector(regfile_data_width-1 DOWNTO 0);
SIGNAL noise_period_o    : std_ulogic_vector(regfile_data_width-1 DOWNTO 0);
SIGNAL noise_control_o   : std_ulogic_vector(1 DOWNTO 0);
SIGNAL pattern_length_o  : std_ulogic_vector(regfile_data_width-1 DOWNTO 0);

```

```

SIGNAL pattern_period_o  : std_ulogic_vector(regfile_data_width-1 DOWNTO 0);
SIGNAL pattern_control_o : std_ulogic_vector(2 DOWNTO 0);

-- noise signals
SIGNAL noise_freq_div : std_ulogic;
SIGNAL en_noise_gen   : std_ulogic;

-- pwm signals
SIGNAL pwm_freq_div : std_ulogic;
SIGNAL en_pwm_gen   : std_ulogic;

-- pattern signals
SIGNAL pattern_freq_div      : std_ulogic;
SIGNAL en_write_pm          : std_ulogic;
SIGNAL en_cntup_addr        : std_ulogic;
SIGNAL en_pattern_freq_div  : std_ulogic;
SIGNAL en_pm_cnt            : std_ulogic;
SIGNAL en_continuous_cntup_addr : std_ulogic;
SIGNAL clr_cntup_addr       : std_ulogic;
SIGNAL cntup_addr_o         : std_ulogic_vector(7 DOWNTO 0);
SIGNAL cntup_addr_tc        : std_ulogic;
SIGNAL pattern_valid       : std_ulogic;

BEGIN

serial_rx_uart : serial_rx
  GENERIC MAP (
    CLK_DIV_VAL => CLK_DIV_VAL,
    PARITY_BIT  => PARITY_BIT)
  PORT MAP (
    CLK      => clock,
    RST      => NOT reset, -- workaround is an synchronous high active reset!
    UART_CLK_EN => en_serial,
    UART_RXD   => serial_data,
    DOUT       => serial_data_o,
    DOUT_VLD   => serial_data_valid_o,
    FRAME_ERROR => OPEN,
    PARITY_ERROR => OPEN);

serial_receiver_registers : serial_receiver_reg
  PORT MAP (
    rst_ni      => reset,
    clk_i       => clock,
    en_addr_reg_i => en_addr_reg,
    en_data_reg_i => en_data_reg,
    rxd_data_i   => serial_data_o,
    regfile_addr_o => regfile_addr_o,
    regfile_data_o => regfile_data_o);

serial_receiver_state_machine : serial_receiver_fsm
  PORT MAP (
    clk          => clock,
    rst_n        => reset,
    rxd_rec      => serial_data_valid_o,
    addr         => regfile_addr_o,
    pm_checked   => pm_checked,
    en_addr_reg  => en_addr_reg,
    en_data_reg  => en_data_reg,
    en_regfile_wr => en_regfile_wr,
    pm_control_changed => pm_control_changed);

register_file : regfile

```

```

GENERIC MAP (
    ADDR_WIDTH => regfile_addr_width,
    DATA_WIDTH => regfile_data_width)
PORT MAP (
    clk_i           => clock,
    wr_en_i         => en_regfile_wr,
    w_addr_i        => regfile_addr_o,
    r_addr_i        => (OTHERS => '0'), -- not used
    w_data_i        => regfile_data_o,
    system_control_o => system_control_o,
    pwm_pulse_width_o => pwm_pulse_width_o,
    pwm_period_o    => pwm_period_o,
    pwm_control_o    => pwm_control_o,
    noise_length_o   => noise_length_o,
    noise_period_o   => noise_period_o,
    noise_control_o  => noise_control_o,
    pattern_mem_depth_o => pattern_length_o,
    pattern_period_o => pattern_period_o,
    pattern_control_o => pattern_control_o,
    r_data_o         => OPEN); -- not used

-- pwm components
pwm_freq_control : freq_control
PORT MAP (
    clk_i    => clock,
    rst_ni   => reset,
    en_pi    => en_main AND pwm_control_o(0),
    count_o  => OPEN,
    freq_o   => pwm_freq_div,
    period_i => pwm_period_o);

pwm_gen : pwm_generator
PORT MAP (
    en_pi    => en_pwm_gen,
    rst_ni   => reset,
    pwm_width_i => pwm_pulse_width_o,
    clk_i    => clock,
    pwm_o    => pwm_o);

-- noise components
noise_freq_control : freq_control
PORT MAP (
    clk_i    => clock,
    rst_ni   => reset,
    en_pi    => en_main AND noise_control_o(0),
    count_o  => OPEN,
    freq_o   => noise_freq_div,
    period_i => noise_period_o);

noise_gen : noise_generator
PORT MAP (
    clk_i           => clock,
    rst_ni          => reset,
    en_pi           => en_noise_gen,
    en_noise_generator_i => system_control_o(0) AND noise_control_o(0),
    noise_prbsg_length_i => noise_length_o,
    prbs_o          => prbs_o,
    noise_o         => noise_o,
    eoc_o           => eoc_o);

-- pattern components
pattern_freq_control : freq_control

```

```

PORT MAP (
    clk_i    => clock,
    rst_ni   => reset,
    en_pi    => en_pattern_freq_div,
    count_o  => OPEN,
    freq_o   => pattern_freq_div,
    period_i => pattern_period_o);

pattern_gen : pattern_generator
PORT MAP (
    en_write_pm => en_write_pm,
    clk_i       => clock,
    pm_control_i => pattern_control_o(1 DOWNT0 0),
    addr_cnt_i  => cntup_addr_o,
    rxd_data_i  => serial_data_o,
    pattern_o   => pattern_o);

pattern_generator_state_machine : pattern_generator_fsm
PORT MAP (
    clk           => clock,
    rst_n         => reset,
    rxd_rec       => serial_data_valid_o,
    tc_pm         => cntup_addr_tc,
    pm_control_changed => pm_control_changed,
    pm_control    => pattern_control_o(1 DOWNT0 0),
    addr_cnt_enabled => en_cntup_addr,
    en_pm         => en_write_pm,
    en_pm_cnt     => en_pm_cnt,
    clr_pm_cnt    => clr_cntup_addr,
    pm_checked    => pm_checked,
    pattern_valid => pattern_valid);

cntup_address : cntup_addr
PORT MAP (
    clk_i => clock,
    clr_i => clr_cntup_addr,
    rst_ni => reset,
    en_pi => en_cntup_addr,
    len_i => pattern_length_o,
    q_o  => cntup_addr_o,
    tc_o => cntup_addr_tc);

-- basic signals connections
clock    <= clk_i;
reset    <= rst_ni;
ext_trigger <= ext_trig_i;
en_main  <= en_tsg_pi AND system_control_o(0);

-- output signals
rxd_rdy_o    <= serial_data_valid_o;
tc_pm_count_o <= cntup_addr_tc;
pattern_valid_o <= pattern_valid;
regfile_o    <= regfile_data_o; -- write data
addr_reg_o   <= std_ulogic_vector(resize(unsigned(regfile_addr_o), 8));
data_reg_o   <= regfile_data_o;

-- serial data connections
en_serial <= en_serial_i;
serial_data <= serial_data_i;

-- pwm connections
en_pwm_gen <= (pwm_freq_div AND en_main AND pwm_control_o(0)) WHEN pwm_control_o(1) = '0'

```

```

        ELSE (ext_trigger AND system_control_o(0) AND pwm_control_o(0));

-- noise connections
en_noise_gen <= (noise_freq_div AND en_main AND noise_control_o(0)) WHEN noise_control_o(1) =
↪ '0'
        ELSE (ext_trigger AND system_control_o(0) AND noise_control_o(0));

-- pattern connections
WITH pattern_control_o(1 DOWNT0 0) SELECT
    en_pattern_freq_div <= en_main WHEN "01" | "10", -- burst or continous burst
    '0'                      WHEN "00" | "11", -- stop or load
    '0'                      WHEN OTHERS;

en_continuous_cntup_addr <= (en_main AND en_pm_cnt AND pattern_freq_div) WHEN
↪ pattern_control_o(2) = '0'
        ELSE (ext_trigger AND system_control_o(0) AND pattern_valid);

WITH pattern_control_o(1 DOWNT0 0) SELECT
    en_cntup_addr <= en_pm_cnt WHEN "11", -- load, speed of clock
    en_continuous_cntup_addr WHEN "01" | "10", -- burst or continous burst;
    -- speed of enable
    '0'              WHEN "00", -- stop
    '0'              WHEN OTHERS;

END structure;

-----
-- Revisions:
-- -----
-- $Id:$
-----

```

serial:

```

-----
-- Module      : serial_rx
-----
-- modified by: Johann Faerber
-----
--              modified according to our design rules:
--              using std_ulogic instead of std_logic
-----
-- Original PROJECT: SIMPLE UART FOR FPGA
-----
-- AUTHORS: Jakub Cabal <jakubcabal@gmail.com>
-- LICENSE: The MIT License, please read LICENSE file
-- WEBSITE: https://github.com/jakubcabal/uart-for-fpga
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;

ENTITY serial_rx IS
    GENERIC (
        CLK_DIV_VAL : integer := 16;
        PARITY_BIT   : string  := "none" -- type of parity: "none", "even", "odd", "mark", "space"
    );
    PORT (
        CLK           : IN std_ulogic; -- system clock

```

```

RST          : IN  std_ulogic;      -- high active synchronous reset
-- UART INTERFACE
UART_CLK_EN  : IN  std_ulogic;      -- oversampling (16x) UART clock enable
UART_RXD     : IN  std_ulogic;      -- serial receive data
-- USER DATA OUTPUT INTERFACE
DOUT         : OUT std_ulogic_vector(7 DOWNTO 0); -- output data received via UART
DOUT_VLD     : OUT std_ulogic;      -- when DOUT_VLD = 1, output data (DOUT) are valid without
↪ errors (is assert only for one clock cycle)
FRAME_ERROR  : OUT std_ulogic;      -- when FRAME_ERROR = 1, stop bit was invalid (is assert only
↪ for one clock cycle)
PARITY_ERROR : OUT std_ulogic      -- when PARITY_ERROR = 1, parity bit was invalid (is assert
↪ only for one clock cycle)
);
END ENTITY;

ARCHITECTURE rtl OF serial_rx IS

    SIGNAL rx_clk_en          : std_ulogic;
    SIGNAL rx_data            : std_ulogic_vector(7 DOWNTO 0);
    SIGNAL rx_bit_count       : unsigned(2 DOWNTO 0);
    SIGNAL rx_parity_bit      : std_ulogic;
    SIGNAL rx_parity_error    : std_ulogic;
    SIGNAL rx_parity_check_en : std_ulogic;
    SIGNAL rx_done            : std_ulogic;
    SIGNAL fsm_idle           : std_ulogic;
    SIGNAL fsm_databits       : std_ulogic;
    SIGNAL fsm_stopbit        : std_ulogic;

    TYPE state IS (idle, startbit, databits, paritybit, stopbit);
    SIGNAL fsm_pstate : state;
    SIGNAL fsm_nstate : state;

BEGIN

    -----
    -- UART RECEIVER CLOCK DIVIDER AND CLOCK ENABLE FLAG
    -----

    rx_clk_divider_i : ENTITY work.UART_CLK_DIV
    GENERIC MAP (
        DIV_MAX_VAL => CLK_DIV_VAL,
        DIV_MARK_POS => 3
    )
    PORT MAP (
        CLK      => CLK,
        RST      => RST,
        CLEAR    => fsm_idle,
        ENABLE   => UART_CLK_EN,
        DIV_MARK => rx_clk_en
    );

    -----
    -- UART RECEIVER BIT COUNTER
    -----

    uart_rx_bit_counter_p : PROCESS (CLK)
    BEGIN
        IF (rising_edge(CLK)) THEN
            IF (RST = '1') THEN
                rx_bit_count <= (OTHERS => '0');
            ELSIF (rx_clk_en = '1' AND fsm_databits = '1') THEN
                IF (rx_bit_count = "111") THEN

```



```

        rx_bit_count <= (OTHERS => '0');
    ELSE
        rx_bit_count <= rx_bit_count + 1;
    END IF;
END IF;
END IF;
END IF;
END PROCESS;

-----

-- UART RECEIVER DATA SHIFT REGISTER
-----

uart_rx_data_shift_reg_p : PROCESS (CLK)
BEGIN
    IF (rising_edge(CLK)) THEN
        IF (rx_clk_en = '1' AND fsm_databits = '1') THEN
            rx_data <= UART_RXD & rx_data(7 DOWNT0 1);
        END IF;
    END IF;
END PROCESS;

DOUT <= rx_data;

-----

-- UART RECEIVER PARITY GENERATOR AND CHECK
-----

uart_rx_parity_g : IF (PARITY_BIT /= "none") GENERATE
    uart_rx_parity_gen_i : ENTITY work.UART_PARITY
        GENERIC MAP (
            DATA_WIDTH => 8,
            PARITY_TYPE => PARITY_BIT
        )
        PORT MAP (
            DATA_IN => rx_data,
            PARITY_OUT => rx_parity_bit
        );

    uart_rx_parity_check_reg_p : PROCESS (CLK)
    BEGIN
        IF (rising_edge(CLK)) THEN
            IF (rx_clk_en = '1') THEN
                rx_parity_error <= rx_parity_bit XOR UART_RXD;
            END IF;
        END IF;
    END PROCESS;
END GENERATE;

uart_rx_noparity_g : IF (PARITY_BIT = "none") GENERATE
    rx_parity_error <= '0';
END GENERATE;

-----

-- UART RECEIVER OUTPUT REGISTER
-----

rx_done <= rx_clk_en AND fsm_stopbit;

uart_rx_output_reg_p : PROCESS (CLK)
BEGIN
    IF (rising_edge(CLK)) THEN
        IF (RST = '1') THEN

```

```

DOUT_VLD      <= '0';
FRAME_ERROR   <= '0';
PARITY_ERROR  <= '0';
ELSE
  DOUT_VLD      <= rx_done AND NOT rx_parity_error AND UART_RXD;
  FRAME_ERROR   <= rx_done AND NOT UART_RXD;
  PARITY_ERROR  <= rx_done AND rx_parity_error;
END IF;
END IF;
END PROCESS;

```

```

-- -----
--  UART RECEIVER FSM
-- -----

```

```

-- PRESENT STATE REGISTER

```

```

PROCESS (CLK)
BEGIN
  IF (rising_edge(CLK)) THEN
    IF (RST = '1') THEN
      fsm_pstate <= idle;
    ELSE
      fsm_pstate <= fsm_nstate;
    END IF;
  END IF;
END PROCESS;

```

```

-- NEXT STATE AND OUTPUTS LOGIC

```

```

PROCESS (fsm_pstate, UART_RXD, rx_clk_en, rx_bit_count)
BEGIN
  CASE fsm_pstate IS

    WHEN idle =>
      fsm_stopbit <= '0';
      fsm_databits <= '0';
      fsm_idle     <= '1';

      IF (UART_RXD = '0') THEN
        fsm_nstate <= startbit;
      ELSE
        fsm_nstate <= idle;
      END IF;

    WHEN startbit =>
      fsm_stopbit <= '0';
      fsm_databits <= '0';
      fsm_idle     <= '0';

      IF (rx_clk_en = '1') THEN
        fsm_nstate <= databits;
      ELSE
        fsm_nstate <= startbit;
      END IF;

    WHEN databits =>
      fsm_stopbit <= '0';
      fsm_databits <= '1';
      fsm_idle     <= '0';

      IF ((rx_clk_en = '1') AND (rx_bit_count = "111")) THEN
        IF (PARITY_BIT = "none") THEN
          fsm_nstate <= stopbit;

```

```

        ELSE
            fsm_nstate <= paritybit;
        END IF;
    ELSE
        fsm_nstate <= databits;
    END IF;

    WHEN paritybit =>
        fsm_stopbit <= '0';
        fsm_databits <= '0';
        fsm_idle <= '0';

        IF (rx_clk_en = '1') THEN
            fsm_nstate <= stopbit;
        ELSE
            fsm_nstate <= paritybit;
        END IF;

    WHEN stopbit =>
        fsm_stopbit <= '1';
        fsm_databits <= '0';
        fsm_idle <= '0';

        IF (rx_clk_en = '1') THEN
            fsm_nstate <= idle;
        ELSE
            fsm_nstate <= stopbit;
        END IF;

    WHEN OTHERS =>
        fsm_stopbit <= '0';
        fsm_databits <= '0';
        fsm_idle <= '0';
        fsm_nstate <= idle;

    END CASE;
END PROCESS;

```

END ARCHITECTURE;

serial:

```

-----
-- Module      : serial_tx
-----
-- modified by: Johann Faerber
-----
--              modified according to our design rules:
--              using std_ulogic instead of std_logic
-----
-- PROJECT: SIMPLE UART FOR FPGA
-----
-- AUTHORS: Jakub Cabal <jakubcabal@gmail.com>
-- LICENSE: The MIT License, please read LICENSE file
-- WEBSITE: https://github.com/jakubcabal/uart-for-fpga
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

```

```

USE IEEE.NUMERIC_STD.ALL;

ENTITY UART_TX IS
  GENERIC (
    CLK_DIV_VAL : integer := 16;
    PARITY_BIT  : string  := "none" -- type of parity: "none", "even", "odd", "mark", "space"
  );
  PORT (
    CLK      : IN std_ulogic;      -- system clock
    RST      : IN std_ulogic;      -- high active synchronous reset
    -- UART INTERFACE
    UART_CLK_EN : IN std_ulogic;    -- oversampling (16x) UART clock enable
    UART_TXD    : OUT std_ulogic;   -- serial transmit data
    -- USER DATA INPUT INTERFACE
    DIN         : IN std_ulogic_vector(7 DOWNTO 0); -- input data to be transmitted over UART
    DIN_VLD     : IN std_ulogic;    -- when DIN_VLD = 1, input data (DIN) are valid
    DIN_RDY     : OUT std_ulogic -- when DIN_RDY = 1, transmitter is ready and valid input data
    ↪ will be accepted for transmitting
  );
END ENTITY;

ARCHITECTURE RTL OF UART_TX IS

  SIGNAL tx_clk_en      : std_ulogic;
  SIGNAL tx_clk_div_clr : std_ulogic;
  SIGNAL tx_data        : std_ulogic_vector(7 DOWNTO 0);
  SIGNAL tx_bit_count   : unsigned(2 DOWNTO 0);
  SIGNAL tx_bit_count_en : std_ulogic;
  SIGNAL tx_ready       : std_ulogic;
  SIGNAL tx_parity_bit  : std_ulogic;
  SIGNAL tx_data_out_sel : std_ulogic_vector(1 DOWNTO 0);

  TYPE state IS (idle, txsync, startbit, databits, paritybit, stopbit);
  SIGNAL tx_pstate : state;
  SIGNAL tx_nstate : state;

BEGIN

  DIN_RDY <= tx_ready;

  -- -----
  -- UART TRANSMITTER CLOCK DIVIDER AND CLOCK ENABLE FLAG
  -- -----

  tx_clk_divider_i : ENTITY work.UART_CLK_DIV
    GENERIC MAP(
      DIV_MAX_VAL => CLK_DIV_VAL,
      DIV_MARK_POS => 1
    )
    PORT MAP (
      CLK      => CLK,
      RST      => RST,
      CLEAR    => tx_clk_div_clr,
      ENABLE   => UART_CLK_EN,
      DIV_MARK => tx_clk_en
    );

  -- -----
  -- UART TRANSMITTER INPUT DATA REGISTER
  -- -----

  uart_tx_input_data_reg_p : PROCESS (CLK)

```

```

BEGIN
    IF (rising_edge(CLK)) THEN
        IF (DIN_VLD = '1' AND tx_ready = '1') THEN
            tx_data <= DIN;
        END IF;
    END IF;
END PROCESS;

-----

-- UART TRANSMITTER BIT COUNTER
-----

uart_tx_bit_counter_p : PROCESS (CLK)
BEGIN
    IF (rising_edge(CLK)) THEN
        IF (RST = '1') THEN
            tx_bit_count <= (OTHERS => '0');
        ELSIF (tx_bit_count_en = '1' AND tx_clk_en = '1') THEN
            IF (tx_bit_count = "111") THEN
                tx_bit_count <= (OTHERS => '0');
            ELSE
                tx_bit_count <= tx_bit_count + 1;
            END IF;
        END IF;
    END IF;
END PROCESS;

-----

-- UART TRANSMITTER PARITY GENERATOR
-----

uart_tx_parity_g : IF (PARITY_BIT /= "none") GENERATE
    uart_tx_parity_gen_i : ENTITY work.UART_PARITY
        GENERIC MAP (
            DATA_WIDTH => 8,
            PARITY_TYPE => PARITY_BIT
        )
        PORT MAP (
            DATA_IN => tx_data,
            PARITY_OUT => tx_parity_bit
        );
    END GENERATE;

uart_tx_noparity_g : IF (PARITY_BIT = "none") GENERATE
    tx_parity_bit <= '0';
END GENERATE;

-----

-- UART TRANSMITTER OUTPUT DATA REGISTER
-----

uart_tx_output_data_reg_p : PROCESS (CLK)
BEGIN
    IF (rising_edge(CLK)) THEN
        IF (RST = '1') THEN
            UART_TXD <= '1';
        ELSE
            CASE tx_data_out_sel IS
                WHEN "01" => -- START BIT
                    UART_TXD <= '0';
                WHEN "10" => -- DATA BITS
                    UART_TXD <= tx_data(to_integer(tx_bit_count));
            END CASE;
        END IF;
    END IF;
END PROCESS;

```

```

        WHEN "11" =>                                -- PARITY BIT
            UART_TXD <= tx_parity_bit;
        WHEN OTHERS =>                                -- STOP BIT OR IDLE
            UART_TXD <= '1';
    END CASE;
END IF;
END IF;
END PROCESS;

```

```

-----
-- UART TRANSMITTER FSM
-----

```

```

-- PRESENT STATE REGISTER

```

```

PROCESS (CLK)
BEGIN
    IF (rising_edge(CLK)) THEN
        IF (RST = '1') THEN
            tx_pstate <= idle;
        ELSE
            tx_pstate <= tx_nstate;
        END IF;
    END IF;
END PROCESS;

```

```

-- NEXT STATE AND OUTPUTS LOGIC

```

```

PROCESS (tx_pstate, DIN_VLD, tx_clk_en, tx_bit_count)
BEGIN

```

```

    CASE tx_pstate IS

```

```

        WHEN idle =>
            tx_ready      <= '1';
            tx_data_out_sel <= "00";
            tx_bit_count_en <= '0';
            tx_clk_div_clr <= '1';

```

```

        IF (DIN_VLD = '1') THEN
            tx_nstate <= txsync;
        ELSE
            tx_nstate <= idle;
        END IF;

```

```

        WHEN txsync =>
            tx_ready      <= '0';
            tx_data_out_sel <= "00";
            tx_bit_count_en <= '0';
            tx_clk_div_clr <= '0';

```

```

        IF (tx_clk_en = '1') THEN
            tx_nstate <= startbit;
        ELSE
            tx_nstate <= txsync;
        END IF;

```

```

        WHEN startbit =>
            tx_ready      <= '0';
            tx_data_out_sel <= "01";
            tx_bit_count_en <= '0';
            tx_clk_div_clr <= '0';

```

```

        IF (tx_clk_en = '1') THEN

```

```

        tx_nstate <= databits;
    ELSE
        tx_nstate <= startbit;
    END IF;

    WHEN databits =>
        tx_ready      <= '0';
        tx_data_out_sel <= "10";
        tx_bit_count_en <= '1';
        tx_clk_div_clr <= '0';

        IF ((tx_clk_en = '1') AND (tx_bit_count = "111")) THEN
            IF (PARITY_BIT = "none") THEN
                tx_nstate <= stopbit;
            ELSE
                tx_nstate <= paritybit;
            END IF;
        ELSE
            tx_nstate <= databits;
        END IF;

    WHEN paritybit =>
        tx_ready      <= '0';
        tx_data_out_sel <= "11";
        tx_bit_count_en <= '0';
        tx_clk_div_clr <= '0';

        IF (tx_clk_en = '1') THEN
            tx_nstate <= stopbit;
        ELSE
            tx_nstate <= paritybit;
        END IF;

    WHEN stopbit =>
        tx_ready      <= '1';
        tx_data_out_sel <= "00";
        tx_bit_count_en <= '0';
        tx_clk_div_clr <= '0';

        IF (DIN_VLD = '1') THEN
            tx_nstate <= txsync;
        ELSIF (tx_clk_en = '1') THEN
            tx_nstate <= idle;
        ELSE
            tx_nstate <= stopbit;
        END IF;

    WHEN OTHERS =>
        tx_ready      <= '0';
        tx_data_out_sel <= "00";
        tx_bit_count_en <= '0';
        tx_clk_div_clr <= '0';
        tx_nstate      <= idle;

    END CASE;
END PROCESS;

END ARCHITECTURE;

```

serial:

```

-----
-- Module      : serial_rx
-----
-- modified by: Johann Faerber
-----
--              modified according to our design rules:
--              using std_ulogic instead of std_logic
-----

-- PROJECT: SIMPLE UART FOR FPGA
-----

-- AUTHORS: Jakub Cabal <jakubcabal@gmail.com>
-- LICENSE: The MIT License, please read LICENSE file
-- WEBSITE: https://github.com/jakubcabal/uart-for-fpga
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;
USE IEEE.MATH_REAL.ALL;

ENTITY UART_CLK_DIV IS
  GENERIC (
    DIV_MAX_VAL  : integer := 16;
    DIV_MARK_POS : integer := 1
  );
  PORT (
    CLK      : IN  std_ulogic;      -- system clock
    RST      : IN  std_ulogic;      -- high active synchronous reset
    -- USER INTERFACE
    CLEAR    : IN  std_ulogic;      -- clock divider counter clear
    ENABLE   : IN  std_ulogic;      -- clock divider counter enable
    DIV_MARK : OUT std_ulogic -- output divider mark (divided clock enable)
  );
END ENTITY;

ARCHITECTURE RTL OF UART_CLK_DIV IS

  CONSTANT CLK_DIV_WIDTH : integer := integer(ceil(log2(real(DIV_MAX_VAL))));

  SIGNAL clk_div_cnt      : unsigned(CLK_DIV_WIDTH-1 DOWNTO 0);
  SIGNAL clk_div_cnt_mark : std_ulogic;

BEGIN

  clk_div_cnt_p : PROCESS (CLK)
  BEGIN
    IF (rising_edge(CLK)) THEN
      IF (CLEAR = '1') THEN
        clk_div_cnt <= (OTHERS => '0');
      ELSIF (ENABLE = '1') THEN
        IF (clk_div_cnt = DIV_MAX_VAL-1) THEN
          clk_div_cnt <= (OTHERS => '0');
        ELSE
          clk_div_cnt <= clk_div_cnt + 1;
        END IF;
      END IF;
    END IF;
  END IF;
END PROCESS;

clk_div_cnt_mark <= '1' WHEN (clk_div_cnt = DIV_MARK_POS) ELSE '0';

```



```

div_mark_p : PROCESS (CLK)
BEGIN
    IF (rising_edge(CLK)) THEN
        DIV_MARK <= ENABLE AND clk_div_cnt_mark;
    END IF;
END PROCESS;

END ARCHITECTURE;

```

serial:

```

-----
-- Module      : UART_PARITY
-----
-- modified by: Johann Faerber
-----
--              modified according to our design rules:
--              using std_ulogic instead of std_logic
-----
-- PROJECT: SIMPLE UART FOR FPGA
-----
-- AUTHORS: Jakub Cabal <jakubcabal@gmail.com>
-- LICENSE: The MIT License, please read LICENSE file
-- WEBSITE: https://github.com/jakubcabal/uart-for-fpga
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;

ENTITY UART_PARITY IS
    GENERIC (
        DATA_WIDTH : integer := 8;
        PARITY_TYPE  : string  := "none" -- legal values: "none", "even", "odd", "mark", "space"
    );
    PORT (
        DATA_IN      : IN  std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
        PARITY_OUT    : OUT std_ulogic
    );
END ENTITY;

ARCHITECTURE RTL OF UART_PARITY IS

BEGIN

    -----
    -- PARITY BIT GENERATOR
    -----

    even_parity_g : IF (PARITY_TYPE = "even") GENERATE
        PROCESS (DATA_IN)
            VARIABLE parity_temp : std_ulogic;
        BEGIN
            parity_temp := '0';
            FOR i IN DATA_IN'range LOOP
                parity_temp := parity_temp XOR DATA_IN(i);
            END LOOP;
            PARITY_OUT <= parity_temp;
        END PROCESS;
    END GENERATE;

```

```

END GENERATE;

odd_parity_g : IF (PARITY_TYPE = "odd") GENERATE
PROCESS (DATA_IN)
    VARIABLE parity_temp : std_ulogic;
BEGIN
    parity_temp := '1';
    FOR i IN DATA_IN'range LOOP
        parity_temp := parity_temp XOR DATA_IN(i);
    END LOOP;
    PARITY_OUT <= parity_temp;
END PROCESS;
END GENERATE;

mark_parity_g : IF (PARITY_TYPE = "mark") GENERATE
    PARITY_OUT <= '1';
END GENERATE;

space_parity_g : IF (PARITY_TYPE = "space") GENERATE
    PARITY_OUT <= '0';
END GENERATE;

END ARCHITECTURE;

```

serial:

```

-- Description: takes information on the address and the data externally (serial reciever),
-- to then store to registers.
-- In the scope of the project, this then gets sent to the register file to be
-- processed from there.

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity serial_receiver_reg is
    port (
        rst_ni : in std_ulogic;
        clk_i : in std_ulogic;
        en_addr_reg_i : in std_ulogic;
        en_data_reg_i : in std_ulogic;
        rxd_data_i : in std_ulogic_vector(7 downto 0); -- uart data
        regfile_addr_o : out std_ulogic_vector(3 downto 0);
        regfile_data_o : out std_ulogic_vector(7 downto 0)
    );
end entity serial_receiver_reg;

architecture rtl of serial_receiver_reg is

begin

    addr_register : regfile_addr_o <= (others => '0') WHEN rst_ni = '0' ELSE
        std_ulogic_vector(resize(unsigned(rxd_data_i), 4)) WHEN rising_edge(clk_i) AND (en_addr_reg_i
        ⇨ = '1'); -- slices the four most significant bits off of the address

    data_register : regfile_data_o <= (others => '0') WHEN rst_ni = '0' ELSE
        rxd_data_i WHEN rising_edge(clk_i) AND (en_data_reg_i = '1');

```

```
end architecture rtl;
```

serial:

```
-- This file was generated by
-- Qfsm Version 0.55
-- (C) Stefan Duffner, Rainer Strobel, Aaron Erhardt

-- Inputs:  rxd_rec  addr[3]  addr[2]  addr[1]  addr[0]  pm_checked
-- State/Output      en_addr_reg en_data_reg en_regfile_wr pm_control_changed
-- wait_for_addr_s      0          0          0          0
-- fetch_addr_s          1          0          0          0
-- wait_for_data_s      0          0          0          0
-- fetch_data_s          0          1          0          0
-- write_regfile_s      0          0          1          0
-- check_written_addr_s  0          0          0          0
-- pattern_control_changed_s  0          0          0          1
-- wait_cycle_s          0          0          0          0
-- wait_for_sync_reset_serialrx_s  0          0          0          0
-- wait_for_sync_reset_serialrx2_s 0          0          0          0

LIBRARY IEEE;

USE IEEE.std_logic_1164.ALL;

ENTITY serial_receiver_fsm IS
  PORT (clk: IN std_ulogic;
        rst_n: IN std_ulogic;
        rxd_rec: IN std_ulogic;
        addr: IN std_ulogic_vector(3 DOWNTO 0);
        pm_checked: IN std_ulogic;
        en_addr_reg: OUT std_ulogic;
        en_data_reg: OUT std_ulogic;
        en_regfile_wr: OUT std_ulogic;
        pm_control_changed: OUT std_ulogic);
END serial_receiver_fsm;

ARCHITECTURE behave OF serial_receiver_fsm IS

  TYPE state_type IS (wait_for_addr_s, fetch_addr_s, wait_for_data_s, fetch_data_s, write_regfile_s,
    ⇨ check_written_addr_s, pattern_control_changed_s, wait_cycle_s,
    ⇨ wait_for_sync_reset_serialrx_s, wait_for_sync_reset_serialrx2_s);
  SIGNAL next_state, current_state : state_type;

BEGIN
  state_register: PROCESS (rst_n, clk)
  BEGIN
    IF rst_n='0' THEN
      current_state <= wait_for_sync_reset_serialrx_s;
    ELSIF rising_edge(clk) THEN
      current_state <= next_state;
    END IF;
  END PROCESS;

  next_state_and_output_logic: PROCESS (current_state, rxd_rec, addr(3 DOWNTO 0), pm_checked)
    VARIABLE temp_input : std_ulogic_vector(5 DOWNTO 0);
    VARIABLE temp_output : std_ulogic_vector(3 DOWNTO 0);
  BEGIN
```

temp_input="011001" or
temp_input="010011" or

```

    next_state <= wait_for_data_s;
ELSIF temp_input="100000" or temp_input="110000" or temp_input="101000" or
↪ temp_input="100100" or temp_input="100010" or temp_input="100001" or
↪ temp_input="111000" or temp_input="110100" or temp_input="110010" or
↪ temp_input="110001" or temp_input="101100" or temp_input="101010" or
↪ temp_input="101001" or temp_input="100110" or temp_input="100101" or
↪ temp_input="100011" or temp_input="111100" or temp_input="111010" or
↪ temp_input="111001" or temp_input="110110" or temp_input="110101" or
↪ temp_input="110011" or temp_input="101110" or temp_input="101101" or
↪ temp_input="101011" or temp_input="100111" or temp_input="111110" or
↪ temp_input="111101" or temp_input="111011" or temp_input="110111" or
↪ temp_input="101111" or temp_input="111111" THEN
    next_state <= fetch_data_s;
ELSE
    next_state <= current_state;
END IF;
WHEN fetch_data_s => temp_output := "0100";
IF temp_input="100000" or temp_input="110000" or temp_input="101000" or
↪ temp_input="100100" or temp_input="100010" or temp_input="100001" or
↪ temp_input="111000" or temp_input="110100" or temp_input="110010" or
↪ temp_input="110001" or temp_input="101100" or temp_input="101010" or
↪ temp_input="101001" or temp_input="100110" or temp_input="100101" or
↪ temp_input="100011" or temp_input="111100" or temp_input="111010" or
↪ temp_input="111001" or temp_input="110110" or temp_input="110101" or
↪ temp_input="110011" or temp_input="101110" or temp_input="101101" or
↪ temp_input="101011" or temp_input="100111" or temp_input="111110" or
↪ temp_input="111101" or temp_input="111011" or temp_input="110111" or
↪ temp_input="101111" or temp_input="111111" THEN
    next_state <= fetch_data_s;
ELSIF temp_input="000000" or temp_input="010000" or temp_input="001000" or
↪ temp_input="000100" or temp_input="000010" or temp_input="000001" or
↪ temp_input="011000" or temp_input="010100" or temp_input="010010" or
↪ temp_input="010001" or temp_input="001100" or temp_input="001010" or
↪ temp_input="001001" or temp_input="000110" or temp_input="000101" or
↪ temp_input="000011" or temp_input="011100" or temp_input="011010" or
↪ temp_input="011001" or temp_input="010110" or temp_input="010101" or
↪ temp_input="010011" or temp_input="001110" or temp_input="001101" or
↪ temp_input="001011" or temp_input="000111" or temp_input="001110" or
↪ temp_input="001101" or temp_input="011011" or temp_input="010111" or
↪ temp_input="001111" or temp_input="011111" THEN
    next_state <= write_regfile_s;
ELSE
    next_state <= current_state;
END IF;
WHEN write_regfile_s => temp_output := "0010";
    next_state <= check_written_addr_s;
WHEN check_written_addr_s => temp_output := "0000";
IF temp_input="011110" or temp_input="111110" or temp_input="011111" or
↪ temp_input="111111" THEN
    next_state <= pattern_control_changed_s;
ELSE
    next_state <= wait_for_addr_s;
END IF;
WHEN pattern_control_changed_s => temp_output := "0001";
IF temp_input="000000" or temp_input="100000" or temp_input="010000" or
↪ temp_input="001000" or temp_input="000100" or temp_input="000010" or
↪ temp_input="110000" or temp_input="101000" or temp_input="100100" or
↪ temp_input="100010" or temp_input="011000" or temp_input="010100" or
↪ temp_input="010010" or temp_input="001100" or temp_input="001010" or
↪ temp_input="000110" or temp_input="111000" or temp_input="110100" or
↪ temp_input="110010" or temp_input="101100" or temp_input="101010" or
↪ temp_input="100110" or temp_input="011100" or temp_input="011010" or
↪ temp_input="010110" or temp_input="001110" or temp_input="111100" or
↪ temp_input="111010" or temp_input="110110" or temp_input="101110" or
↪ temp_input="011110" or temp_input="111110" THEN

```

```

    next_state <= pattern_control_changed_s;
ELSIF temp_input="000001" or temp_input="100001" or temp_input="010001" or
↪ temp_input="001001" or temp_input="000101" or temp_input="000011" or
↪ temp_input="110001" or temp_input="101001" or temp_input="100101" or
↪ temp_input="100011" or temp_input="011001" or temp_input="010101" or
↪ temp_input="010011" or temp_input="001101" or temp_input="001011" or
↪ temp_input="000111" or temp_input="111001" or temp_input="110101" or
↪ temp_input="110011" or temp_input="101101" or temp_input="101011" or
↪ temp_input="100111" or temp_input="011101" or temp_input="011011" or
↪ temp_input="010111" or temp_input="001111" or temp_input="111101" or
↪ temp_input="111011" or temp_input="110111" or temp_input="101111" or
↪ temp_input="011111" or temp_input="111111" THEN
    next_state <= wait_cycle_s;
ELSE
    next_state <= current_state;
END IF;
WHEN wait_cycle_s => temp_output := "0000";
    next_state <= wait_for_addr_s;
WHEN wait_for_sync_reset_serialrx_s => temp_output := "0000";
    IF temp_input="000000" or temp_input="010000" or temp_input="001000" or
↪ temp_input="000100" or temp_input="000010" or temp_input="000001" or
↪ temp_input="011000" or temp_input="010100" or temp_input="010010" or
↪ temp_input="010001" or temp_input="001100" or temp_input="001010" or
↪ temp_input="001001" or temp_input="000110" or temp_input="000101" or
↪ temp_input="000011" or temp_input="011100" or temp_input="011010" or
↪ temp_input="011001" or temp_input="010110" or temp_input="010101" or
↪ temp_input="010011" or temp_input="001110" or temp_input="001101" or
↪ temp_input="001011" or temp_input="000111" or temp_input="011110" or
↪ temp_input="011101" or temp_input="011011" or temp_input="010111" or
↪ temp_input="001111" or temp_input="011111" THEN
        next_state <= wait_for_sync_reset_serialrx_s;
    ELSIF temp_input="100000" or temp_input="110000" or temp_input="101000" or
↪ temp_input="100100" or temp_input="100010" or temp_input="100001" or
↪ temp_input="111000" or temp_input="110100" or temp_input="110010" or
↪ temp_input="110001" or temp_input="101100" or temp_input="101010" or
↪ temp_input="101001" or temp_input="100110" or temp_input="100101" or
↪ temp_input="100011" or temp_input="111100" or temp_input="111010" or
↪ temp_input="111001" or temp_input="110110" or temp_input="110101" or
↪ temp_input="110011" or temp_input="101110" or temp_input="101101" or
↪ temp_input="101011" or temp_input="100111" or temp_input="111110" or
↪ temp_input="111101" or temp_input="111011" or temp_input="110111" or
↪ temp_input="101111" or temp_input="111111" THEN
        next_state <= wait_for_sync_reset_serialrx2_s;
    ELSE
        next_state <= current_state;
    END IF;
WHEN wait_for_sync_reset_serialrx2_s => temp_output := "0000";
    IF temp_input="100000" or temp_input="110000" or temp_input="101000" or
↪ temp_input="100100" or temp_input="100010" or temp_input="100001" or
↪ temp_input="111000" or temp_input="110100" or temp_input="110010" or
↪ temp_input="110001" or temp_input="101100" or temp_input="101010" or
↪ temp_input="101001" or temp_input="100110" or temp_input="100101" or
↪ temp_input="100011" or temp_input="111100" or temp_input="111010" or
↪ temp_input="111001" or temp_input="110110" or temp_input="110101" or
↪ temp_input="110011" or temp_input="101110" or temp_input="101101" or
↪ temp_input="101011" or temp_input="100111" or temp_input="111110" or
↪ temp_input="111101" or temp_input="111011" or temp_input="110111" or
↪ temp_input="101111" or temp_input="111111" THEN
        next_state <= wait_for_sync_reset_serialrx2_s;
    ELSIF temp_input="000000" or temp_input="010000" or temp_input="001000" or
↪ temp_input="000100" or temp_input="000010" or temp_input="000001" or
↪ temp_input="011000" or temp_input="010100" or temp_input="010010" or
↪ temp_input="010001" or temp_input="001100" or temp_input="001010" or
↪ temp_input="001001" or temp_input="000110" or temp_input="000101" or
↪ temp_input="000011" or temp_input="011100" or temp_input="011010" or
↪ temp_input="011001" or temp_input="010110" or temp_input="010101" or
↪ temp_input="010011" or temp_input="001110" or temp_input="001101" or
↪ temp_input="001011" or temp_input="000111" or temp_input="011110" or
↪ temp_input="011101" or temp_input="011011" or temp_input="010111" or
↪ temp_input="001111" or temp_input="011111"

```

```

        next_state <= wait_for_addr_s;
    ELSE
        next_state <= current_state;
    END IF;
    WHEN OTHERS => temp_output := (OTHERS => 'X');
    next_state <= wait_for_addr_s;
END CASE;
en_addr_reg <= temp_output(3);
en_data_reg <= temp_output(2);
en_regfile_wr <= temp_output(1);
pm_control_changed <= temp_output(0);
END PROCESS;

END behave;

```

pattern:

```

-- Description: Functions by taking in data from the register file, to then output the data in
-- a serial binary form.
-- the pattern memory is stored in ssram.
-- takes data in to switch between stop, single burst of the data, continuous stream/repition
-- or to load new data into the pattern generator.

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
-- use IEEE.numeric_std.all;

ENTITY pattern_generator IS
    PORT (
        en_write_pm : IN std_ulogic;
        clk_i       : IN std_ulogic;
        pm_control_i : IN std_ulogic_vector(1 downto 0); -- only the control bits are needed (not bit
        ↪ 2)
        addr_cnt_i   : IN std_ulogic_vector(7 downto 0);
        rxd_data_i   : IN std_ulogic_vector(7 DOWNTO 0); -- uart data
        pattern_o    : OUT std_ulogic_vector(7 DOWNTO 0)
    );
END ENTITY pattern_generator;

ARCHITECTURE structure OF pattern_generator IS

    COMPONENT sp_ssram IS
        GENERIC (
            addr_width : positive; -- a number > 0
            data_width  : positive);
        PORT (
            clk_i : IN std_ulogic;
            we_i  : IN std_ulogic;
            addr_i : IN std_ulogic_vector;
            d_i    : IN std_ulogic_vector;
            q_o    : OUT std_ulogic_vector);
    END COMPONENT sp_ssram;

    CONSTANT addr_width : natural := 8;
    CONSTANT data_width  : natural := 8;

    SIGNAL pm_out      : std_ulogic_vector(data_width - 1 DOWNTO 0);
    SIGNAL pattern_temp : std_ulogic_vector(data_width - 1 DOWNTO 0);

BEGIN

```

```

pattern_memory : sp_ssram
  GENERIC MAP (
    addr_width => addr_width,
    data_width => data_width)
  PORT MAP (
    clk_i  => clk_i,
    we_i   => en_write_pm,
    addr_i => addr_cnt_i,
    d_i    => rxd_data_i,
    q_o    => pm_out);

  WITH pm_control_i SELECT
    pattern_temp <= (OTHERS => '0') WHEN "00", -- stop
    pm_out       WHEN "01", -- single burst
    pm_out       WHEN "10", -- continuous burst
    (OTHERS      => '0') WHEN "11", -- load
    (OTHERS      => '0') WHEN OTHERS;

  output_register : pattern_o <= pattern_temp WHEN rising_edge(clk_i);

END ARCHITECTURE structure;

```

pattern:

```

-----
-- Module      : sp_ssram
-----
-- Author      : Johann Faerber
-- Company     : University of Applied Sciences Augsburg
-----
-- Description: Synchronous Single-Port SRAM
--
--
-----
-- Revisions   : see end of file
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY sp_ssram IS
  GENERIC (
    addr_width : positive := 8;
    data_width : positive := 8);
  PORT (
    clk_i : IN  std_ulogic;
    we_i  : IN  std_ulogic;
    addr_i : IN  std_ulogic_vector;
    d_i    : IN  std_ulogic_vector;
    q_o    : OUT std_ulogic_vector
  );
END;

ARCHITECTURE rtl OF sp_ssram IS
  TYPE ram_t IS ARRAY(0 TO 2 ** addr_width - 1) OF std_ulogic_vector(data_width-1 DOWNTO 0);
  SIGNAL ram : ram_t;

```



```

BEGIN

mem_p : PROCESS(clk_i)
BEGIN
  IF rising_edge(clk_i) THEN
    IF we_i = '1' THEN
      ram(to_integer(unsigned(addr_i))) <= d_i;
    END IF;
    q_o <= ram(to_integer(unsigned(addr_i)));
  END IF;
END PROCESS mem_p;

END;

```

pattern:

```

-- This file was generated by
-- Qfsm Version 0.55
-- (C) Stefan Duffner, Rainer Strobel, Aaron Erhardt

-- Inputs:  rxd_rec  tc_pm  pm_control_changed  pm_control[1]  pm_control[0]
-- ↪ addr_cnt_enabled
-- State/Output      en_pm en_pm_cnt clr_pm_cnt pm_checked pattern_valid
-- wait_for_pm_change  0    0          0          0          0
-- clr_wait_addr_cnt   0    0          1          0          0
-- wait_for_pm_data    0    0          0          0          0
-- fetch_pm_data       1    0          0          0          0
-- cnt_addr_up_serialmode 0    1          0          0          0
-- check_addr_end      0    0          0          0          0
-- pm_is_checked       0    0          0          1          0
-- cnt_addr_up_cntmode  0    1          0          0          1
-- cnt_addr_free       0    1          0          0          1

LIBRARY IEEE;

USE IEEE.std_logic_1164.ALL;

ENTITY pattern_generator_fsm IS
  PORT (clk: IN std_ulogic;
        rst_n: IN std_ulogic;
        rxd_rec: IN std_ulogic;
        tc_pm: IN std_ulogic;
        pm_control_changed: IN std_ulogic;
        pm_control: IN std_ulogic_vector(1 DOWNTO 0);
        addr_cnt_enabled: IN std_ulogic;
        en_pm: OUT std_ulogic;
        en_pm_cnt: OUT std_ulogic;
        clr_pm_cnt: OUT std_ulogic;
        pm_checked: OUT std_ulogic;
        pattern_valid: OUT std_ulogic);
END pattern_generator_fsm;

ARCHITECTURE behave OF pattern_generator_fsm IS

  TYPE state_type IS (wait_for_pm_change, clr_wait_addr_cnt, wait_for_pm_data, fetch_pm_data,
    ↪ cnt_addr_up_serialmode, check_addr_end, pm_is_checked, cnt_addr_up_cntmode, cnt_addr_free);
  SIGNAL next_state, current_state : state_type;

BEGIN

```

```

state_register: PROCESS (rst_n, clk)
BEGIN
    IF rst_n='0' THEN
        current_state <= wait_for_pm_change;
    ELSIF rising_edge(clk) THEN
        current_state <= next_state;
    END IF;
END PROCESS;

next_state_and_output_logic: PROCESS (current_state, rxd_rec, tc_pm, pm_control_changed,
↪ pm_control(1 DOWNTO 0), addr_cnt_enabled)
    VARIABLE temp_input : std_ulogic_vector(5 DOWNTO 0);
    VARIABLE temp_output : std_ulogic_vector(4 DOWNTO 0);
BEGIN
    temp_input := rxd_rec & tc_pm & pm_control_changed & pm_control(1) & pm_control(0) &
↪ addr_cnt_enabled;
    CASE current_state IS
        WHEN wait_for_pm_change => temp_output := "00000";
            IF temp_input="001110" or temp_input="101110" or temp_input="011110" or
↪ temp_input="001111" or temp_input="111110" or temp_input="101111" or
↪ temp_input="011111" or temp_input="111111" THEN
                next_state <= wait_for_pm_data;
            ELSIF temp_input="001010" or temp_input="101010" or temp_input="011010" or
↪ temp_input="001011" or temp_input="111010" or temp_input="101011" or
↪ temp_input="011011" or temp_input="111011" or temp_input="001000" or
↪ temp_input="101000" or temp_input="011000" or temp_input="001001" or
↪ temp_input="111000" or temp_input="101001" or temp_input="011001" or
↪ temp_input="111001" or temp_input="001000" or temp_input="101000" or
↪ temp_input="011000" or temp_input="001001" or temp_input="111000" or
↪ temp_input="101001" or temp_input="011001" or temp_input="111001" THEN
                next_state <= pm_is_checked;
            ELSE
                next_state <= wait_for_pm_change;
            END IF;
        WHEN clr_wait_addr_cnt => temp_output := "00100";
            next_state <= wait_for_pm_change;
        WHEN wait_for_pm_data => temp_output := "00000";
            IF temp_input="100000" or temp_input="110000" or temp_input="101000" or
↪ temp_input="100100" or temp_input="100010" or temp_input="100001" or
↪ temp_input="111000" or temp_input="110100" or temp_input="110010" or
↪ temp_input="110001" or temp_input="101100" or temp_input="101010" or
↪ temp_input="101001" or temp_input="100110" or temp_input="100101" or
↪ temp_input="100011" or temp_input="111100" or temp_input="111010" or
↪ temp_input="111001" or temp_input="110110" or temp_input="110101" or
↪ temp_input="110011" or temp_input="101110" or temp_input="101101" or
↪ temp_input="101011" or temp_input="100111" or temp_input="111110" or
↪ temp_input="111101" or temp_input="111011" or temp_input="110111" or
↪ temp_input="101111" or temp_input="111111" THEN
                next_state <= fetch_pm_data;
            ELSIF temp_input="000000" or temp_input="010000" or temp_input="001000" or
↪ temp_input="000100" or temp_input="000010" or temp_input="000001" or
↪ temp_input="011000" or temp_input="010100" or temp_input="010010" or
↪ temp_input="010001" or temp_input="001100" or temp_input="001010" or
↪ temp_input="001001" or temp_input="000110" or temp_input="000101" or
↪ temp_input="000011" or temp_input="011100" or temp_input="011010" or
↪ temp_input="011001" or temp_input="010110" or temp_input="010101" or
↪ temp_input="010011" or temp_input="001110" or temp_input="001101" or
↪ temp_input="001011" or temp_input="000111" or temp_input="011110" or
↪ temp_input="011101" or temp_input="011011" or temp_input="010111" or
↪ temp_input="001111" or temp_input="011111" THEN
                next_state <= wait_for_pm_data;
            ELSE
                next_state <= current_state;
            END IF;
    END CASE;
END PROCESS;

```

```

END IF;
WHEN fetch_pm_data => temp_output := "10000";
IF temp_input="000000" or temp_input="010000" or temp_input="001000" or
↳ temp_input="000100" or temp_input="000010" or temp_input="000001" or
↳ temp_input="011000" or temp_input="010100" or temp_input="010010" or
↳ temp_input="010001" or temp_input="001100" or temp_input="001010" or
↳ temp_input="001001" or temp_input="000110" or temp_input="000101" or
↳ temp_input="000011" or temp_input="011100" or temp_input="011010" or
↳ temp_input="011001" or temp_input="010110" or temp_input="010101" or
↳ temp_input="010011" or temp_input="001110" or temp_input="001101" or
↳ temp_input="001011" or temp_input="000111" or temp_input="011110" or
↳ temp_input="011101" or temp_input="011011" or temp_input="010111" or
↳ temp_input="001111" or temp_input="011111" THEN
    next_state <= cnt_addr_up_serialmode;
ELSIF temp_input="100000" or temp_input="110000" or temp_input="101000" or
↳ temp_input="100100" or temp_input="100010" or temp_input="100001" or
↳ temp_input="111000" or temp_input="110100" or temp_input="110010" or
↳ temp_input="110001" or temp_input="101100" or temp_input="101010" or
↳ temp_input="101001" or temp_input="100110" or temp_input="100101" or
↳ temp_input="100011" or temp_input="111100" or temp_input="111010" or
↳ temp_input="111001" or temp_input="110110" or temp_input="110101" or
↳ temp_input="110011" or temp_input="101110" or temp_input="101101" or
↳ temp_input="101011" or temp_input="100111" or temp_input="111110" or
↳ temp_input="111101" or temp_input="111011" or temp_input="110111" or
↳ temp_input="101111" or temp_input="111111" THEN
    next_state <= fetch_pm_data;
ELSE
    next_state <= current_state;
END IF;
WHEN cnt_addr_up_serialmode => temp_output := "01000";
IF temp_input="000001" or temp_input="100001" or temp_input="010001" or
↳ temp_input="001001" or temp_input="000101" or temp_input="000011" or
↳ temp_input="110001" or temp_input="101001" or temp_input="100101" or
↳ temp_input="100011" or temp_input="011001" or temp_input="010101" or
↳ temp_input="010011" or temp_input="001101" or temp_input="001011" or
↳ temp_input="000111" or temp_input="111001" or temp_input="110101" or
↳ temp_input="110011" or temp_input="101101" or temp_input="101011" or
↳ temp_input="100111" or temp_input="011101" or temp_input="011011" or
↳ temp_input="010111" or temp_input="001111" or temp_input="111101" or
↳ temp_input="111011" or temp_input="110111" or temp_input="101111" or
↳ temp_input="011111" or temp_input="111111" THEN
    next_state <= check_addr_end;
ELSIF temp_input="000000" or temp_input="100000" or temp_input="010000" or
↳ temp_input="001000" or temp_input="000100" or temp_input="000010" or
↳ temp_input="110000" or temp_input="101000" or temp_input="100100" or
↳ temp_input="100010" or temp_input="011000" or temp_input="010100" or
↳ temp_input="010010" or temp_input="001100" or temp_input="001010" or
↳ temp_input="000110" or temp_input="111000" or temp_input="110100" or
↳ temp_input="110010" or temp_input="101100" or temp_input="101010" or
↳ temp_input="100110" or temp_input="011100" or temp_input="011010" or
↳ temp_input="010110" or temp_input="001110" or temp_input="111100" or
↳ temp_input="111010" or temp_input="110110" or temp_input="101110" or
↳ temp_input="011110" or temp_input="111110" THEN
    next_state <= cnt_addr_up_serialmode;
ELSE
    next_state <= current_state;
END IF;
WHEN check_addr_end => temp_output := "00000";
IF temp_input="010000" or temp_input="110000" or temp_input="011000" or
↳ temp_input="010100" or temp_input="010010" or temp_input="010001" or
↳ temp_input="111000" or temp_input="110100" or temp_input="110010" or
↳ temp_input="110001" or temp_input="011100" or temp_input="011010" or
↳ temp_input="011001" or temp_input="010110" or temp_input="010101" or
↳ temp_input="010011" or temp_input="111100" or temp_input="111010" or
↳ temp_input="111001" or temp_input="110110" or temp_input="110101" or
↳ temp_input="110011" or temp_input="011110" or temp_input="011101" or
↳ temp_input="111101" or temp_input="111011" or temp_input="110111" or
↳ temp_input="111111" or temp_input="111111" THEN
    next_state <= current_state;
ELSE
    next_state <= current_state;
END IF;

```

```

    next_state <= pm_is_checked;
ELSIF temp_input="000000" or temp_input="100000" or temp_input="001000" or
↪ temp_input="000100" or temp_input="000010" or temp_input="000001" or
↪ temp_input="101000" or temp_input="100100" or temp_input="100010" or
↪ temp_input="100001" or temp_input="001100" or temp_input="001010" or
↪ temp_input="001001" or temp_input="000110" or temp_input="000101" or
↪ temp_input="000011" or temp_input="101100" or temp_input="101010" or
↪ temp_input="101001" or temp_input="100110" or temp_input="100101" or
↪ temp_input="100011" or temp_input="001110" or temp_input="001101" or
↪ temp_input="001011" or temp_input="000111" or temp_input="101110" or
↪ temp_input="101101" or temp_input="101011" or temp_input="100111" or
↪ temp_input="001111" or temp_input="101111" THEN
    next_state <= wait_for_pm_data;
ELSE
    next_state <= current_state;
END IF;
WHEN pm_is_checked => temp_output := "00010";
IF temp_input="000110" or temp_input="100110" or temp_input="010110" or
↪ temp_input="001110" or temp_input="000111" or temp_input="110110" or
↪ temp_input="101110" or temp_input="100111" or temp_input="011110" or
↪ temp_input="010111" or temp_input="001111" or temp_input="111110" or
↪ temp_input="110111" or temp_input="101111" or temp_input="011111" or
↪ temp_input="111111" or temp_input="000000" or temp_input="100000" or
↪ temp_input="010000" or temp_input="001000" or temp_input="000001" or
↪ temp_input="110000" or temp_input="101000" or temp_input="100001" or
↪ temp_input="011000" or temp_input="010001" or temp_input="001001" or
↪ temp_input="111000" or temp_input="110001" or temp_input="101001" or
↪ temp_input="011001" or temp_input="111001" THEN
    next_state <= clr_wait_addr_cnt;
ELSIF temp_input="000100" or temp_input="100100" or temp_input="010100" or
↪ temp_input="001100" or temp_input="000101" or temp_input="110100" or
↪ temp_input="101100" or temp_input="100101" or temp_input="011100" or
↪ temp_input="010101" or temp_input="001101" or temp_input="111100" or
↪ temp_input="110101" or temp_input="101101" or temp_input="011101" or
↪ temp_input="111101" or temp_input="000010" or temp_input="100010" or
↪ temp_input="010010" or temp_input="001010" or temp_input="000011" or
↪ temp_input="110010" or temp_input="101010" or temp_input="100011" or
↪ temp_input="011010" or temp_input="010011" or temp_input="001011" or
↪ temp_input="111010" or temp_input="110011" or temp_input="101011" or
↪ temp_input="011011" or temp_input="111011" THEN
    next_state <= cnt_addr_up_cntmode;
ELSE
    next_state <= current_state;
END IF;
WHEN cnt_addr_up_cntmode => temp_output := "01001";
IF temp_input="000001" or temp_input="100001" or temp_input="010001" or
↪ temp_input="000101" or temp_input="000011" or temp_input="110001" or
↪ temp_input="100101" or temp_input="100011" or temp_input="010101" or
↪ temp_input="010011" or temp_input="000111" or temp_input="110101" or
↪ temp_input="110011" or temp_input="100111" or temp_input="010111" or
↪ temp_input="110111" THEN
    next_state <= cnt_addr_free;
ELSIF temp_input="001000" or temp_input="101000" or temp_input="011000" or
↪ temp_input="001100" or temp_input="001010" or temp_input="001001" or
↪ temp_input="111000" or temp_input="101100" or temp_input="101010" or
↪ temp_input="101001" or temp_input="011100" or temp_input="011010" or
↪ temp_input="001001" or temp_input="001110" or temp_input="001101" or
↪ temp_input="001011" or temp_input="111100" or temp_input="111010" or
↪ temp_input="111001" or temp_input="101110" or temp_input="101101" or
↪ temp_input="101011" or temp_input="011110" or temp_input="011101" or
↪ temp_input="011011" or temp_input="001111" or temp_input="111110" or
↪ temp_input="111101" or temp_input="111011" or temp_input="101111" or
↪ temp_input="011111" or temp_input="111111" THEN

```

```

        next_state <= clr_wait_addr_cnt;
    ELSE
        next_state <= cnt_addr_up_cntmode;
    END IF;
    WHEN cnt_addr_free => temp_output := "01001";
    IF temp_input="001000" or temp_input="101000" or temp_input="011000" or
    ↪ temp_input="001100" or temp_input="001010" or temp_input="001001" or
    ↪ temp_input="111000" or temp_input="101100" or temp_input="101010" or
    ↪ temp_input="101001" or temp_input="011100" or temp_input="011010" or
    ↪ temp_input="011001" or temp_input="001110" or temp_input="001101" or
    ↪ temp_input="001011" or temp_input="111100" or temp_input="111010" or
    ↪ temp_input="111001" or temp_input="101110" or temp_input="101101" or
    ↪ temp_input="101011" or temp_input="011110" or temp_input="011101" or
    ↪ temp_input="011011" or temp_input="001111" or temp_input="111110" or
    ↪ temp_input="111101" or temp_input="111011" or temp_input="101111" or
    ↪ temp_input="011111" or temp_input="111111" or temp_input="010010" or
    ↪ temp_input="110010" or temp_input="010011" or temp_input="110011" THEN
        next_state <= clr_wait_addr_cnt;
    ELSE
        next_state <= cnt_addr_free;
    END IF;
    WHEN OTHERS => temp_output := (OTHERS => 'X');
    next_state <= wait_for_pm_change;
END CASE;
en_pm <= temp_output(4);
en_pm_cnt <= temp_output(3);
clr_pm_cnt <= temp_output(2);
pm_checked <= temp_output(1);
pattern_valid <= temp_output(0);
END PROCESS;

END behave;

```

pattern:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;

entity cntup_addr is
    port (
        clk_i : in std_ulogic;
        clr_i : in std_ulogic; -- synchronous clear
        rst_ni : in std_ulogic; -- asynchronous reset
        en_pi : in std_ulogic;
        len_i : in std_ulogic_vector(7 downto 0);
        q_o : out std_ulogic_vector(7 downto 0);
        tc_o : out std_ulogic -- one at end of cycle
    );
end entity cntup_addr;

architecture rtl of cntup_addr is

    signal current_state : unsigned(7 downto 0);

begin

    cntup: process(clk_i, rst_ni, clr_i, en_pi)
    begin
        if rst_ni = '0' then
            current_state <= (others => '0');
        elsif rising_edge(clk_i) and en_pi = '1' then

```

```

        if current_state = unsigned(len_i) - 1 or clr_i = '1' then
            current_state <= (others => '0');
        else
            current_state <= current_state + 1;
        end if;
    end if;
end process cntup;

q_o <= std_ulogic_vector(current_state);
tc_o <= '1' when current_state = 0 else '0';

end architecture rtl;

```

noise generator:

-- Description: Allows for switching between a number of different bits for the lfsr. Choose the
 ↳ bitwidth and where the feedbacks are for the xor.

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

-- https://www.itu.int/rec/T-REC-O.150-199605-I/en
ENTITY config_noise_generator IS
    GENERIC (
        num_of_bits : positive := 4;           -- just a default value
        tap_high    : positive := 4;           -- xor connection 1
        tap_low     : positive := 3;           -- xor connection 2
    );
    PORT (
        en_pi : IN  std_ulogic;
        clk_i : IN  std_ulogic;
        rst_ni : IN  std_ulogic;
        prbs_o : OUT std_ulogic_vector(num_of_bits - 1 DOWNTO 0); --
        noise_o : OUT std_ulogic;
        eoc_o  : OUT std_ulogic
    );
END ENTITY config_noise_generator;

ARCHITECTURE rtl OF config_noise_generator IS

    SIGNAL q      : std_ulogic_vector(num_of_bits - 1 DOWNTO 0); -- current state
    SIGNAL d      : std_ulogic_vector(num_of_bits - 1 DOWNTO 0); -- next state
    CONSTANT init : std_ulogic_vector(num_of_bits - 1 DOWNTO 0) := (0 => '1', OTHERS => '0');

BEGIN
    -- lfsr with xor feedback; 0 lines are on the right of the shift register, highest on the left
    -- next state logic
    d(num_of_bits - 2 DOWNTO 0) <= q(num_of_bits - 1 DOWNTO 1);
    d(num_of_bits - 1)         <= q(num_of_bits - tap_low) XOR q(num_of_bits - tap_high); --
    ↳ feedback

    -- outputs
    noise_o <= q(0);
    prbs_o  <= q;
    eoc_o   <= '1' WHEN q = init ELSE '0'; -- end/start of cycle

    state_register : q <= init WHEN rst_ni = '0' ELSE
        d WHEN rising_edge(clk_i) AND en_pi = '1';

```

```
END ARCHITECTURE rtl;
```

noise generator:

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY noise_generator IS
  PORT (
    clk_i      : IN  std_ulogic;
    rst_ni     : IN  std_ulogic;
    en_pi      : IN  std_ulogic; -- enable for frequency controlled output of noise
    ↪ (pulsed enable)
    en_noise_generator_i : IN  std_ulogic; -- enable noise generator outputs else zero (continuous
    ↪ enable)
    noise_prbsg_length_i : IN  std_ulogic_vector(7 DOWNTO 0);
    prbs_o     : OUT std_ulogic_vector(22 DOWNTO 0);
    noise_o    : OUT std_ulogic;
    eoc_o     : OUT std_ulogic
  );
END ENTITY noise_generator;

ARCHITECTURE structure OF noise_generator IS

  COMPONENT config_noise_generator IS
    GENERIC (
      num_of_bits : positive;
      tap_high    : positive;
      tap_low     : positive);
    PORT (
      en_pi : IN  std_ulogic;
      clk_i : IN  std_ulogic;
      rst_ni : IN  std_ulogic;
      prbs_o : OUT std_ulogic_vector(num_of_bits - 1 DOWNTO 0);
      noise_o : OUT std_ulogic;
      eoc_o : OUT std_ulogic);
  END COMPONENT config_noise_generator;

  CONSTANT idx_4bit  : natural := 0;
  CONSTANT idx_7bit  : natural := 1;
  CONSTANT idx_15bit : natural := 2;
  CONSTANT idx_17bit : natural := 3;
  CONSTANT idx_20bit : natural := 4;
  CONSTANT idx_23bit : natural := 5;

  SIGNAL en : std_ulogic;
  SIGNAL ens : std_ulogic_vector(5 DOWNTO 0);
  SIGNAL clk : std_ulogic;
  SIGNAL rst : std_ulogic;

  SIGNAL prbs4_o : std_ulogic_vector(3 DOWNTO 0);
  SIGNAL prbs7_o : std_ulogic_vector(6 DOWNTO 0);
  SIGNAL prbs15_o : std_ulogic_vector(14 DOWNTO 0);
  SIGNAL prbs17_o : std_ulogic_vector(16 DOWNTO 0);
  SIGNAL prbs20_o : std_ulogic_vector(19 DOWNTO 0);
  SIGNAL prbs23_o : std_ulogic_vector(22 DOWNTO 0);
  SIGNAL prbs_us : unsigned(22 DOWNTO 0); -- for resize to work temporary signal
  SIGNAL prbs_us_switch : unsigned(22 DOWNTO 0);
```

```
SIGNAL noises : std_ulogic_vector (5 DOWNT0 0);
SIGNAL noise  : std_ulogic;
SIGNAL noise_switch : std_ulogic;

SIGNAL eocs : std_ulogic_vector(5 DOWNT0 0);
SIGNAL eoc  : std_ulogic;
SIGNAL eoc_switch : std_ulogic;
```

BEGIN

```
noise_generator_4 : config_noise_generator
  GENERIC MAP (
    num_of_bits => 4,
    tap_high    => 4,
    tap_low     => 3)
  PORT MAP (
    en_pi  => ens(idx_4bit),
    clk_i  => clk,
    rst_ni => rst,
    prbs_o => prbs4_o,
    noise_o => noises(idx_4bit),
    eoc_o  => eocs(idx_4bit));

noise_generator_7 : config_noise_generator
  GENERIC MAP (
    num_of_bits => 7,
    tap_high    => 7,
    tap_low     => 6)
  PORT MAP (
    en_pi  => ens(idx_7bit),
    clk_i  => clk,
    rst_ni => rst,
    prbs_o => prbs7_o,
    noise_o => noises(idx_7bit),
    eoc_o  => eocs(idx_7bit));

noise_generator_15 : config_noise_generator
  GENERIC MAP (
    num_of_bits => 15,
    tap_high    => 15,
    tap_low     => 14)
  PORT MAP (
    en_pi  => ens(idx_15bit),
    clk_i  => clk,
    rst_ni => rst,
    prbs_o => prbs15_o,
    noise_o => noises(idx_15bit),
    eoc_o  => eocs(idx_15bit));

noise_generator_17 : config_noise_generator
  GENERIC MAP (
    num_of_bits => 17,
    tap_high    => 17,
    tap_low     => 14)
  PORT MAP (
    en_pi  => ens(idx_17bit),
    clk_i  => clk,
    rst_ni => rst,
    prbs_o => prbs17_o,
    noise_o => noises(idx_17bit),
    eoc_o  => eocs(idx_17bit));
```



```

noise_generator_20 : config_noise_generator
  GENERIC MAP (
    num_of_bits => 20,
    tap_high    => 20,
    tap_low     => 17)          -- also available with 3
  PORT MAP (
    en_pi  => ens(idx_20bit),
    clk_i  => clk,
    rst_ni => rst,
    prbs_o => prbs20_o,
    noise_o => noises(idx_20bit),
    eoc_o  => eocs(idx_20bit));

noise_generator_23 : config_noise_generator
  GENERIC MAP (
    num_of_bits => 23,
    tap_high    => 23,
    tap_low     => 18)
  PORT MAP (
    en_pi  => ens(idx_23bit),
    clk_i  => clk,
    rst_ni => rst,
    prbs_o => prbs23_o,
    noise_o => noises(idx_23bit),
    eoc_o  => eocs(idx_23bit));

-- every time there is a change in signals in the process sensitivity list, all
-- of the sequential statements in the process are re-evaluated
switch : PROCESS(noise_prbsg_length_i, en, eocs, noises,
                 prbs4_o, prbs7_o, prbs15_o, prbs17_o, prbs20_o, prbs23_o)
BEGIN
  CASE noise_prbsg_length_i IS
    WHEN "00000000" =>
      prbs_us <= resize(unsigned(prbs4_o), prbs_o'length);
      noise   <= noises(idx_4bit);
      eoc     <= eocs(idx_4bit);
      ens     <= (idx_4bit => en, OTHERS => '0');
    WHEN "00000001" =>
      prbs_us <= resize(unsigned(prbs7_o), prbs_o'length);
      noise   <= noises(idx_7bit);
      eoc     <= eocs(idx_7bit);
      ens     <= (idx_7bit => en, OTHERS => '0');
    WHEN "00000010" =>
      prbs_us <= resize(unsigned(prbs15_o), prbs_o'length);
      noise   <= noises(idx_15bit);
      eoc     <= eocs(idx_15bit);
      ens     <= (idx_15bit => en, OTHERS => '0');
    WHEN "00000011" =>
      prbs_us <= resize(unsigned(prbs17_o), prbs_o'length);
      noise   <= noises(idx_17bit);
      eoc     <= eocs(idx_17bit);
      ens     <= (idx_17bit => en, OTHERS => '0');
    WHEN "00000100" =>
      prbs_us <= resize(unsigned(prbs20_o), prbs_o'length);
      noise   <= noises(idx_20bit);
      eoc     <= eocs(idx_20bit);
      ens     <= (idx_20bit => en, OTHERS => '0');
    WHEN "00000101" =>
      prbs_us <= resize(unsigned(prbs23_o), prbs_o'length);
      noise   <= noises(idx_23bit);
      eoc     <= eocs(idx_23bit);

```

```

    ens    <= (idx_23bit => en, OTHERS => '0');
    WHEN OTHERS =>
        prbs_us <= (OTHERS => '0');
        noise   <= '0';
        eoc     <= '0';
        ens     <= (OTHERS => '0');
    END CASE;
END PROCESS switch;

clk    <= clk_i;
rst    <= rst_ni;
en     <= en_pi;

prbs_us_switch <= prbs_us WHEN en_noise_generator_i = '1' ELSE (OTHERS => '0');
noise_switch <= noise WHEN en_noise_generator_i = '1' ELSE '0';
eoc_switch <= eoc WHEN en_noise_generator_i = '1' ELSE '0';

prbs_o <= (OTHERS => '0') WHEN rst = '0' ELSE
    std_ulogic_vector(prbs_us_switch) WHEN rising_edge(clk);
noise_o <= '0' WHEN rst = '0' ELSE
    noise_switch WHEN rising_edge(clk);
eoc_o <= '0' WHEN rst = '0' ELSE
    eoc_switch WHEN rising_edge(clk);

END ARCHITECTURE structure;

```

pwm generator:

```

-- Leo Hillinger and Ruairí Dillon 28/05/2021

-- Description: Intakes an enable, system clock, reset and a value to set the
-- width (i.e. frequency). The width is the size of the whole signal (high and
-- low). It then outputs a signal which forms the pwm of the set size.

LIBRARY ieee;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY pwm_generator IS

    PORT(
        en_pi      : IN  std_ulogic;           -- enable pin
        rst_ni     : IN  std_ulogic;           -- reset
        pwm_width_i : IN  std_ulogic_vector(7 DOWNTO 0); -- size of the pwm total signal
        clk_i      : IN  std_ulogic;           -- clock in
        pwm_o      : OUT std_ulogic;           -- output signal from module
    );

END pwm_generator;

ARCHITECTURE rtl OF pwm_generator IS

    SIGNAL next_state, current_state : unsigned(7 DOWNTO 0); -- states

    SIGNAL pwm_temp : std_ulogic; -- temporary place holder for state logic below

BEGIN
    -- "just a down counter"
    -- next state is "11111111" current state is equal zero. this is then used to

```

```

-- be compared to the requested width from freq_control
-- the width is the size of the whole signal (high and
-- low). It then outputs a signal which forms the pwm of the set size.
--current state will be equal to "00000000" when the reset is pressed, or
--else it will be equal to the next_state value when enabled.
next_state_logic : next_state <= to_unsigned(255, 8) WHEN current_state = 0 ELSE
                                current_state - 1;

state_register : current_state <= (others => '0') WHEN rst_ni = '0' ELSE
                                next_state WHEN rising_edge(clk_i) AND (en_pi = '1');

-- sets the output value to pwm temp when current state is lesser than the
-- width, thus making the desired pulse width proportional to the 8 bits (255).
counter_output : pwm_temp <= '1' WHEN current_state < unsigned(pwm_width_i) ELSE
                                '0';

-- setting the output to a register for integration with other modules
output_register : pwm_o <= '0' WHEN rst_ni = '0' ELSE
                    pwm_temp WHEN rising_edge(clk_i);

END rtl;

```

frequency control:

```

-----
-- Module      : noise_freq_control
-----
-- Author      : Leo Hillinger, Ruairi Dillon & David Cunningham
-- Company     : University of Applied Sciences Augsburg
-----
-- Description: This module is to act like the frequency controller for the
-- three generators in the project.
-----
-- Revisions  : see end of file
-----

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY freq_control IS

    PORT (clk_i      : IN  std_ulogic;
          rst_ni     : IN  std_ulogic;
          en_pi      : IN  std_ulogic;
          count_o    : OUT std_ulogic_vector(7 DOWNTO 0);
          freq_o     : OUT std_ulogic;
          period_i   : IN  std_ulogic_vector(7 DOWNTO 0)
          );
END freq_control;

ARCHITECTURE rtl OF freq_control IS

    SIGNAL next_state, current_state : unsigned(7 DOWNTO 0);

    CONSTANT zero : unsigned(current_state'length-1 DOWNTO 0) := (OTHERS => '0'); -- means vector
    ⇨ with only zeros

```

```

-- "The constant is like a variable object type, the value of which cannot
-- be changed. A signal object can be of different types; we saw before, for
--example, that a signal object can be of type std logic or of other types
--like integer, custom types, etc. The same applies for variable objects."

BEGIN

    -- includes decrementer and modulo logic
    next_state_logic : next_state <= unsigned(period_i) WHEN current_state = 0 ELSE
                        current_state - 1;

    state_register : current_state <= zero WHEN rst_ni = '0' ELSE
                        next_state WHEN rising_edge(clk_i) AND (en_pi = '1');

    counter_output : count_o <= std_ulogic_vector(current_state);

    terminal_count : freq_o <= '1' WHEN current_state = 0 ELSE '0';

END rtl;

-----
-- Revisions:
-- -----
-- $Id:$
-----

```

register file:

```

-----
-- Module      : regfile
-----
-- Author       : <johann.fauber@hs-augsburg.de>
-- Company      : University of Applied Sciences Augsburg
-- Copyright (c) 2021 <johann.fauber@hs-augsburg.de>
-----
-- Description: Register File - parameterisable by data width and address width
-----
-- Revisions    : see end of file
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY regfile IS
    GENERIC(
        ADDR_WIDTH : integer := 4;
        DATA_WIDTH : integer := 8
    );
    PORT(
        clk_i          : IN  std_ulogic;
        wr_en_i        : IN  std_ulogic;
        w_addr_i        : IN  std_ulogic_vector (ADDR_WIDTH-1 DOWNTO 0);
        r_addr_i        : IN  std_ulogic_vector (ADDR_WIDTH-1 DOWNTO 0);
        w_data_i        : IN  std_ulogic_vector (DATA_WIDTH-1 DOWNTO 0);

        system_control_o : OUT std_ulogic_vector(1 DOWNTO 0);
    );
END regfile;

```

```

pwm_pulse_width_o    : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pwm_period_o         : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pwm_control_o        : OUT std_ulogic_vector(1 DOWNT0 0);
noise_length_o       : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
noise_period_o       : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
noise_control_o      : OUT std_ulogic_vector(1 DOWNT0 0);
pattern_mem_depth_o  : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pattern_period_o     : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
pattern_control_o    : OUT std_ulogic_vector(2 DOWNT0 0);
r_data_o             : OUT std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0)
);
END regfile;

ARCHITECTURE rtl OF regfile IS
    TYPE array_2d_t IS ARRAY (0 TO 2**ADDR_WIDTH-1) OF -- array = (2^address width)-1
        std_ulogic_vector(DATA_WIDTH-1 DOWNT0 0);
    SIGNAL array_reg : array_2d_t;
BEGIN
    PROCESS(clk_i)
    BEGIN
        IF rising_edge(clk_i) THEN
            IF wr_en_i = '1' THEN -- if the write is enabled
                array_reg(to_integer(unsigned(w_addr_i))) <= w_data_i; -- then it takes address, turns
-- to integer for use as index of array,
                END IF; -- then it writes data to the
-- array at the index of address
            END IF;
        END PROCESS;

        system_control_o <= array_reg(1)(1 DOWNT0 0); -- because system control is two bits
        pwm_pulse_width_o <= array_reg(4);
        pwm_period_o <= array_reg(5);
        pwm_control_o <= array_reg(6)(1 DOWNT0 0);
        noise_length_o <= array_reg(8);
        noise_period_o <= array_reg(9);
        noise_control_o <= array_reg(11)(1 DOWNT0 0);
        pattern_mem_depth_o <= array_reg(12);
        pattern_period_o <= array_reg(14);
        pattern_control_o <= array_reg(15)(2 DOWNT0 0); -- because pattern control has three bits to
-- write to

-- read port
        r_data_o <= array_reg(to_integer(unsigned(r_addr_i)));
    END rtl;

```

del tsg:

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY del_tsg IS
    PORT (
        CLOCK_50 : IN std_ulogic;           -- 50 MHz Clock

        KEY0 : IN std_ulogic;                -- KEY[0] = rst_ni

        KEY2 : IN std_ulogic;                -- KEY[2] = ext_trig
        SW0 : IN std_ulogic;                 -- SW0=0 pattern_o LEDR[7:0]
        -- SW0=1 prbs_o LEDR[7:0]
    );

```

```

UART_RXD : IN std_ulogic;          -- UART_RXD = rxd_i

LEDR  : OUT std_ulogic_vector(9 DOWNTO 0); -- LEDR[9] = pwm_o
LEDG  : OUT std_ulogic_vector(7 DOWNTO 0); -- LEDG[7] = noise_o, [5:3]
      -- = ALU, [1:0] = KEY
HEX0  : OUT std_ulogic_vector(6 DOWNTO 0); -- register data low
HEX1  : OUT std_ulogic_vector(6 DOWNTO 0); -- register data high
HEX2  : OUT std_ulogic_vector(6 DOWNTO 0); -- register address
HEX3  : OUT std_ulogic_vector(6 DOWNTO 0); -- sequence count
GPO_1 : OUT std_ulogic_vector(8 DOWNTO 0) -- Output Connector GPO_1
      -- GPO_1[0] = clk_i
      -- GPO_1[1] = en_serial_i
      -- GPO_1[2] = serial_data_i
      -- GPO_1[3] = rxd_rdy_o
      -- GPO_1[4] = frame_err_o
      -- GPO_1[5] = parity_err_o
      -- GPO_1[6] = pwm
      -- GPO_1[7] = noise
      -- GPO_1[8] = eoc

);
END ENTITY del_tsg;

ARCHITECTURE structure OF del_tsg IS

  COMPONENT tsg IS
    PORT (
      clk_i      : IN std_ulogic;
      rst_ni     : IN std_ulogic;
      en_tsg_pi  : IN std_ulogic;
      en_serial_i : IN std_ulogic;
      serial_data_i : IN std_ulogic;
      rxd_rdy_o  : OUT std_ulogic;
      ext_trig_i  : IN std_ulogic;
      pwm_o      : OUT std_ulogic;
      noise_o    : OUT std_ulogic;
      prbs_o     : OUT std_ulogic_vector(22 DOWNTO 0);
      eoc_o      : OUT std_ulogic;
      pattern_o  : OUT std_ulogic_vector(7 DOWNTO 0);
      pattern_valid_o : OUT std_ulogic;
      tc_pm_count_o : OUT std_ulogic;
      regfile_o  : OUT std_ulogic_vector(7 DOWNTO 0);
      addr_reg_o : OUT std_ulogic_vector(7 DOWNTO 0);
      data_reg_o : OUT std_ulogic_vector(7 DOWNTO 0));
  END COMPONENT tsg;

  COMPONENT cntdnmodm IS
    GENERIC (
      n : natural;
      m : natural);
    PORT (
      clk_i : IN std_ulogic;
      rst_ni : IN std_ulogic;
      en_pi : IN std_ulogic;
      count_o : OUT std_ulogic_vector(n-1 DOWNTO 0);
      tc_o : OUT std_ulogic);
  END COMPONENT cntdnmodm;

  COMPONENT synchroniser IS
    PORT (
      clk_i : IN std_ulogic;
      rst_ni : IN std_ulogic;

```

```

    async_i : IN std_ulogic;
    sync_o  : OUT std_ulogic);
END COMPONENT synchroniser;

COMPONENT falling_edge_detector IS
  PORT (
    clk_i : IN std_ulogic;
    rst_ni : IN std_ulogic;
    x_i    : IN std_ulogic;
    fall_o : OUT std_ulogic);
END COMPONENT falling_edge_detector;

COMPONENT sequence_detector IS
  PORT (
    clk      : IN std_ulogic;
    rst_n    : IN std_ulogic;
    ser_i    : IN std_ulogic;
    done_o   : OUT std_ulogic);
END COMPONENT sequence_detector;

COMPONENT alu IS
  PORT (
    a_i : IN std_ulogic_vector(2 DOWNTO 0);
    b_i : IN std_ulogic_vector(2 DOWNTO 0);
    sel_i : IN std_ulogic_vector(1 DOWNTO 0);
    y_o : OUT std_ulogic_vector(2 DOWNTO 0));
END COMPONENT alu;

COMPONENT binto7segment IS
  PORT (
    bin_i : IN std_ulogic_vector(3 DOWNTO 0);
    segments_o : OUT std_ulogic_vector(6 DOWNTO 0));
END COMPONENT binto7segment;

-- basic signals
SIGNAL clk_i : std_ulogic;
SIGNAL rst_ni : std_ulogic;
SIGNAL en_tsg_pi : std_ulogic;
SIGNAL en_serial_i : std_ulogic;
SIGNAL serial_data_i : std_ulogic;
SIGNAL ext_trig_i : std_ulogic;

SIGNAL en_seq_cnt : std_ulogic;
SIGNAL count_value : unsigned(3 DOWNTO 0);

SIGNAL pwm : std_ulogic;
SIGNAL noise : std_ulogic;
SIGNAL prbs : std_ulogic_vector(22 DOWNTO 0);
SIGNAL pattern : std_ulogic_vector(7 DOWNTO 0);
SIGNAL addr_reg : std_ulogic_vector(7 DOWNTO 0);
SIGNAL data_reg : std_ulogic_vector(7 DOWNTO 0);

-----
-- signals for debugging at GPIO
-----

SIGNAL rxd_rdy : std_ulogic;
SIGNAL parity_err : std_ulogic;
SIGNAL frame_err : std_ulogic;
SIGNAL eoc : std_ulogic;
-----

BEGIN

```

```

test_signal_generator : tsg
  PORT MAP (
    clk_i          => clk_i,
    rst_ni         => rst_ni,
    en_tsg_pi      => en_tsg_pi,
    en_serial_i    => en_serial_i,
    serial_data_i  => serial_data_i,
    rxd_rdy_o      => rxd_rdy,
    ext_trig_i     => ext_trig_i,
    pwm_o          => pwm,
    noise_o        => noise,
    prbs_o         => prbs,
    eoc_o          => eoc,
    pattern_o      => pattern,
    pattern_valid_o => OPEN,
    tc_pm_count_o  => OPEN,
    regfile_o      => OPEN,
    addr_reg_o     => addr_reg,
    data_reg_o     => data_reg);

time_base : cntdnmodm          -- 10 MHz
  GENERIC MAP (
    n => 4,
    m => 5)
  PORT MAP (
    clk_i  => clk_i,
    rst_ni => rst_ni,
    en_pi  => '1',
    count_o => OPEN,
    tc_o   => en_tsg_pi);

baud_oversample : cntdnmodm    -- baudrate 9600 with 50MHz clock
  GENERIC MAP (
    n => 9,
    m => 326)
  PORT MAP (
    clk_i  => clk_i,
    rst_ni => rst_ni,
    en_pi  => '1',
    count_o => OPEN,
    tc_o   => en_serial_i);

sync : synchroniser
  PORT MAP (
    clk_i  => clk_i,
    rst_ni => rst_ni,
    async_i => UART_RXD,
    sync_o  => serial_data_i);

external_trigger : falling_edge_detector
  PORT MAP (
    clk_i  => clk_i,
    rst_ni => rst_ni,
    x_i    => KEY2,
    fall_o => ext_trig_i);

seq_detector : sequence_detector
  PORT MAP (
    clk  => clk_i,
    rst_n => rst_ni,
    ser_i => noise,

```



```

done_o => en_seq_cnt);

arithmetic : alu
PORT MAP (
    a_i    => pattern(2 DOWNTO 0),
    b_i    => pattern(5 DOWNTO 3),
    sel_i  => pattern(7 DOWNTO 6),
    y_o    => LEDG(5 DOWNTO 3));

HEX_0 : binto7segment          -- register data low
PORT MAP (
    bin_i    => data_reg(3 DOWNTO 0),
    segments_o => HEX0);

HEX_1 : binto7segment          -- register data high
PORT MAP (
    bin_i    => data_reg(7 DOWNTO 4),
    segments_o => HEX1);

HEX_2 : binto7segment          -- register address
PORT MAP (
    bin_i    => addr_reg(3 DOWNTO 0),
    segments_o => HEX2);

HEX_3 : binto7segment          -- sequence count
PORT MAP (
    bin_i    => std_ulogic_vector(count_value),
    segments_o => HEX3);

clk_i      <= CLOCK_50;
rst_ni     <= KEY0;
LEDG(1 DOWNTO 0) <= KEY2 & KEY0;

counter : count_value <= to_unsigned(0, 4) WHEN rst_ni = '0' -- sequence counter
        ELSE count_value + 1 WHEN rising_edge(clk_i) AND en_seq_cnt = '1';

LEDR(9) <= pwm;
LEDG(7) <= noise;

LEDR(7 DOWNTO 0) <= pattern(7 DOWNTO 0) WHEN SW0 = '0'
        ELSE prbs(7 DOWNTO 0);

LEDR(8) <= '0';
LEDG(6) <= '0';
LEDG(2) <= '0';

-----
-- debugging
-----

-- clk_i routed to output port
GPO_1(0) <= clk_i;

-- baud rate oversampling
GPO_1(1) <= en_serial_i;

-- serial data input connected to GPIO
GPO_1(2) <= serial_data_i;

-- finished transfer cyle
GPO_1(3) <= rxd_rdy;

-- frame error

```

```

GPO_1(4) <= frame_err;

-- parity error
GPO_1(5) <= parity_err;

-- pwm
GPO_1(6) <= pwm;

-- noise
GPO_1(7) <= noise;

-- noise
GPO_1(8) <= eoc;

```

END ARCHITECTURE structure;

de1 components:

```

-----
-- Module      : cntdnmodm
-----

-- Author      : Johann Faerber
-- Company     : University of Applied Sciences Augsburg
-----

-- Description: Modulo-m n-Bit Down-Counter
--              including a low-active asynchronous reset input rst_ni
--              and a high-active enable input en_pi
--              additionally, a high_active output signal tc_o is produced,
--              when the counter reaches it's minimum value
-----

-- Revisions   : see end of file
-----

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY cntdnmodm IS
  GENERIC (
    n : natural := 4;           -- counter width
    m : natural := 10);        -- modulo value
  PORT (clk_i   : IN  std_ulogic;
        rst_ni  : IN  std_ulogic;
        en_pi   : IN  std_ulogic;
        count_o : OUT std_ulogic_vector(n-1 DOWNT0 0);
        tc_o    : OUT std_ulogic
        );
END cntdnmodm;

ARCHITECTURE rtl OF cntdnmodm IS

  SIGNAL next_state, current_state : unsigned(n-1 DOWNT0 0);

  CONSTANT zero: unsigned(current_state'length-1 DOWNT0 0) := (OTHERS => '0'); -- means vector
  ⇨ with only zeros

BEGIN

  -- includes decrementer and modulo logic
  next_state_logic : next_state <= to_unsigned(m-1, n) WHEN current_state = 0 ELSE
                                current_state - 1;

```

```

state_register : current_state <= zero WHEN rst_ni = '0' ELSE
    next_state WHEN rising_edge(clk_i) AND (en_pi = '1');

counter_output : count_o <= std_ulogic_vector(current_state);

terminal_count : tc_o <= '1' WHEN current_state = 0 ELSE '0';

END rtl;

-----
-- Revisions:
-- -----
-- $Id:$
-----

```

del components:

```

-----
-- Module      : falling_edge_detector
-----
-- Author       : Johann Faerber
-- Company      : University of Applied Sciences Augsburg
-----
-- Description: detects a falling edge of input signal x_i
--              and produces a high-active signal for one clock period at
--              output fall_o
--              clk_i  __|__|__|__|__|__|__|__|__|__|__|__|__|
--              x_i    -----|-----|-----|-----|
--              fall_o _____|-----|-----|-----|
-----
-- Revisions    : see end of file
-----

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

ENTITY falling_edge_detector IS
    PORT (
        clk_i  : IN  std_ulogic;
        rst_ni : IN  std_ulogic;
        x_i     : IN  std_ulogic;
        fall_o  : OUT std_ulogic
    );
END falling_edge_detector;

-----
-- Revisions:
-- -----
-- $Id:$
-----

```

del components:

```

-----
-- Module      : rtl
-----
-- Author       : Johann Faerber

```

```

-- Company      : University of Applied Sciences Augsburg
-----
-- Description: detects a falling edge of input signal x_i
--              and produces a high-active signal for one clock period at
--              output fall_o
--              clk_i  __|__|__|__|__|__|__|__|__|__|__|__|__|__|__|__|
--              x_i    ----|-----|-----|-----|-----|-----|
--              fall_o  -----|-----|-----|-----|-----|-----|
--
--              rtl model based on two flip flops with output logic
-----
-- Revisions   : see end of file
-----

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

ARCHITECTURE rtl OF falling_edge_detector IS

    SIGNAL q0, q1 : std_ulogic;          -- D-Type Flip-Flop outputs

BEGIN

    dflop0 : q0 <= '0' WHEN (rst_ni = '0') ELSE
                x_i WHEN rising_edge(clk_i);

    dflop1 : q1 <= '0' WHEN (rst_ni = '0') ELSE
                q0 WHEN rising_edge(clk_i);

    output_logic : fall_o <= NOT q0 AND q1;

END rtl;

-----
-- Revisions:
-----
-- $Id:$
-----

```

de1 components:

```

-----
-- Module      : binto7segment
-----
-- Author      : Johann Faerber
-- Company     : University of Applied Sciences Augsburg
-----
-- Description: binary-to-7-segment decoder
--              function modelled as a truth table
--              using a selected signal assignment
--              segments get illuminated by a low-active signal
-----
-- Revisions   : see end of file
-----

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

ENTITY binto7segment IS
    PORT (bin_i      : IN  std_ulogic_vector(3 DOWNTO 0);
          segments_o : OUT std_ulogic_vector(6 DOWNTO 0)
    );

```

```

END binto7segment;

ARCHITECTURE truthtable OF binto7segment IS

    -- seven-segment positions
    --
    -- segment positions      input vector index      segment name
    --      a                  0                      =>      a
    --      ---                  1                      =>      b
    --  f |      | b            2                      =>      c
    --      ---      <- g      3                      =>      d
    --  e |      | c            4                      =>      e
    --      ---                  5                      =>      f
    --      d                  6                      =>      g

BEGIN

    decoder : WITH bin_i SELECT
        segments_o <=
            -- outputs:      |      inputs:
            -----
            -- index        |      number displayed
            -- 6543210      |
            -----
            "1000000" WHEN "0000", -- 0
            "1111001" WHEN "0001", -- 1
            "0100100" WHEN "0010", -- 2
            "0110000" WHEN "0011", -- 3
            "0011001" WHEN "0100", -- 4
            "0010010" WHEN "0101", -- 5
            "0000010" WHEN "0110", -- 6
            "1111000" WHEN "0111", -- 7
            "0000000" WHEN "1000", -- 8
            "0010000" WHEN "1001", -- 9
            "0001000" WHEN "1010", -- A
            "0000011" WHEN "1011", -- b
            "1000110" WHEN "1100", -- C
            "0100001" WHEN "1101", -- d
            "0000100" WHEN "1110", -- e
            "0001110" WHEN "1111", -- F
            "0000110" WHEN OTHERS; -- displays Symbol 'E' for ERROR

END truthtable;

-----
-- Revisions:
-- -----
-- $Id:$
-----

```

de1 components:

```

-----
-- Module      : ALU
-----
-- Author      : Hillinger, Dillon & Cunningham
-- Company     : University of Applied Sciences Augsburg
-----
-- Description: This module offers the use the ability to perform logical
-- arithmetic on two three bit signals. It also offers the user the ability to
-- select an operation via the sel_i variable.

```

```

-- In the scope of the project, the output is meant to be sent to LEDRs. The
-- pattern generator will be connected (first three wired to a_i, next three to
-- b_i and the final two to be used for the select.
-----
-- Revisions : see end of file
-----
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY alu IS
    PORT (a_i : IN std_ulogic_vector(2 DOWNTO 0);      -- data input a
          b_i : IN std_ulogic_vector(2 DOWNTO 0);      -- data input b
          sel_i : IN std_ulogic_vector(1 DOWNTO 0);    -- select which input is connected to y

          y_o : OUT std_ulogic_vector(2 DOWNTO 0)      -- data output y
    );
END ENTITY alu;

ARCHITECTURE rtl OF alu IS

    SIGNAL y_out : unsigned(2 DOWNTO 0); -- set as unsigned so it can be written
                                         -- to after the conversion

BEGIN

    WITH sel_i SELECT y_out <= -- uses select value to determine the operation below
        (unsigned(a_i) + unsigned(b_i)) WHEN "00", -- converted to unsigned to make logical arithmetic
        ↪ possible
        (unsigned(a_i) - unsigned(b_i)) WHEN "01", -- WHEN statement
        (unsigned(a_i and b_i)) WHEN "10", -- possible issues with data type
        (unsigned(a_i or b_i)) WHEN "11", -- possible issues with data type
        (OTHERS => '0') WHEN others;

    y_o <= std_ulogic_vector(y_out); -- converting the output to std_ulogic_vect
                                     -- to output

END rtl;

-----
-- Revisions:
-- -----
-- $Id:$
-----

```

del components:

```

-- This file was generated by
-- Qfsm Version 0.55
-- (C) Stefan Duffner, Rainer Strobel, Aaron Erhardt

-- Inputs:  ser_i
-- State/Output done_o
-- State_0      0
-- State_1      0
-- State_2      0
-- State_3      1

LIBRARY IEEE;

```

```

USE IEEE.std_logic_1164.ALL;

ENTITY sequence_detector IS
  PORT (clk: IN std_ulogic;
        rst_n: IN std_ulogic;
        ser_i: IN std_ulogic;
        done_o: OUT std_ulogic);
END sequence_detector;

ARCHITECTURE behave OF sequence_detector IS

  TYPE state_type IS (State_0, State_1, State_2, State_3);
  SIGNAL next_state, current_state : state_type;

BEGIN
  state_register: PROCESS (rst_n, clk)
  BEGIN
    IF rst_n='0' THEN
      current_state <= State_0;
    ELSIF rising_edge(clk) THEN
      current_state <= next_state;
    END IF;
  END PROCESS;

  next_state_and_output_logic: PROCESS (current_state, ser_i)
    VARIABLE temp_input : std_ulogic_vector(0 DOWNTO 0);
    VARIABLE temp_output : std_ulogic_vector(0 DOWNTO 0);
  BEGIN
    temp_input(0) := ser_i;
    CASE current_state IS
      WHEN State_0 => temp_output := "0";
      IF temp_input="1" THEN
        next_state <= State_1;
      ELSIF temp_input="0" THEN
        next_state <= State_0;
      ELSE
        next_state <= current_state;
      END IF;
      WHEN State_1 => temp_output := "0";
      IF temp_input="0" THEN
        next_state <= State_2;
      ELSIF temp_input="1" THEN
        next_state <= State_1;
      ELSE
        next_state <= current_state;
      END IF;
      WHEN State_2 => temp_output := "0";
      IF temp_input="1" THEN
        next_state <= State_3;
      ELSIF temp_input="0" THEN
        next_state <= State_0;
      ELSE
        next_state <= current_state;
      END IF;
      WHEN State_3 => temp_output := "1";
      IF temp_input="0" THEN
        next_state <= State_0;
      ELSIF temp_input="1" THEN
        next_state <= State_1;
      ELSE
        next_state <= current_state;
    
```

```

        END IF;
        WHEN OTHERS => temp_output := (OTHERS => 'X');
        next_state <= State_0;
    END CASE;
    done_o <= temp_output(0);
END PROCESS;

END behave;

```

del components:

```

-- Description: Synchroniser functions by taking in asynchronous data, then it
-- goes through two flip flops, the Q of the first flip flop is connected to
-- the D of the other flipflop. The output of this is a signal synchronous with
-- the clock input.
-- Clocks and resets are common for both flipflops.

-- ASK LEO HOW THE FLIP FLOPS ARE ACTUALLY INSTANTIATED

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

entity synchroniser is
    port (
        clk_i : in std_ulogic; -- common clock
        rst_ni : in std_ulogic; -- common reset
        async_i : in std_ulogic; -- the input, asynchronous data
        sync_o : out std_ulogic -- the data ouput
    );
end entity synchroniser;

architecture rtl of synchroniser is

    signal ff1_i, ff2_i : std_ulogic; -- flip flop one and flip flop two's input
    signal ff1_o, ff2_o : std_ulogic; -- flip flop one and flip flop two's output

BEGIN

    --Sensitivity lists are parameters to a process which lists all the signals that the process is
    --> sensitive to. If any
    --of the signals change, the process will wake up, and the code within it is executed. We've
    --> already learned to
    --use the wait on and wait until statements for waking up a process when a signal changes.

    sync: process(clk_i, rst_ni) -- sensitivity list
    begin
        if rst_ni = '0' then
            ff1_o <= '0';
            ff2_o <= '0';
        elsif rising_edge(clk_i) then
            ff1_o <= ff1_i; -- connects the input of the first flip flop to the
                           -- output of the first
            ff2_o <= ff2_i;
        end if;
    end process sync;

    ff1_i <= async_i; -- setting the input as the input of flip flop 1
    ff2_i <= ff1_o; --flip flop two's input being wired to

```



```
    sync_o <= ff2_o; -- then the overall system's output  
end architecture rtl;
```